

Hindbookcenter



Hind Book Center & Photostat


MADE EASY

**Electrical Engineering
Toppers Handwritten Notes
Network Theory
By-Aditya Sir**

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

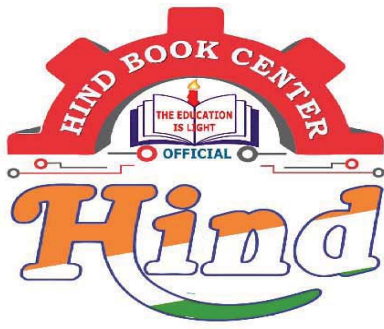**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393**



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

NETWORK THEORY

-Aditya sir

ESE: 22-24 M

≈ 14 que.

Gate: 10M


① Topics:

- ① Basics:
- ϕ, I, V, P, N
 - R, L, C
 - KVL, KCL, ohm's Law
 - Mesh Nodal
 - Equivalent R, L, C, Z

- ② Two-port Network:
- Parameters (Z, Y, h, g, T, t)
 - Interconnection
 - Gyration


- ③ Theorems:
- superposition
 - Thevenin
 - Nortons
 - Maximum power Transfer
 - Reciprocity
 - Millman's
 - Compensation
 - substitution
 - Tellegen's theorem
- Gate
- ESE

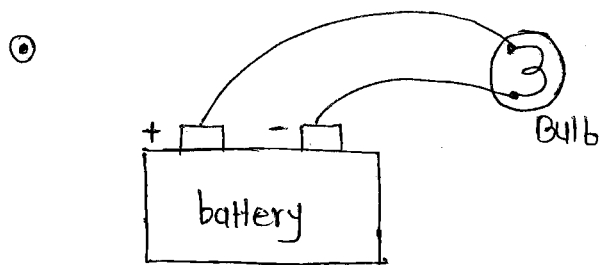- ④ Transient:
- 1st order circuit (RC, RL)
 - 2nd order circuits
 - Initial condition
 - Laplace transform



Electrical circuit : our main Aim is to transferred the energy from one Point to another Point. Hence for this We require An interconnection betⁿ electrical Compa.

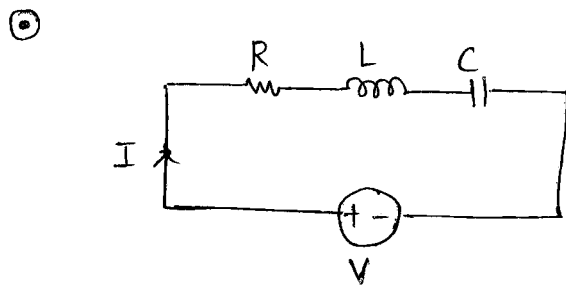Interview
Highest basic quantity in electrical Network : Charge



① Charge : • charge is the electrical property of the atomic partical of which the Matter consist of. (C)

• [Electrical Property \rightarrow Atomic Particles \rightarrow Matter]

charge on $1 e^- : -1.6 \times 10^{-19} C$

Coulomb is the large Unit of charge.

Que: How many electron contributes towards 1C of charge?

Solⁿ : $1 e^- = 1.6 \times 10^{-19} C$

$$1C = \frac{1}{1.6 \times 10^{-19}} e^- s$$

$$1C = 6.24 \times 10^{18} e^- s$$

② Law of Conservation of charge :

It states that, charge can be neither be created nor be destroyed. It can be only transferred from one body to another body.

Any eqⁿ with the help of show Law of conse. of Charge.

Continuity Eqⁿ : $\nabla \cdot \vec{J} = -\frac{d\rho_v}{dt}$

Lec-2

② Current : The flow of the electrons or the time rate of change of charge through any cross-section is called as a current. (C/s or Amp)


$$I_{av} = \frac{\Delta q}{\Delta t} \text{ C/s or Amp.}$$

• Instantaneous current $i(t)$:

$$i(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

$$i(t) = \frac{dq}{dt}$$

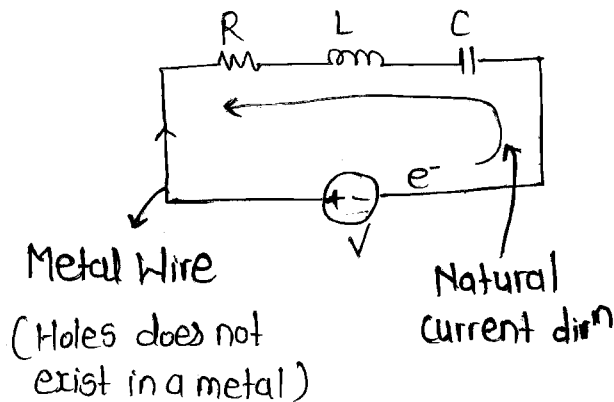• Direction of current in electrical circuit :




Conventionally, $\text{---} \rightarrow$ the current direction is taken in the direction of the positive charge moment.

Naturally, $\text{---} \rightarrow$ the current direction is in the direction of the flow of electrons.

③ Voltage : ① To move the electron from one point to another point in a particular direction & external force is required & in an electrical circuit this force is provided by the electromotive force (EMF) & it is given by

$$E = V = \frac{dW}{dq} \text{ J/C or V}$$

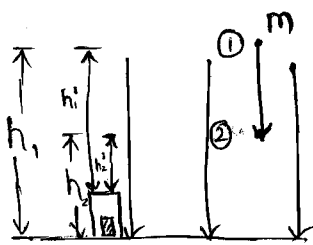
② Voltage or potential difference is the energy required to move a unit charge through an element.



Energy gained by the mass in moving from pt. ① to ②:

$$= mg(h_1 - h_2)$$


gravitational potential diff.

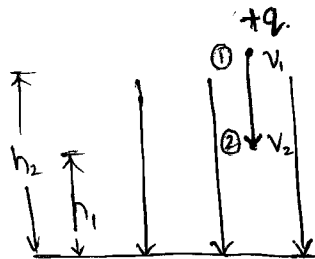


Energy gained by the charge in moving from pt ① to ②:

$$= q(V_1 - V_2)$$

Electrical potential difference.

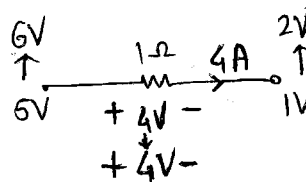

Que:

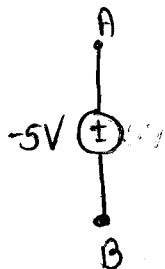


Ⓐ $V_A > V_B$

Ⓑ $V_A = V_B$

Ⓒ $V_A < V_B$

Ⓓ Cant comment

Solⁿ:

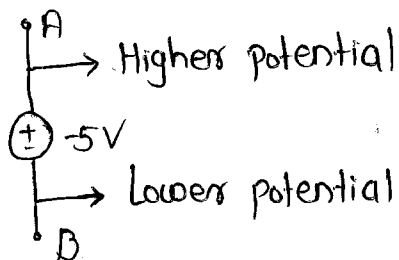

$$\text{Higher Pot.} - \text{Lower Pot.} = -5V$$

$$V_A - V_B = -5V$$


$$V_A = V_B - 5$$

④ Power: It is the time rate of change of Energy [expending or absorbing] and (Watts)

$$P = \frac{dW}{dt} \quad \text{J/s or W}$$


$$P = \frac{dW}{dq} \cdot \frac{dq}{dt}$$

$$P(t) = V(t) \cdot I(t)$$

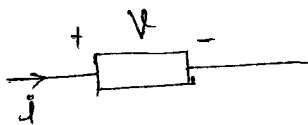

$$P = +VI$$

(a)

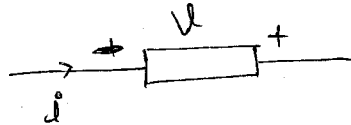

$$P = -VI$$


(b)

- Whenever we calculate the power by using the formula $V \times I$, we always get the power absorbed.


Fig. (a) Power absorbed or
power received or
power dissipated

Fig. (b) Power absorbed
is -ve. or
power is getting
delivered
($P_{del} = +VI$)

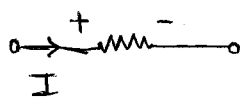Note: ① Whenever current enters into the +ve terminal of the voltage polarity, the element absorbs a power
② And when the current leaves from the +ve terminal or current enters into the -ve terminal, then the element delivers the power.




Power absorbed

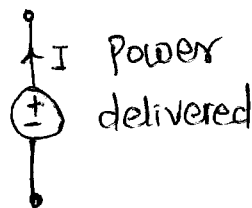


Power delivered

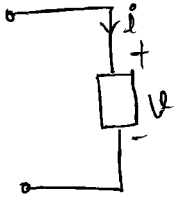
- Hence, for determine sign of the power, The voltage polarity & the ∇ n direction are important.




Power abs.
∴ Load

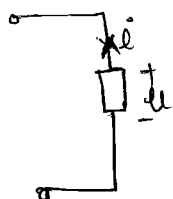


Power deli.
∴ Source

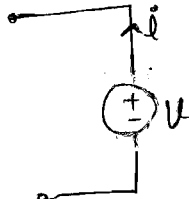


Power deli.
∴ Source

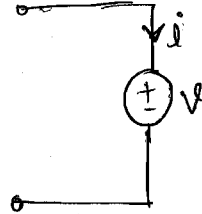

Power abs.
∴ Sink/Load

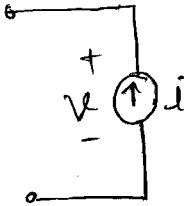

Power deli.
∴ Source

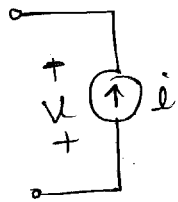

Power abs.
∴ Load

⊙ Law of Conservation of Energy :

It states that, Energy can neither be created nor be destroyed, It only be transform from one form to another Form.


∴ In Any Electrical Circuit :

$$\sum P = 0$$

$$\sum P_{del.} = \sum P_{abs.}$$

- The algebraic sum of the power at any instant of time in a circuit must be equal to zero.

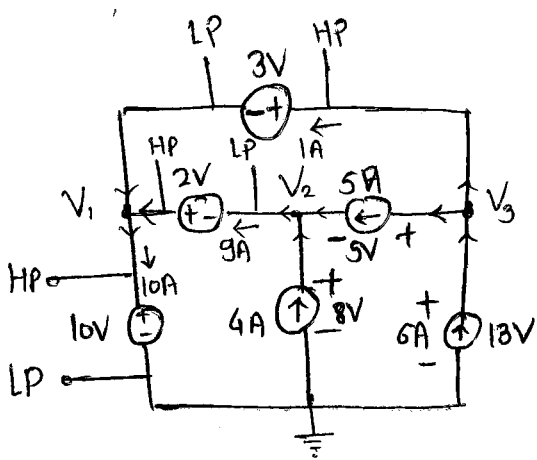Lec 3 Que. Find the power of each element In the below given electrical Network.



Solⁿ:

$$P_{10V} = +10 \times 10 = +100 \text{ W}$$

$$P_{2V} = -9 \times 2 = -18 \text{ W}$$

$$P_{3V} = +3 \times 1 = 3 \text{ W}$$

• By Nodal Analysis:

$$V_1 - 0 = 10V$$

$$V_1 = 10V$$


$$V_1 - V_2 = 2V$$

$$-V_2 = 2 - 10$$

$$V_2 = 8V$$

$$V_3 - V_1 = 3V$$

$$V_3 = 13V$$

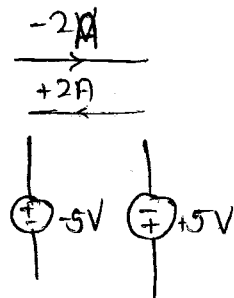

$$P_{4A} = -4 \times 8 = -32 \text{ W}$$

$$P_{5A} = +5 \times 5 = 25 \text{ W}$$

$$P_{6A} = -13 \times 6 = -78 \text{ W}$$

• Not part of Solⁿ:

$$\sum P_{abs.} = +100 + 3 + 25 \quad \dots \text{ (+ve power)}$$

$$= 128 \text{ W}$$

$$\sum P_{del.} = +8 + 32 + 78 \quad \dots \text{ (-ve power with +ve sign)}$$

$$= 128 \text{ W}$$

$$\therefore \sum P_{del.} = \sum P_{abs.}$$

Que: How many electrons flow per second through the filament of a 220V & 110W electric bulb.

Solⁿ: $P = V \times I$ $I = \frac{P}{V} = \frac{110}{220} = \frac{1}{2} \text{ Amp}$

$$I = \frac{Q}{t} = \frac{n \cdot e^-}{t}$$

where, $n = \text{Total no. of } e^-$

$$\frac{n}{t} = 3.125 \times 10^{-8}$$

$$\therefore \frac{n}{t} = \frac{I}{e^-} = \frac{\frac{1}{2}}{1.6 \times 10^{-19}}$$

⑤ Energy: It is the capacity or ability to do the work. (J or Watt-sec)

$$W(t) = \int_0^t P(t) \cdot dt$$


$$W(t) = \int_0^t V(t) \cdot i(t) \cdot dt$$

Grade 2009
 Que. A fully charged mobile phone with a 12V battery is good for 10 min talktime; Assume that during the talktime, battery delivers a constant C/n of 2A and its voltage linearly drop from 12V to 10V as shown in the fig. How much energy does the battery delivered during talktime.


$$\begin{aligned} \text{Sol}^n: W &= \int_0^t P(t) \cdot dt \\ &= \int_0^t V(t) \cdot i(t) \cdot dt \\ &= 2 \left[\int_0^{10 \text{ min}} V(t) \cdot dt \right] \end{aligned}$$

$$\begin{aligned} &= 2 \left[\left(\frac{1}{2} \times 10 \text{ min} \times (12-10) \right) + (10 \times 10) \right] \cdot 60 \\ &= 2 [10 + 100] 60 \\ &= 2 \times 6600 \end{aligned}$$

$$W = 13.2 \text{ KJ}$$

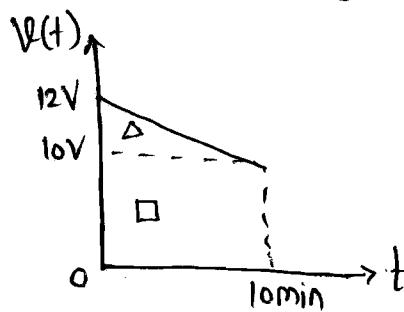

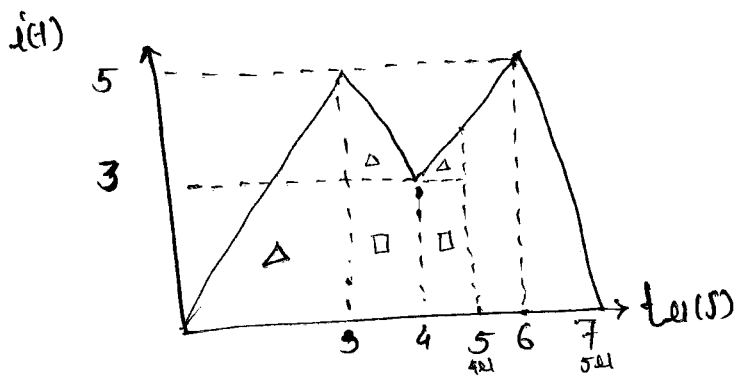que. A c/n $i(t)$ as shown in the fig. is passed thr a capacitor. A charge in μC acquire by the cap^r in 5 μs . will be ---




$$\text{Sol}^n: i(t) = \frac{dq}{dt}$$

$$q = \int_{-\infty}^t i(t) \cdot dt$$

$$q(t) = \int_{-\infty}^0 i(t) \cdot dt + \int_0^t i(t) \cdot dt$$

$$q(t) = q(0) + \int_0^t i(t) \cdot dt$$

$$q(t) = 0 + \int_0^{5u} i(t) \cdot dt$$

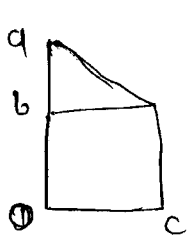

$$\begin{aligned} \text{Area} &= \frac{1}{2}(a-b)c + bc \\ &= \frac{1}{2}ac - \frac{1}{2}bc + bc \\ &= \frac{1}{2}ac + \frac{1}{2}bc \end{aligned}$$

$$\text{Area} = \frac{1}{2}(a+b)c \quad *$$

$$\therefore \text{Area} = \int_0^{3u} i(t) \cdot dt + \int_{3u}^{4u} i(t) \cdot dt + \int_{4u}^{5u} i(t) \cdot dt$$

$$= \left[\frac{1}{2} \times 5 \times 3 \right] + \left[\frac{1}{2} (5+3) \cdot 1 \right] + \left[\frac{1}{2} (4+3) \cdot 1 \right]$$

$$= \left[\frac{15}{2} + \frac{8}{2} + \frac{7}{2} \right] u$$

$$q(t) = \frac{30}{2} u$$

$$q = 15uC$$

que: q flowing through the ckt. ^{element} is given by.

$i(t) = (8t + 5)A$. Find amount of charge passing thr the element in an interval of 0 to 3 sec.

Solⁿ: Given:

$$i(t) = (8t + 5) \text{ A}$$

$$q(t) = 0 + \int_0^t i(t) dt$$

$$q(t) = 0 + \int_0^3 (8t + 5) dt$$
$$= 8 \cdot \left[\frac{t^2}{2} \right]_0^3 + 5 \cdot [t]_0^3$$

$$= 4(3)^2 + 5(3)$$


$$= 36 + 15$$

$$q(t) = 51 \text{ C}$$

Que: The power supplied by a certain battery is constant, 6 W for the 1st 5 min. then 0 for the following 2 min. the value that increases from 0 to 10 W for the next 10 min. and a power that decreases linearly from 10 W to 0 in the following 7 min.

Ⓐ What is the total energy in J. expended during this 24 min. interval. ~~second~~.

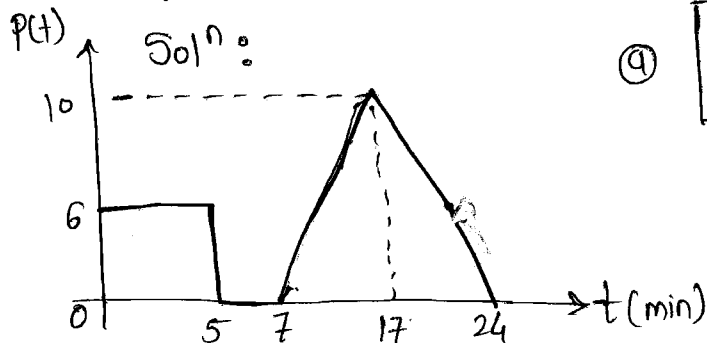Ⓑ What is the avg. power in Watt during this time.



$$\text{Ⓐ } W = \int_0^t P(t) \cdot dt$$


$$= [6 \times 5] + \left[\frac{1}{2} \times 10 \times 10 \right] +$$

$$\left[\frac{1}{2} \times 10 \times 7 \right]$$

$$= [30 + 50 + 35] \times 60$$

$$= [115 \times 60]$$

$$W = 6900 \text{ J}$$

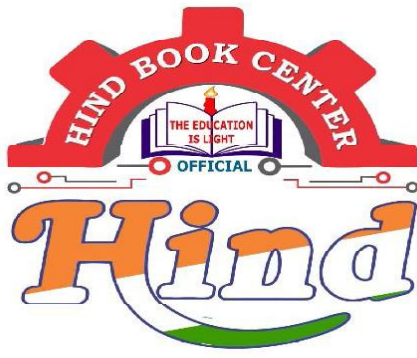

Hindbookcenter



Hind Book Center & Photostat

MADE EASY

Electrical Engineering

Toppers Handwritten Notes


02.ELECTROMAGNETIC THEORY

BY- HIMADRI SHEKHAR SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

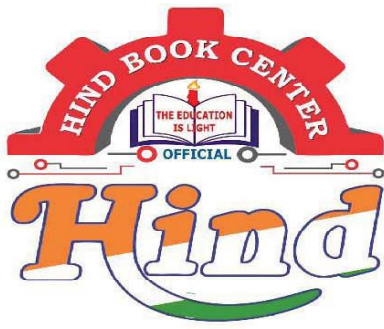Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

-∴ Vector Analysis :-I). co-ordinate system :-

There are 3-types of co-ordinate systems

- (a) Cartesian co-ordinate system (x, y, z)
- (b) cylindrical co-ordinate system (ρ, ϕ, z)
- (c) spherical co-ordinate system (r, θ, ϕ)

All these co-ordinate systems obeys two laws-

(a) Rule of orthogonality :-

(i) The dot product of two similar vectors of the same co-ordinate system results 1.

$$\text{Ex :- } \hat{a}_x \cdot \hat{a}_x = 1 \quad ; \quad \text{ca-co-system}$$

$$\hat{a}_y \cdot \hat{a}_y = 1 \quad ; \quad \text{cy-co-system}$$

$$\hat{a}_r \cdot \hat{a}_r = 1 \quad ; \quad \text{sp-co-system}$$

(ii) The dot product of two different unit vectors of the same co-ordinate system results to 0.

$$\text{Ex :- } \hat{a}_x \cdot \hat{a}_y = 0 \quad ; \quad \text{ca-co-syst.}$$

$$\hat{a}_y \cdot \hat{a}_\phi = 0 \quad ; \quad \text{cy-co-syst.}$$

$$\hat{a}_r \cdot \hat{a}_\theta = 0 \quad ; \quad \text{sp-co-syst.}$$

(b) Rule of orthogonality :-

(i) The cross product of two similar unit vectors of same co-ordinates system results to '0'.

$$\text{Ex :- } \hat{a}_x \times \hat{a}_x = 0 \quad ; \quad \text{ca-co-syst.}$$

$$\hat{a}_\phi \times \hat{a}_\phi = 0 \quad ; \quad \text{cy-co-syst.}$$


$$\hat{a}_r \times \hat{a}_r = 0 \quad ; \quad \text{sp-co-syst.}$$

(ii) The cross product of two different unit vectors of same co-ordinates system results to third unit vector which is mutually perpendicular to the initial vectors.

Ex:- $\hat{a}_x \times \hat{a}_y = \hat{a}_z$; ca. co. syst.
 $\hat{a}_y \times \hat{a}_z = \hat{a}_x$; cy. co. syst.
 $\hat{a}_z \times \hat{a}_x = \hat{a}_y$; sp. co. syst.


(iii) The direction of 3rd unit vector is found using R-H curl rule.

Ex:-

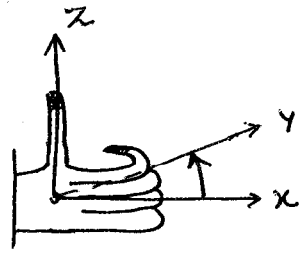


R-H curl Thumb
 x y z


⊙ ≡ out of plane
 ⊗ ≡ into the plane

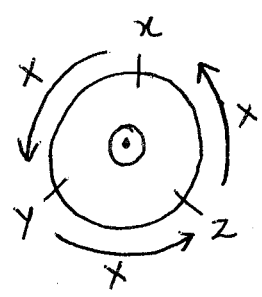

-: ca. co. system :-


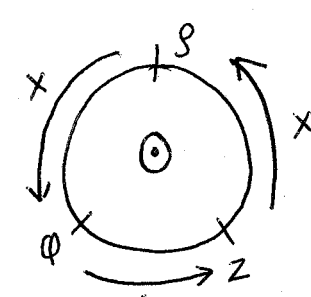


-: cy. co. system :-

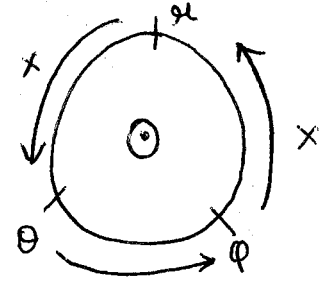


-: sp. co. system :-

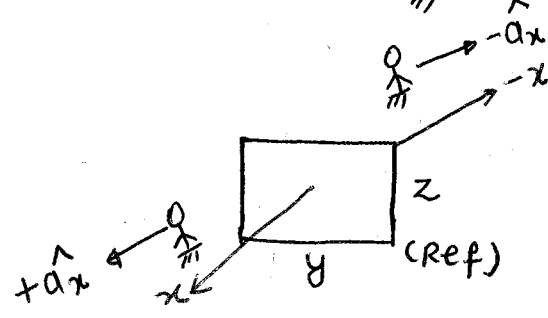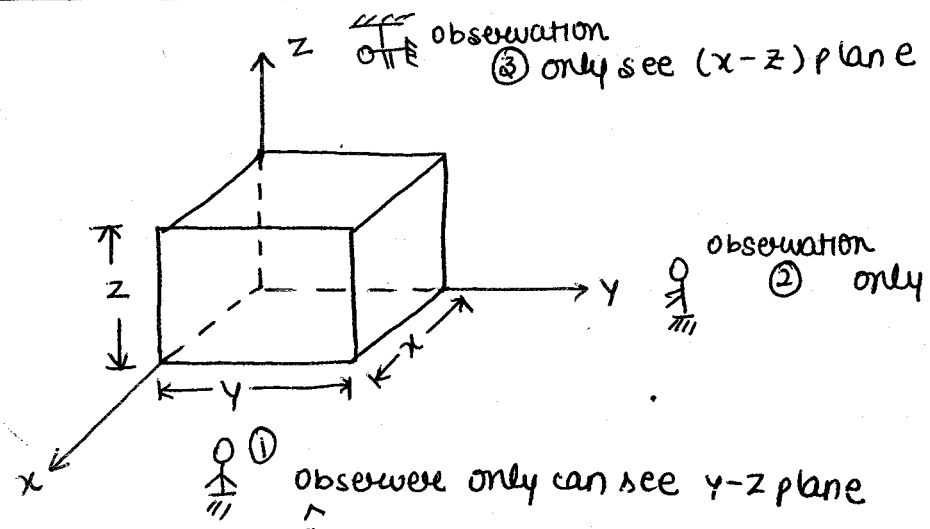Cartesian co-ordinate system :- (x, y, z)




x :- Perpendicular distance from yz plane
 Range : $(\infty, -\infty)$

Y :-

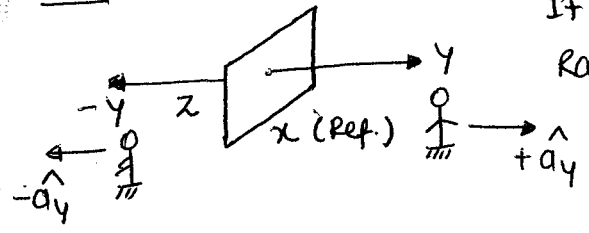

It is perpendicular distance from (x-z) plane
Range : $(-\infty, \infty)$


Z :-

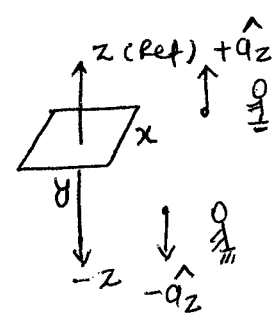

It is perpendicular distance from (x-y) plane.
Range : $(-\infty, \infty)$

concept of differential length, Area and volume :-

Graphical approach :-

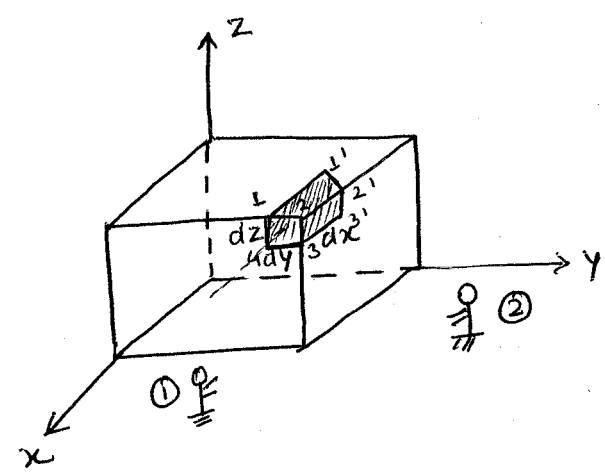


Differential length dl :-

- Differential length along x-axis = $dx \hat{a}_x$
- Differential length along y-axis = $dy \hat{a}_y$
- Differential length along z-axis = $dz \hat{a}_z$

$$\therefore \boxed{d\vec{l} = dx \hat{a}_x + dy \hat{a}_y + dz \hat{a}_z}$$


Differential surface area ds :-

observer ①

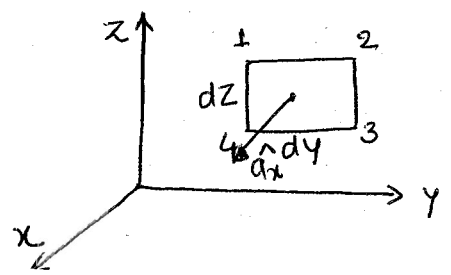


$$\boxed{d\vec{s} = dy dz \hat{a}_z}$$

observer ②

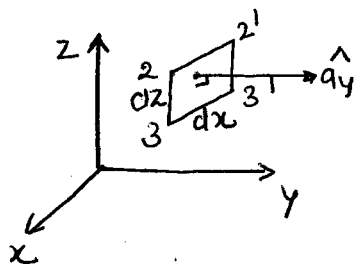

$$\vec{ds} = dx \cdot dz \cdot \hat{a}_y$$

observer ③

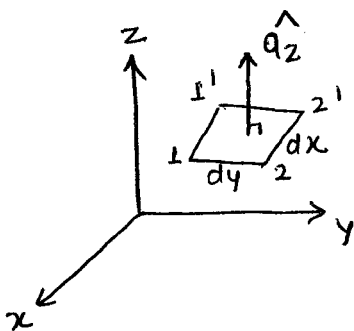

$$\vec{ds} = dx dy \hat{a}_z$$

where area vectors are $\hat{a}_x, \hat{a}_y, \hat{a}_z$ which is always away from the surface.

NOTE:- The direction of area vector is always taken normal to the surface and away from the surface.

Differential volume, dv (scalar quantity):-

$$dv = dx dy dz$$

Analytical approach:-

$$dl = dx \hat{a}_x + dy \hat{a}_y + dz \hat{a}_z$$

$$= 1 \times dx \hat{a}_x + 1 \times dy \hat{a}_y + 1 \times dz \hat{a}_z$$

$$= h_1 \times du \hat{a}_u + h_2 \times dv \hat{a}_v + h_3 \times dw \hat{a}_w$$

$u, v, w = \text{parameter}$

$h_1, h_2, h_3 = \text{scaling factor}$

Hence,

Imp i-co-system :-	\hat{a}_u	\hat{a}_v	\hat{a}_w	du	dv	dw	h_1	h_2	h_3
	\hat{a}_x	\hat{a}_y	\hat{a}_z	dx	dy	dz	1	1	1

$$dl = dx \hat{a}_x + dy \hat{a}_y + dz \hat{a}_z$$

$$ds = 1 \times 1 \times dy dz \hat{a}_x$$


[Find area in direction of \hat{a}_x]

Then freeze the \hat{a}_x & dx & 1]

$$dS = \perp \times \perp dx dy \hat{a}_z \quad [\text{find area in direction of } \hat{a}_z]$$

$$dV = \perp \times \perp \times \perp dx dy dz = dx dy dz$$

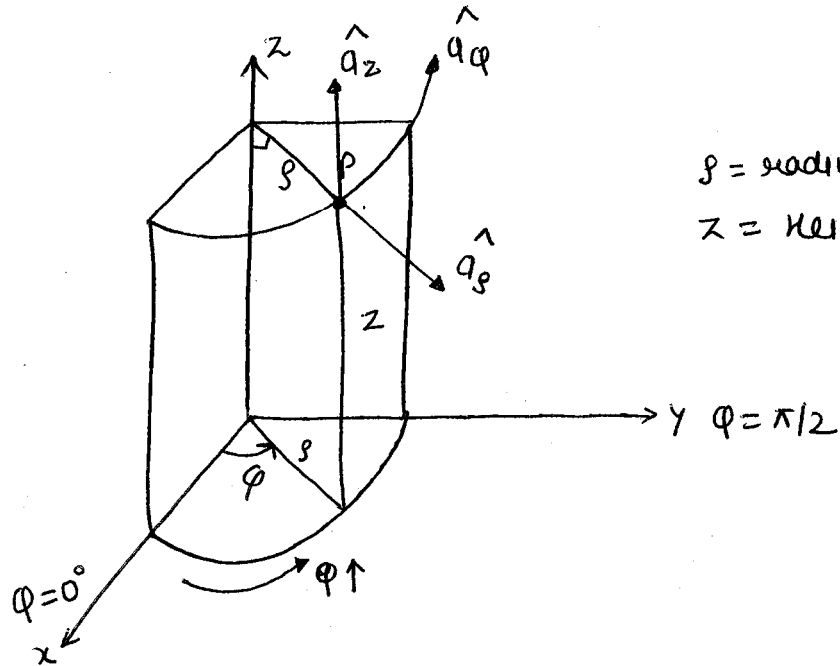cylindrical co-ordinate system $\{s, \phi, z\}$:-



s = radius of cylinder

z = height

$$\vec{A}_p = A_u \hat{a}_u + A_v \hat{a}_v + A_w \hat{a}_w \quad ; \quad u, v, w = \text{parameters}$$

$$\vec{A}_p = A_s \hat{a}_s + A_\phi \hat{a}_\phi + A_z \hat{a}_z$$

→ s : It is the perpendicular distance from reference axis $\{z\text{-axis}\}$
Range of s : $[0, \infty)$


→ ϕ : orientation angle of point about $z\text{-axis}$ and is always measured with respect to $x\text{-axis}$ i.e; @ $x\text{-axis}$, $\phi = 0^\circ$ [Also known as azimuthal angle]
Range of ϕ : $[0, 2\pi]$

→ z : It is Height of point along $z\text{-axis}$.
Range of z : $(-\infty, \infty)$

Relation between Cartesian coordinate system and cylindrical co-ordinate system :-

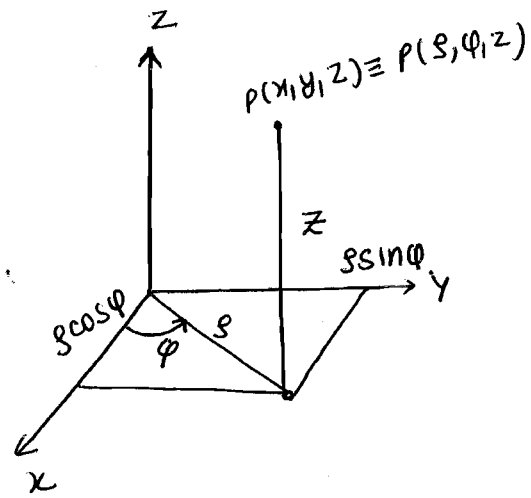(i) In terms of parameters :-

$$\begin{cases} x = \rho \cos \varphi \\ y = \rho \sin \varphi \\ z = z \end{cases}$$



Now;

$$x^2 + y^2 = \rho^2 \cos^2 \varphi + \rho^2 \sin^2 \varphi = \rho^2$$



$$x^2 + y^2 = \rho^2$$

$$\rho = \sqrt{x^2 + y^2}$$

Also; $\frac{y}{x} = \frac{\rho \sin \varphi}{\rho \cos \varphi} = \tan \varphi \Rightarrow \varphi = \tan^{-1}(y/x)$

And; $z = z$

(ii) In terms of unit vectors :-

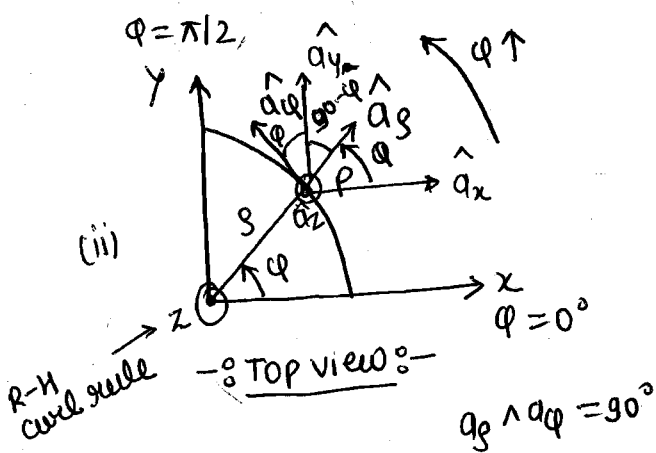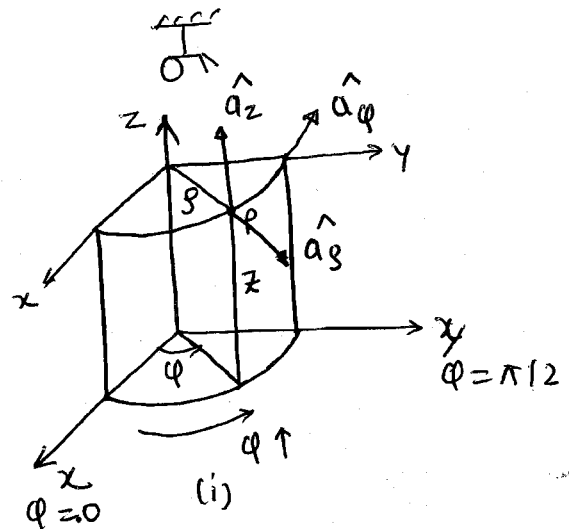

$$\hat{a}_\rho \cdot \hat{a}_x = \cos \varphi$$

$$\hat{a}_\rho \cdot \hat{a}_y = \cos(90 - \varphi) = \sin \varphi$$

$$\hat{a}_\rho \cdot \hat{a}_z = 0$$

$$\hat{a}_\varphi \cdot \hat{a}_x = \cos(90 + \varphi) = -\sin \varphi$$


$$\hat{a}_\varphi \cdot \hat{a}_y = \cos \varphi$$

$$\hat{a}_\varphi \cdot \hat{a}_z = \cos 90^\circ = 0$$

$$\hat{a}_z \cdot \hat{a}_x = \cos 90^\circ = 0$$

$$\hat{a}_z \cdot \hat{a}_y = \cos 90^\circ = 0$$
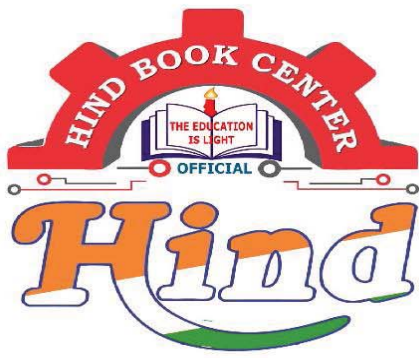
$$\hat{a}_z \cdot \hat{a}_z = \cos 0^\circ = 1$$



Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
03.DIGITAL ELECTRONICS
BY- RAMESH SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

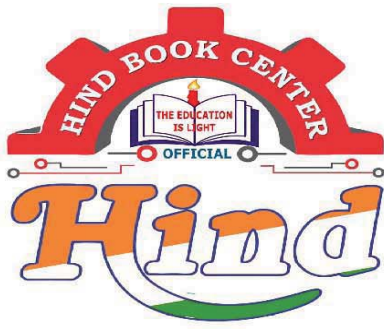Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Introduction

Boolean Logical Ideas -

These are categorized into 3 ways -

- 1) Producing the constants $\rightarrow (0, 1)$ (Null, Identity)
- 2) Unary operations (transfer, complimentary)
 - \downarrow Buffer
 - \downarrow NOT
- 3) Binary operations (AND, OR, NAND, NOR, XOR, EXNOR, Inhibition, Implication)

Note:

For n input variables we get 2^n combinations and 2^{2^n} (2^{2^n}) possible functions.

Truth table -

x	y	f ₀	f ₁	f ₂	f ₃	f ₄	f ₅	f ₆	f ₇	f ₈	f ₉	f ₁₀	f ₁₁	f ₁₂	f ₁₃	f ₁₄
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0

$\rightarrow f_0 = 0$ Null

$\rightarrow f_1 = x \cdot y$ AND

$x \wedge y$

$\rightarrow f_2 = x \cdot \bar{y}$ Inhibition

x / y [x but not y]

$\rightarrow f_3 = x$ transfer [Buffer]

$\rightarrow f_4 = \bar{x} \cdot y$ Inhibition

y / x [y but not x]


$\rightarrow f_5 = y$ Buffer

$\rightarrow f_6 = x \oplus y$ EX-OR

$= \bar{x}y + x\bar{y}$

S ₂ ⊕ S ₁	S ₁	S ₀	S ₂ S ₁ S ₀
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0

Note: For the staircase an escalator & Ex-OR Logic is used.



$\rightarrow f_7 = x + y$ OR

$x \vee y$

$\rightarrow f_8 = \overline{x + y}$ NOR

$\bar{x} \downarrow \bar{y}$

$$\rightarrow f_9 = x \oplus y \quad \boxed{\text{Ex-NOR}}$$

$$= \bar{x}y + x\bar{y}$$

$$\rightarrow f_{14} = \overline{x \cdot y} \quad \boxed{\text{NAND}}$$

$$= \bar{x} + \bar{y}$$

Note - Ex-NOR is also known as coincidence logic gates or equivalence logic gate.

$$\rightarrow f_{15} = 1 \quad \boxed{\text{Identity}}$$

$$\rightarrow f_{10} = \bar{y} \quad \boxed{\text{NOT}}$$

$$\rightarrow f_{11} = x + \bar{y} \quad \boxed{\text{Implication}}$$


$$\rightarrow f_{12} = \bar{x} \quad \boxed{\text{NOT}}$$

$$\rightarrow f_{13} = \bar{x} + y \quad \boxed{\text{Implication}}$$

Logic Gate Symbols




Buffer

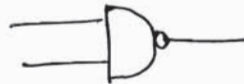

NAND



NOT

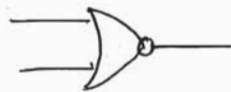

NOR




AND



EX-OR




OR

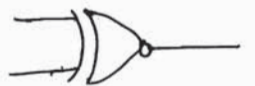

EX-NOR.

→ Basic logic gates - NOT, AND, OR

Universal logic gates - NAND, NOR

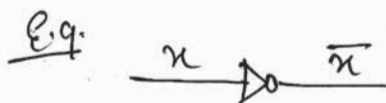

$$= \overline{x \cdot x}$$

$$= \bar{x} + \bar{x}$$

$$= \bar{x}$$

Trick / short-cut.

	NAND	NOR
NOT	1	1
AND	2	3
OR	3	2
EX-OR	4	5
EX-NOR	5	4

Duality

Step-1 Interchange the operator $\rightarrow (\cdot, +)$


Step-2 Interchange the identity $\rightarrow (0, 1)$

AND	OR
$x \cdot x = x$	$x + x = x$
$x \cdot 0 = 0$	$x + 0 = x$
$x \cdot 1 = x$	$x + \bar{x} = 1$
$x \cdot \bar{x} = 0$	$x + 1 = 1$

E.g. i) $x \cdot 0 = 0$
 $x + 1 = 1$

ii) $F = A'B + C$
 $F^D = ?$



$F^D = (A+B) \cdot C$

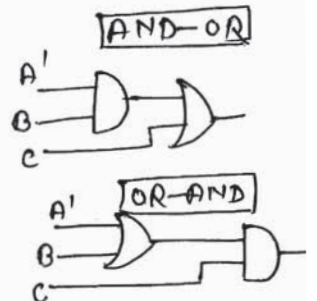


Degenerative forms

When a two level logic gate system o/p is expressed with a single logic gate then the two level logic gate system is known as degenerated form for the single logic gate.

E.g.

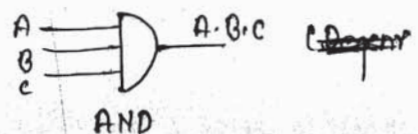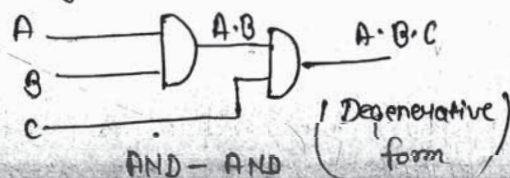


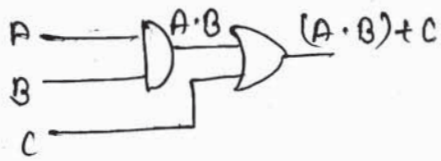

Non-degenerative form.

* Shortcut


AND - OR	OR - AND
NAND - NAND	NOR - NOR
NOR - OR	NAND - AND
OR - NAND	AND - NOR

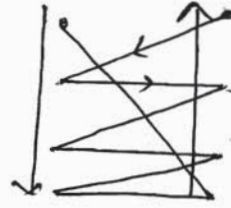

These are non-degenerative forms.

→ In the above representation, combinations present in the same horizontal line are dual forms.

Alternative logic gate setting

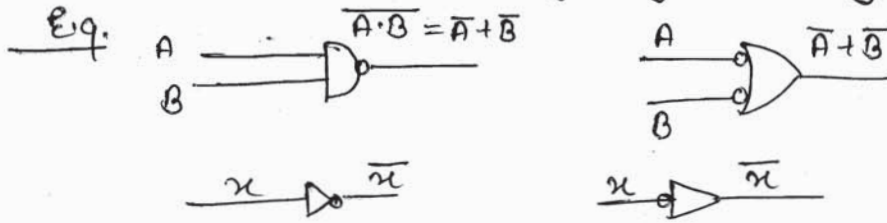

* Shortcut

NAND	bubbled →	OR
NOR	→	AND
AND	→	NOR
OR	→	NAND

Complimenting a boolean expression.

1 - Dual form

2 - Complimenting the individual variable.


E.g. $f = \bar{A} \cdot B + C$

$\bar{f} = ?$

1) $(\bar{A} + B) \cdot C$

2) $(A + \bar{B}) \cdot \bar{C} = \bar{f}$

$\bar{\bar{f}} = f$

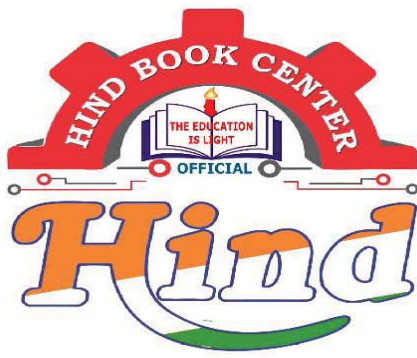

Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
04.CONTROL SYSTEM
BY- HANEEF SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

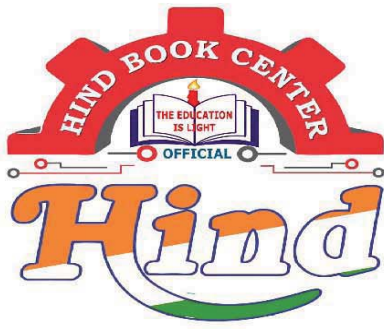Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

System :- The means of transforming a signal.


Signal is a form of energy that contains information of some phenomenon. Mathematically, signal can be defined as one or more number of independent variables.

Ex-: speech = $f(t)$

Room temperature = $f(x, y, h, t)$

Image = $f(x, y)$

video = $f(x, y, t)$

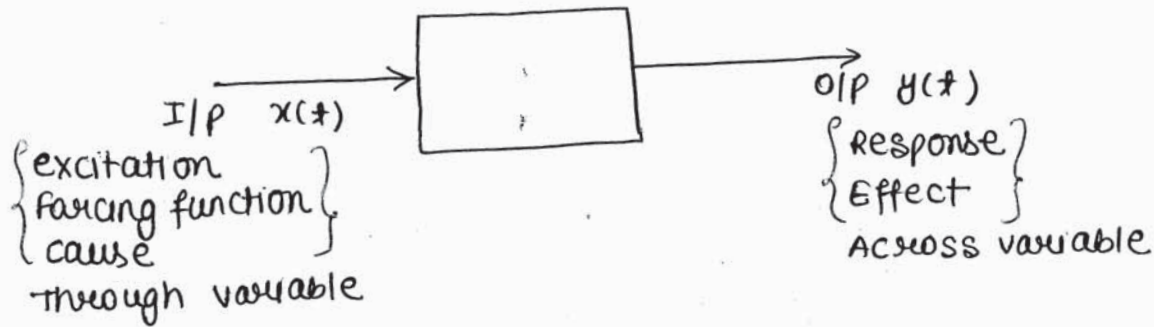

$$y(t) = T[x(t)]$$

Control system :- Control system is that means by which any quantity of interest is maintained or altered according to a desired manner.


Ex-: system : J/K F/F

Master slave F/F : control system

To make control system we need basically two element -

(i) controller

(ii) plant or process

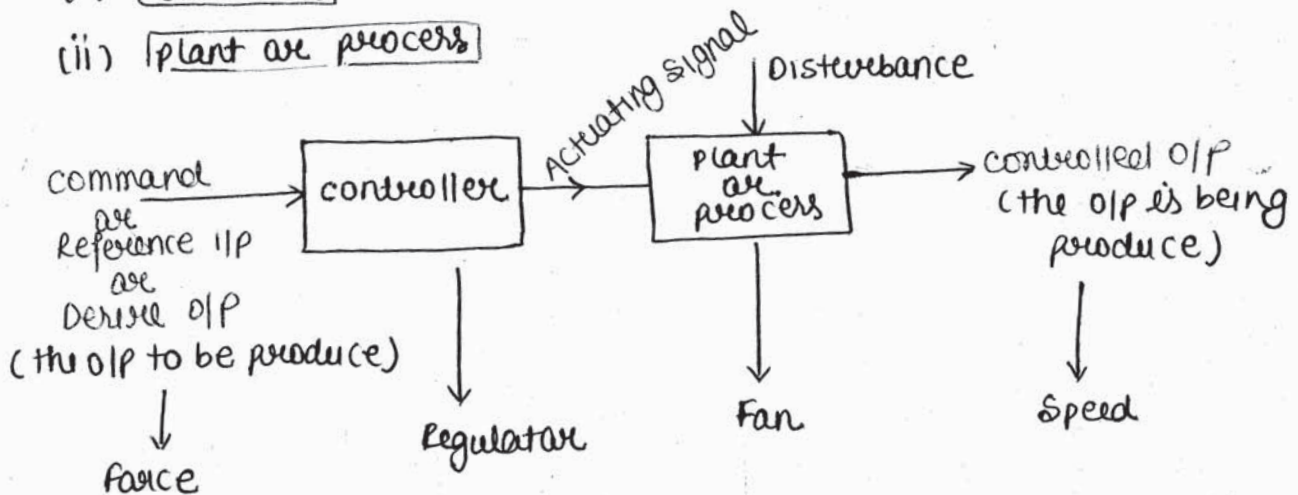

SISO :-

MISO :-


MIMO :- Automobile

SIMO :-

The objective of any control system is to ensure that controlled output become same as desired o/p. This state of the system is called steady state.

without disturbance, control system is Ideal. but in practical system, there will be disturbance along with it.

practical control system :-

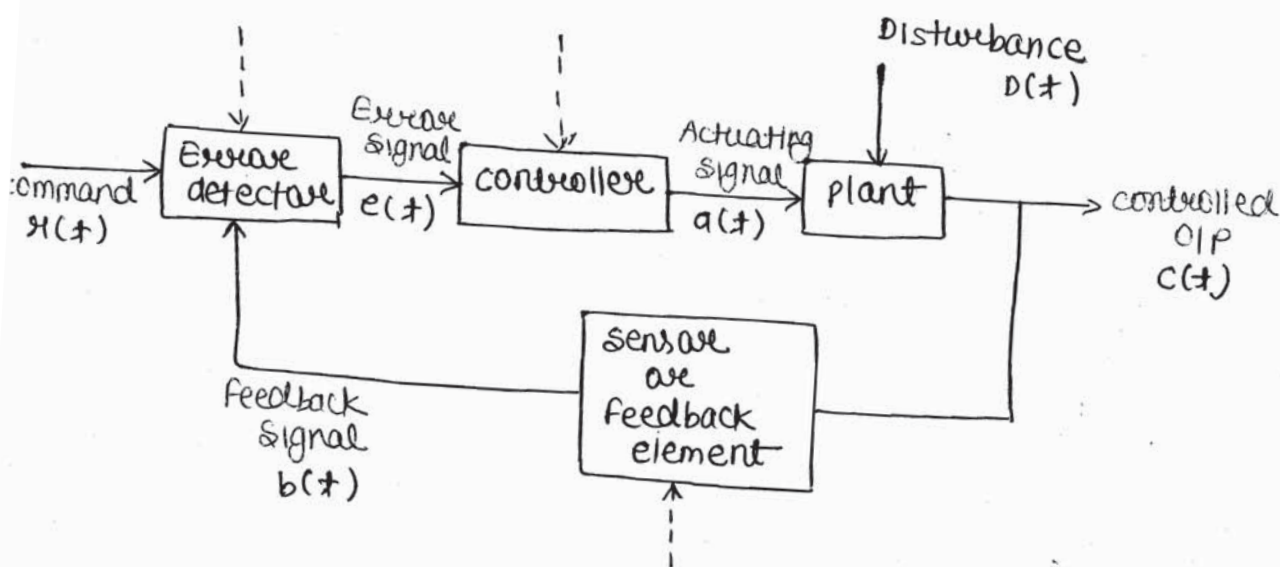

$$C(t) = C_x(t) + C_D(t) \quad [\text{Linear combination because } x(t) \text{ \& } D(t)]$$

both are independent to each other]

$$\text{Disturbation} = \text{Distraction} + \text{Noise}$$


↓ Internal disturbance ↓ External disturbance

Above system can overcome, the effect of disturbance associated only with the plant whereas the other disturbances still continues. Hence a system can attain steady state but not with 100% output within finite time.

+10 = 10∠0° → +ve feedback i.e; in phase

-10∠ = 10∠180° → -ve feedback i.e; out of phase

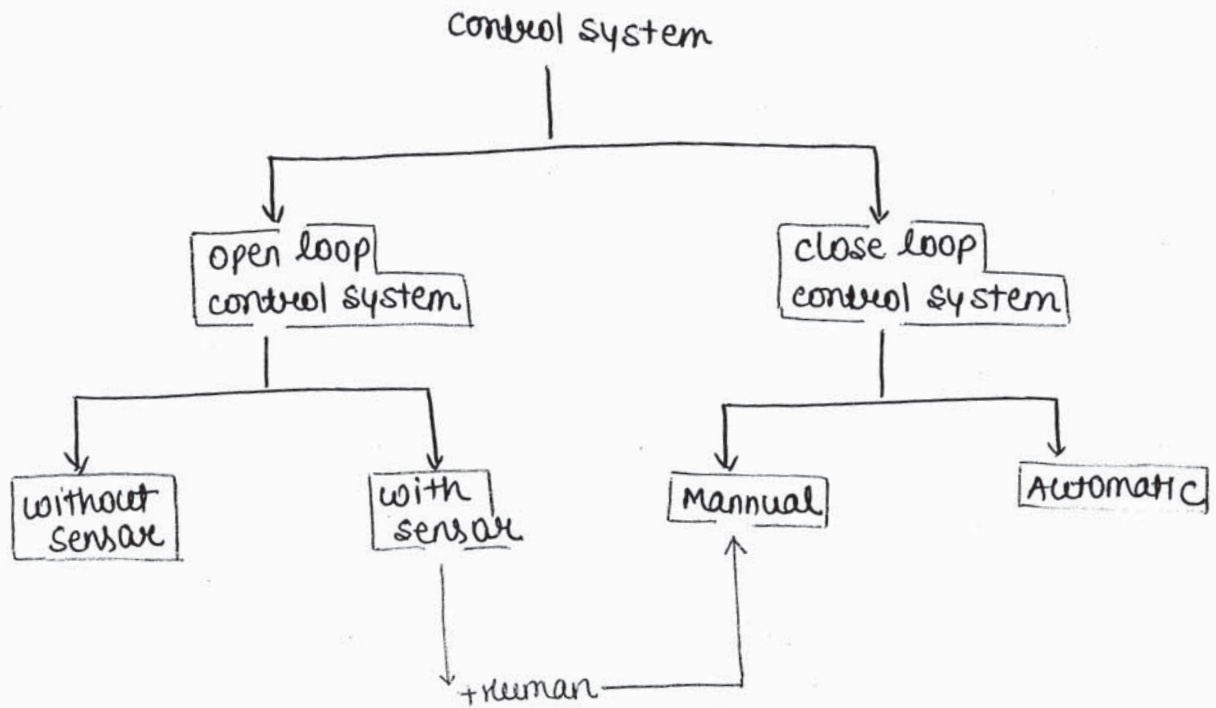control system is classified into two categories -



Differences between open loop and close loop system :-

open loop control system	close loop control system
(i) The behaviour of OLCs does not change, though its output changes. Hence <u>OLCS</u> is <u>not accurate</u> .	(i) The behaviour of close loop system if its output changes. Hence <u>CLCS</u> is <u>accurate</u> .
(ii) open loop system <u>may or may not</u> have <u>sensor</u> but it does <u>not</u> have <u>complete sense</u> .	(ii) close loop system has <u>complete sense</u> either <u>manually</u> or <u>Automatically</u> .
(iii) Time constant of open loop system is larger, due to which transients take large time to die out. Hence <u>open loop system</u> is <u>slow</u> .	(iii) Time constant of close loop system is smaller, due to which transients die out rapidly. Hence <u>close loop system</u> is <u>faster</u> .
(iv) Effect of external disturbance and internal parameter variation is more in OLCs i.e; <u>OLCS</u> is <u>more sensitive</u> .	(iv) Effect of external disturbance and internal parameter variation is less in close loop system. i.e; <u>close loop system</u> is <u>less sensitive</u> .
(v) The OLCs is generally stable but can be stabilize when it becoming unstable.	(v) close loop system <u>can become unstable</u> but <u>can be stabilized</u> .
(vi) OLCs is <u>simple</u> & <u>economical</u>	(vi) CLCS is <u>complex</u> & <u>expensive</u> .

NOTE: (i) The transient in system are due to stored energy / change in i/p / change in load condition.

(ii) sequence of step to stabilize a system -

step 1 :- Apply feedback, preferably negative feedback.

step 2 :- Adjust system parameters preferably open loop gain.

step 3 :- Insert a controller / compensator preferably P+D controller / lead compensator.

ste

(iii) A system can be stable or unstable or marginally stable with any feedback, but a system is always more stable with a negative feedback compared to positive feedback.

(iv) In spite of having negative feedback, control system can still become unstable due to high open loop gain / high type number / high sensitivity / High transportation delay or lag phase.

By default we have to consider — will be close loop control system.

parameter	180°	0°
	-ve F.B.	+ve F.B.
Gain	↓	↑
Bandwidth	↑	↓
Time constant	↓	↑
Speed	↑	↓
sensitivity	↓	↑
stability	↑	↓


Gain × Bandwidth = constant Time constant × speed = constant

sensitivity × stability = constant

- (i) study the system design } mathematically
- (ii) Redesign

standard model :-

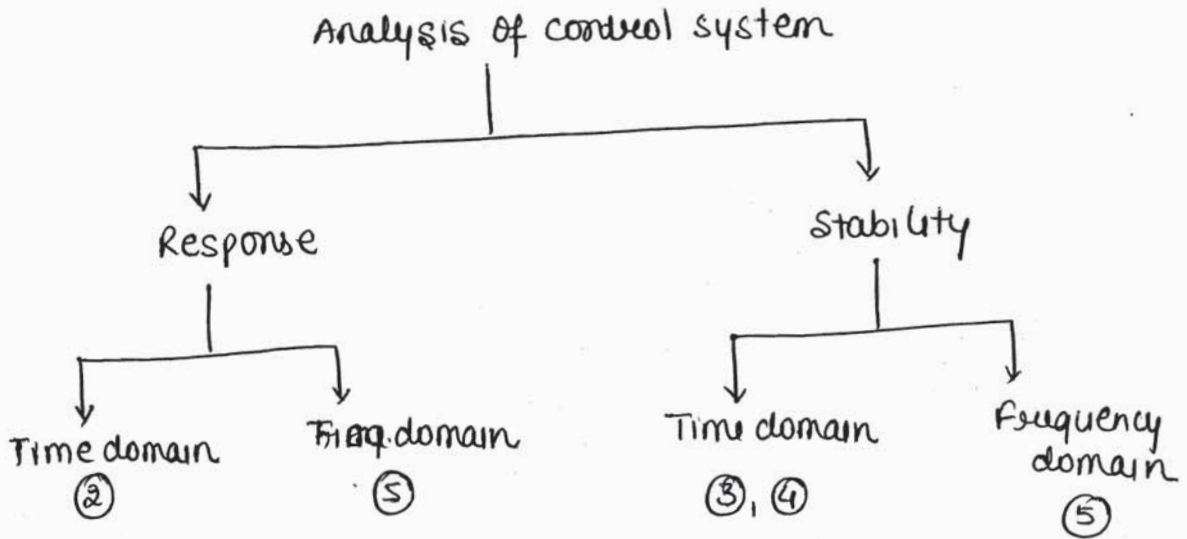- (i) TIF model (only for LTI)
- (ii) state model (Any system)



Redesign — (6)

state model — (7)

	T.D.	F.D.
C.T. System	L.T.	F.T.
D.T. System	Z.T.	D.T.F.T.

L.T. :- Laplace transform

F.T. :- Fourier transform

Z.T. :- Z-transform

DTFT : Discrete time Fourier transform.

$$T.F. = \frac{L[OIP]}{L[IIP]}$$

initial condition = 0

$$\text{Total response} = ZIR + ZSR$$

due to initial
condition/state

due to
i/p

ZIR - zero i/p response
i.e., i/p = 0

ZSR - zero state
response

$$y = c + mx$$

due to i/p because
x is a part of it.

NOTE:- ZIR is consider then analysis will be done in state model only.

zero state response

Transient or Dynamic
Response

steady state or static
Response

$$T.F. = \frac{L[OIP]}{L[IIP]} = \frac{L[IR]}{L[S(t)]} = \frac{L[SR]}{L[U(t)]} = \frac{L[RR]}{L[\int U(t)]} = \frac{L[PR]}{L[\frac{t^2}{2} U(t)]}$$

$$T.F. = L[IR] = sL[SR] = s^2L[RR] = s^3L[PR]$$

Q.N:- SR = $1 - 10e^{-t}$ then T.F. = ?

Solution:- T.F. = $sL[SR]$

$$= s \left[\frac{1}{s} - \frac{10}{s+1} \right] = s \left[\frac{s+1-10}{s(s+1)} \right] = \frac{1-9s}{s+1}$$

$$SR = (1 - 10e^{-t})u(t)$$

$$\frac{d}{dt}(SR) = IR$$

$$\text{NOW } IR = \delta(t) - 10[e^{-t}\delta(t) + u(t)e^{-t}(-1)]$$

$$= \delta(t) - 10\delta(t) + 10e^{-t}u(t)$$

$$= -9\delta(t) + 10e^{-t}u(t)$$

$$\text{T.F.} = L[IR]$$

$$= -9(1) + \frac{10}{s+1} = \frac{1-9s}{s+1} \quad \text{i.e., Transfer function is unique function}$$



$$SR = (1 - 10e^{-t})u(t)$$

$$RR = \int_0^t (SR) dt = \int_0^t (1 - 10e^{-t})u(t) dt =$$


$$SR \Big|_{t=0} = (1 - 10e^{-t}) \Big|_{@ t=0} = -9 \neq 0 \quad \text{i.e., it contains initial condition due to which it is not relaxed}$$

if initial condition is zero then L [Impulse response] = T.F.

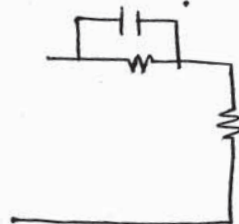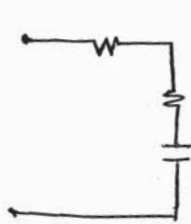Transfer function of a system is unique i.e., one system can not have two transfer function but two or more number of different system may have the same transfer function. because transfer function depends on the component but not their configuration.




$$\frac{s+a}{s+b}$$

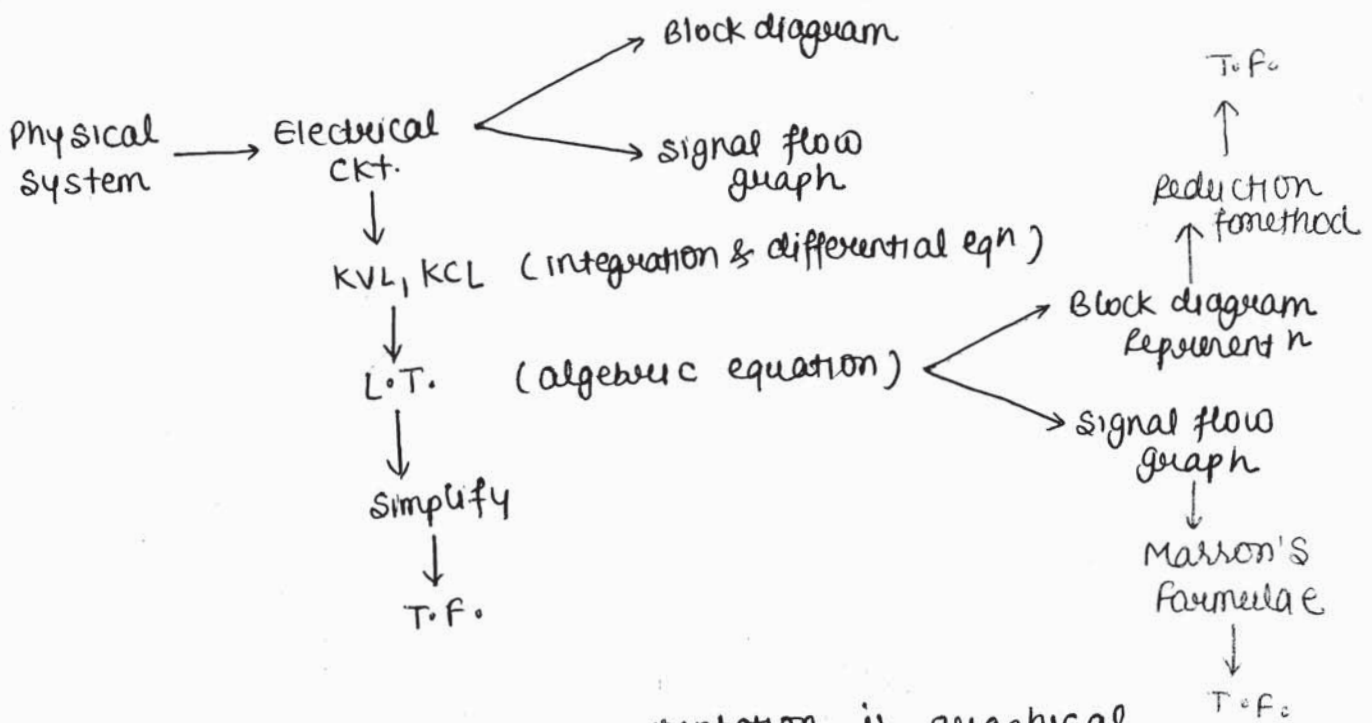

BDR, SFG: BDR or SFG representation is graphical representation of mathematical relation between the variables of a system described in the form of set of linear algebraic equation in cause effect form.

Linear: $y = mx \rightarrow$ BDR / SFG \rightarrow T.F.

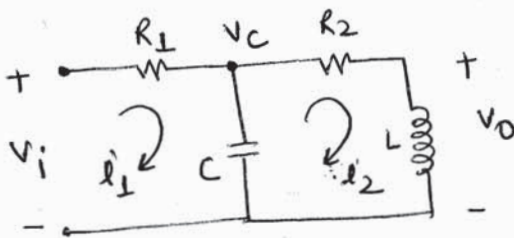Non linear: $y = mx + c \rightarrow$ state diagram \rightarrow state model



$$q = CV$$

$$i = C \frac{dV}{dt}$$

$$-V_i + i_1 R_1 + \int (i_1 - i_2) \cdot dt \cdot \frac{1}{C} = 0$$


$$-V_C + R_2 i_2 + V_o = 0$$

not in cause effect form \Leftarrow ~~$V_i = i_1 R_1 + \frac{1}{C} \int (i_1 - i_2) dt$~~

$$V_o = (sL) i_2$$

$$\frac{V_i}{s} = R_1 \frac{i_1(s)}{s} + \frac{1}{Cs} (i_1 - i_2)$$
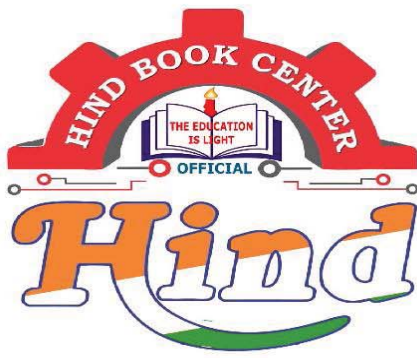
$$\frac{V_i}{s} = \frac{R_1 i_1}{s} + \frac{i_1}{Cs} - \frac{i_2}{Cs}$$



Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
05.SIGNAL & SYSTEM
BY- ROHIT TRIPATHI SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

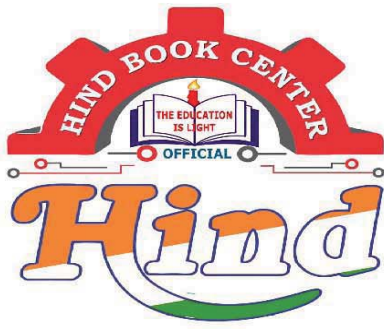Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Chapters :-

1. signals definition and its classification

- Even/Odd
- Periodic / Non-periodic
- conjugate symmetric & conjugate anti symmetric
- Half wave symmetry
- Energy and power signal

2. Different operations in signal

- shifting
- scaling
- Reversal
- Differentiation
- Integration
- convolution

3. Basic system properties

- static / dynamic system
- Linear / non-linear
- causal / Non-causal
- Stable / unstable
- Time invariant / Time variant
- Invertible / Non-invertible

4. Fourier Series (continuous time)

5. Fourier Transform (continuous time)

6. Laplace Transform

7. Sampling Theorem

8. Discrete time signal & system

- Types of signals
- Basic signals
- Different operations on signal
- Types of systems


9. Z-Transform \longrightarrow GATE + IES
10. Discrete Fourier transform (DFT)
and
Fast Fourier transform (FFT)
11. Digital filters
- \rightarrow Infinite impulse response (IIR) filter
 - \rightarrow finite impulse response (FIR) filter
 - \rightarrow Impulse invariance method
 - \rightarrow Bilinear transformation method
12. Discrete cosine transform (DCT)
 \longrightarrow IES only.

www.hindphotostate.com
9311989030

II. Different operations on signal :-


(1) Time shifting :- $\left\{ \begin{array}{l} \rightarrow \text{Left shifting} \\ \rightarrow \text{Right shifting} \end{array} \right.$

$$x(t) \longrightarrow x(t+k)$$

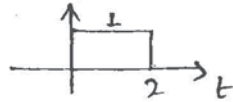


Case (i) :- when $k > 0$ (Left shifting) :-

Example $k=1$

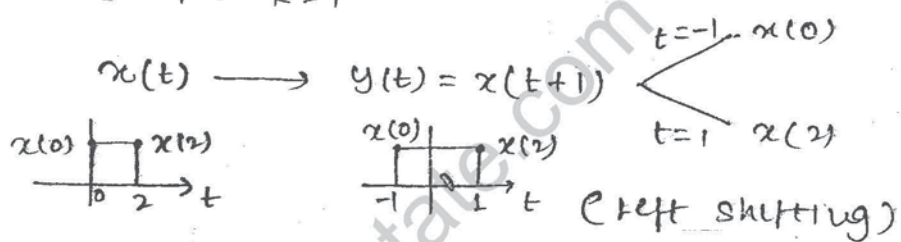

Case (ii) :- when $k < 0$ (Right shifting) :-


Example $k=-1$

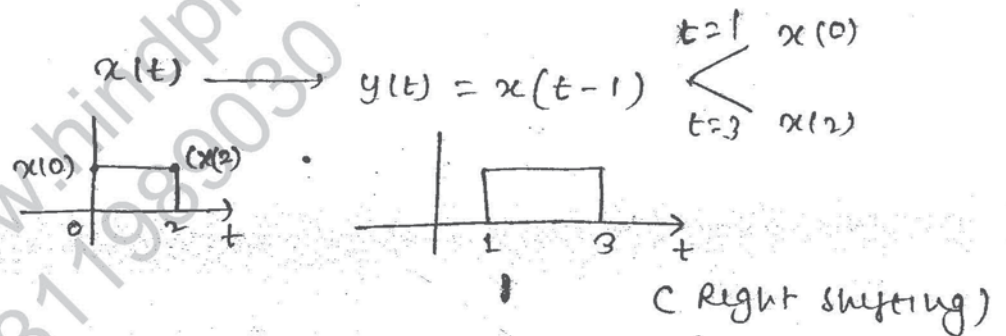

(2) Amplitude shifting :-

$\left\{ \begin{array}{l} \rightarrow \text{upward} \\ \rightarrow \text{downward} \end{array} \right.$

$$x(t) \longrightarrow y(t) = k + x(t)$$

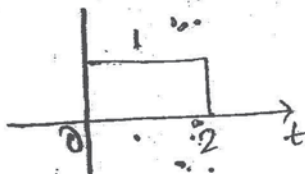

Case (i) when $k > 0$ (upward shifting)

Example $k = 1$



$$x(t) \rightarrow 1 + x(t)$$

$$x(t) = \begin{cases} 0 & ; t < 0 \\ 1 & ; 0 \leq t \leq 2 \\ 0 & ; t > 2 \end{cases}$$

$$y(t) = 1 + x(t) = \begin{cases} 1 + 0 & ; t < 0 \\ 1 + 1 & ; 1 \leq t \leq 2 \\ 1 + 0 & ; t > 2 \end{cases}$$

$$y(t) = \begin{cases} 1 & ; t < 0 \\ 2 & ; 1 \leq t \leq 2 \\ 1 & ; t > 2 \end{cases}$$

$$x(t) \rightarrow y(t) = 1 + x(t)$$

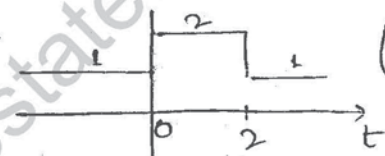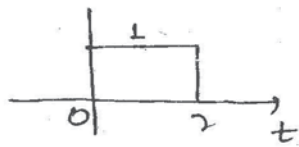

(upward shifting)

Case (ii) when $k < 0$ (downward shifting)

Example $k = -1$

$$x(t) \rightarrow y(t) = -1 + x(t)$$



$$x(t) = \begin{cases} 0 & ; t < 0 \\ 1 & ; 0 \leq t \leq 2 \\ 0 & ; t > 2 \end{cases}$$

$$y(t) = -1 + x(t)$$

$$y(t) = \begin{cases} -1 + 0 & ; t < 0 \\ -1 + 1 & ; 0 \leq t \leq 2 \\ -1 + 0 & ; t > 2 \end{cases}$$

$$y(t) = \begin{cases} -1 & ; t < 0 \\ 0 & ; 1 \leq t \leq 2 \\ -1 & ; t > 2 \end{cases}$$


$$x(t) \rightarrow y(t) = -1 + x(t)$$

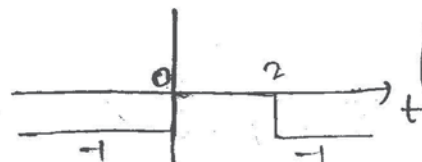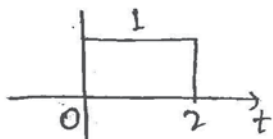

(downward shifting)

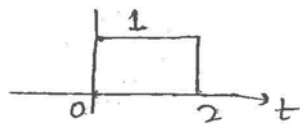
(3) Time - Scaling :-

$$x(t) \longrightarrow x(at), \quad a \neq 0.$$




Case (i) when $a > 1$:- (time compression)

Example $a=2$

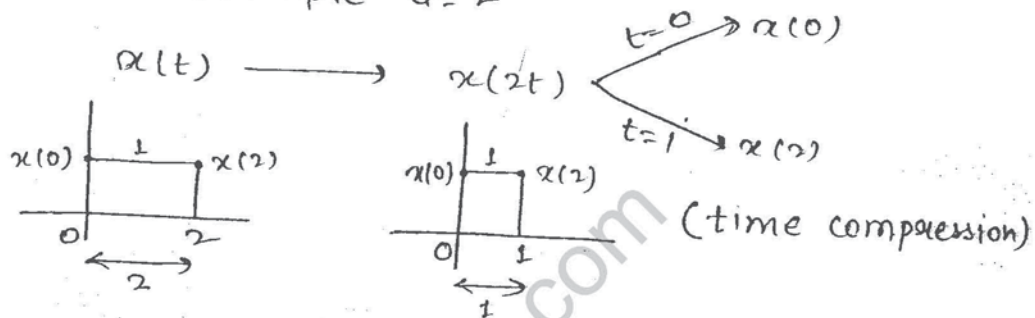


Case (ii) when $0 < a < 1$:- (time expansion)


Example $a=0.5$

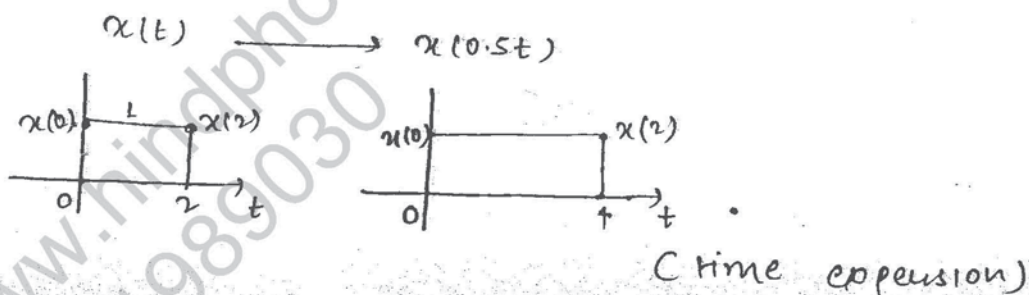


General Rule for Time Scaling :-

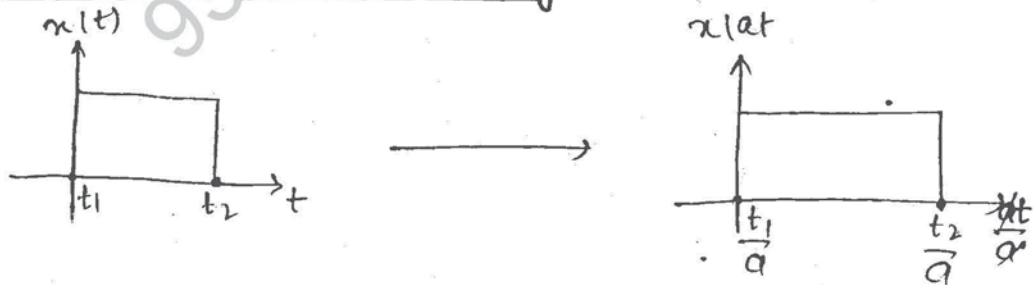

Example :-

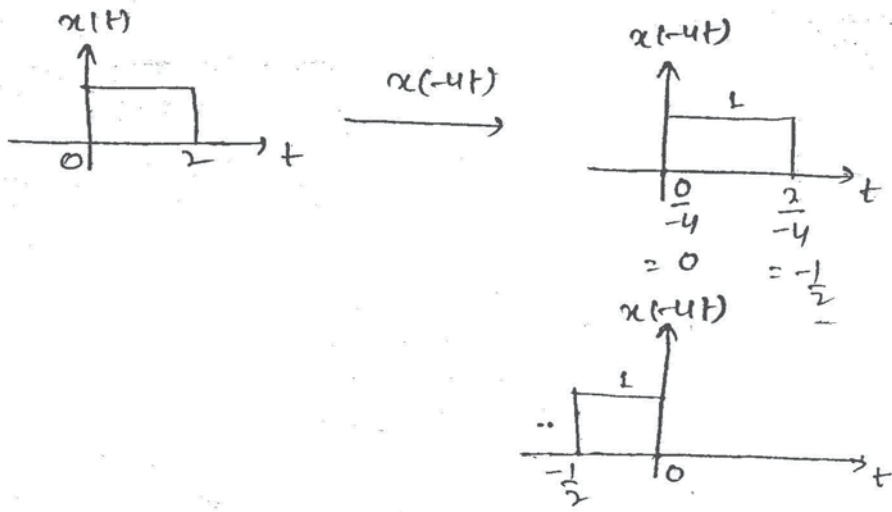


Example :

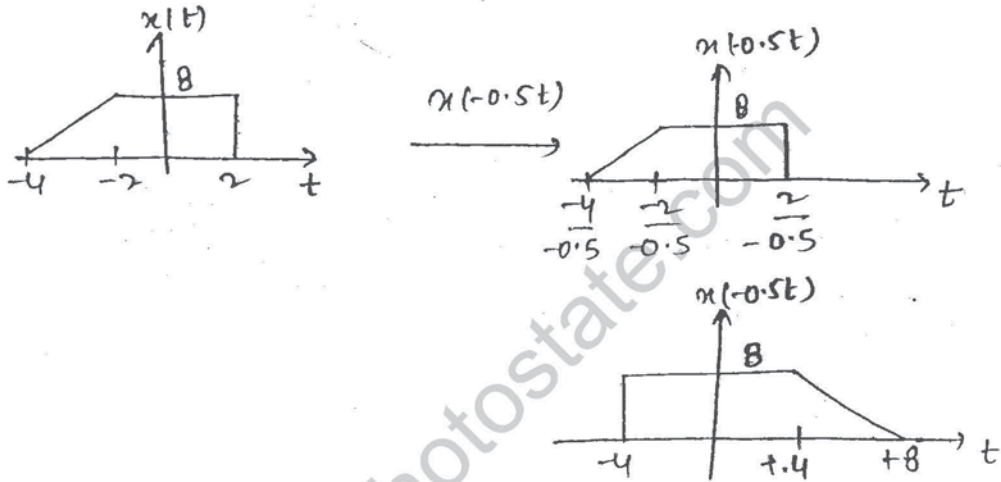


(+) Amplitude Reversal :-


(Folding about x axis)

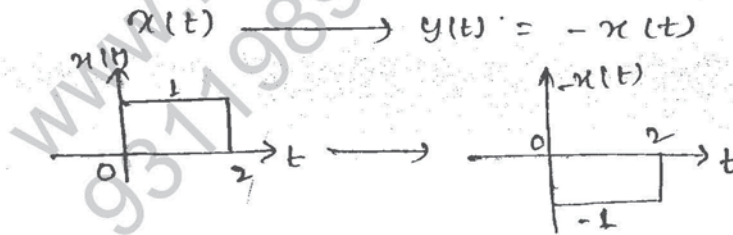


Example :-

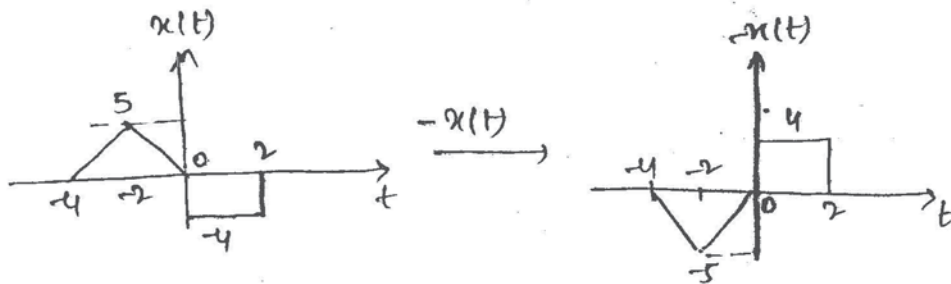

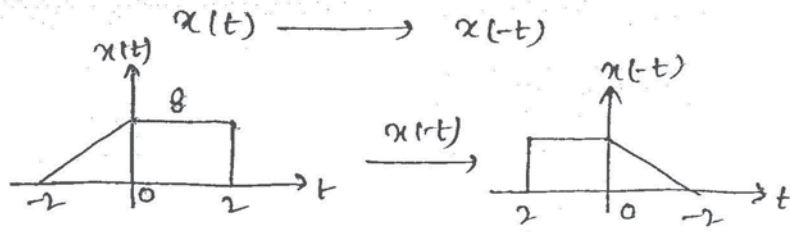(5) Time-Reversal :- (P.ding about y-axis)




Example :-

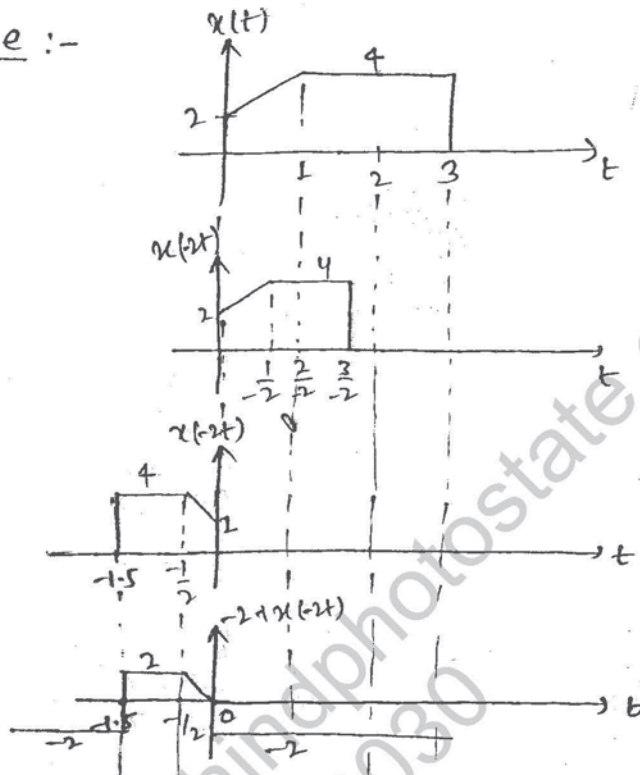


Find $y(t) = ?$

where $y(t) = -2 + x(-2)$


Example :-

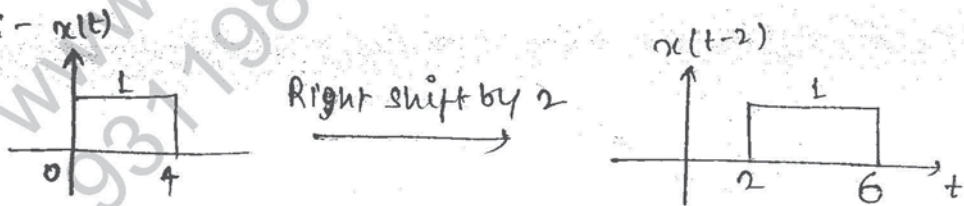


Example :

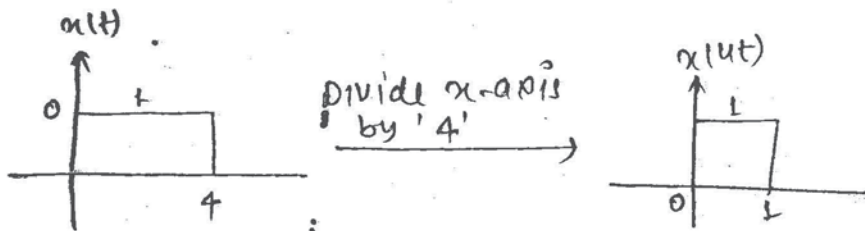


Example :-

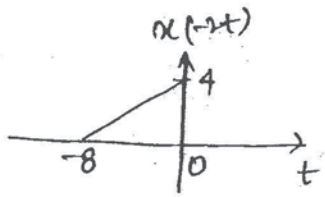


$t \rightarrow t+2$
left shift
by 2

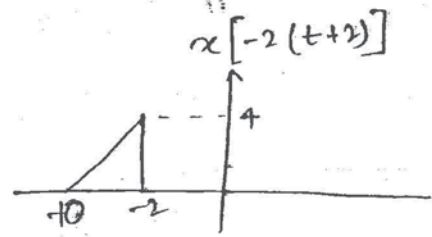


Example :-

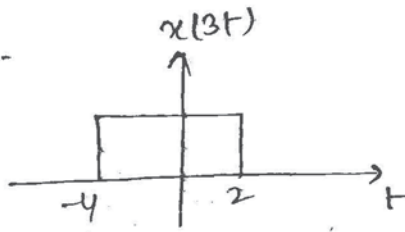

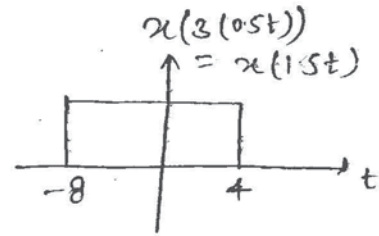
$t \rightarrow 0.5t$
divide x-axis
by 0.5




Example :-

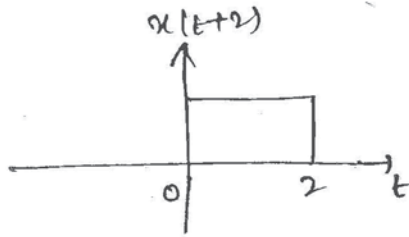


$t \rightarrow 2t$
divide x-axis
by 2

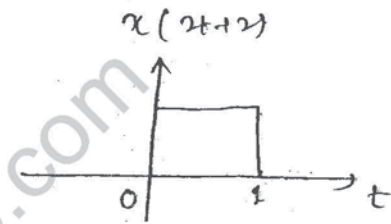


Example :-

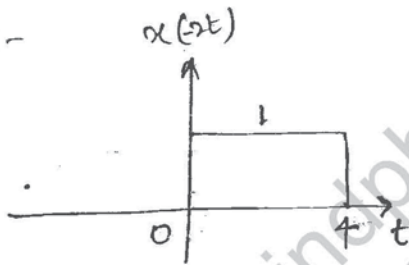

$t \rightarrow t+3$
left shift by 3

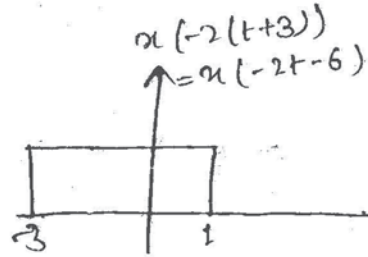

*** Question :-

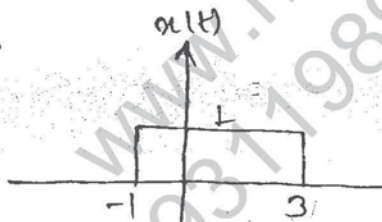

Draw signal $y(t)$

$$y(t) = x(2t+3)$$

$$= x(2(t+1.5))$$

Solution :-



method (1)


time scaling
 $x(t) \rightarrow x(2t)$

L.S = 1.5

अर्थात् 3 से 1.5 की
कमरेगी।

$$x(2t+3) \text{ or } x(2(t+1.5))$$

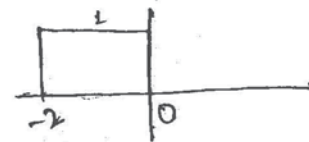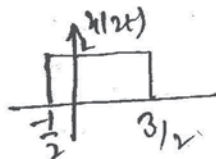

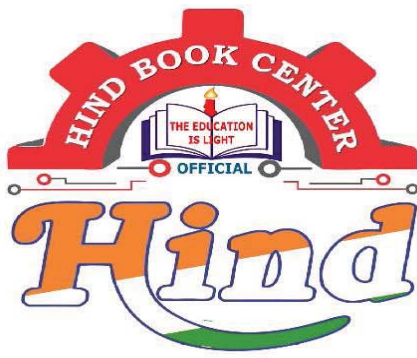

Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
06.ANALOG ELECTRONICS
BY- A.RAJKUMAR SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

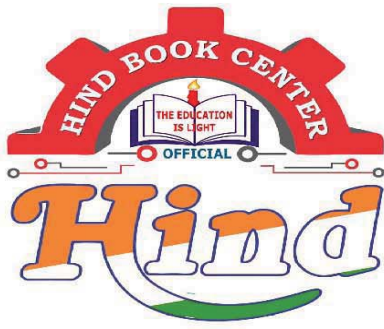Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--


Website: www.hindbookcenter.com

Contact Us: 9711475393

-: Analog Electronics :-

-: Chapter-1 Diode models :-

Ideal model :-

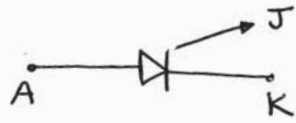

Indication:

A → Anode (+)

K → Cathode (-)

J → Junction

Arrow → unidirectional device

↓
[impedance are different]

conditions for ideal model of diode :-

$V_A - V_K > 0$ then $D = ON$  $V_D = 0, I_D > 0$

$V_A - V_K < 0$ then $D = OFF$  $V_D = V_B, I_D = 0$

$V_A - V_K = 0$ then D just ON  $V_D = 0, I_D = 0$

$V_B =$ Battery voltage

Testing method to check diode status :-

- Short circuit Test (SC Test) [Failure when KVL violates in the ckt]
- open circuit Test (OC Test) [Failure when KCL violates in the ckt]

Procedure to check diode status using SC Test :-

Rule 1:- Assume all the diodes to be S.C.



Rule 2:- Indicate the current direction of each diode from A to K.

Rule 3:- check & calculate I_D of each diode by using KVL or KCL

Status: $I_D > 0$; $D = ON$

$I_D < 0$; $D = OFF$

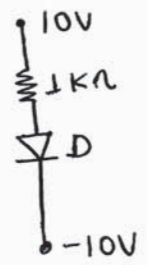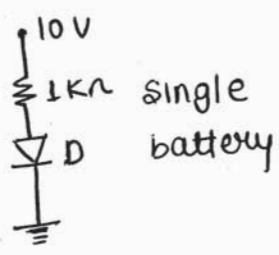Example 1: Check the status of diode D in the given ckt




dual battery

Solution:-



⇒

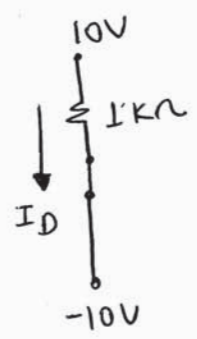


$$I_D = \frac{10 - (-10)}{1K}$$


$$= 20mA > 0$$

↳ D ON

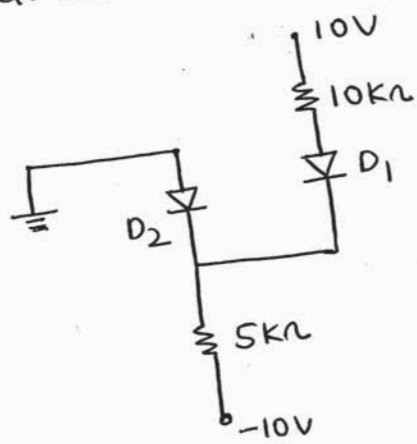Example 2: Check the status of D_1 & D_2 in the given ckt



Solution:-

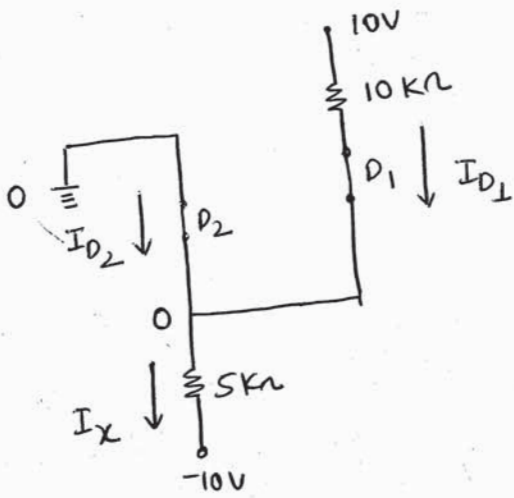

$$I_{D1} = \frac{10 - (0)}{10K} = 1mA > 0$$

↳ D_1 ON

$$I_x = \frac{0 - (-10)}{5K} = 2mA$$

KCL @ node 'a'


$$I_{D1} + I_{D2} = I_x$$

$$I_{D2} = 2mA - 1mA$$





$$I_{D2} = 1mA > 0$$

↳ D_2 ON

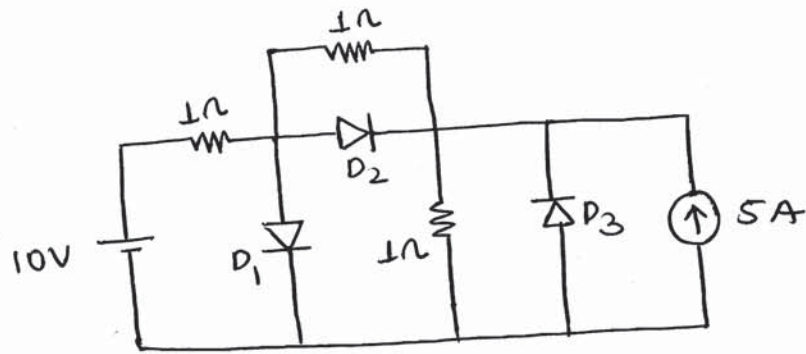Q.N:- what are the states of the three ideal diodes of the circuit



Solution:-

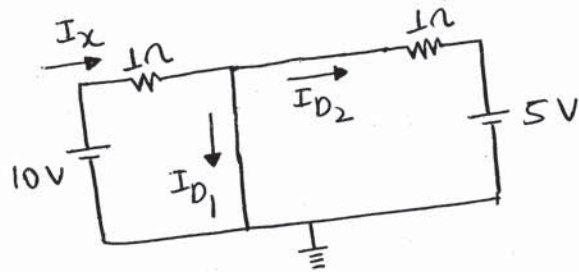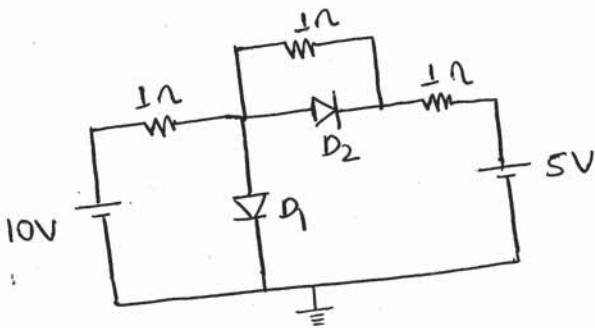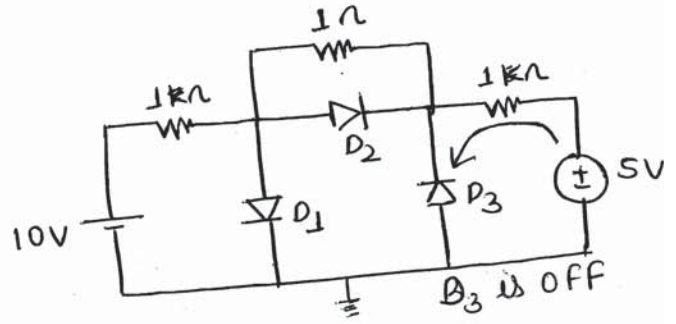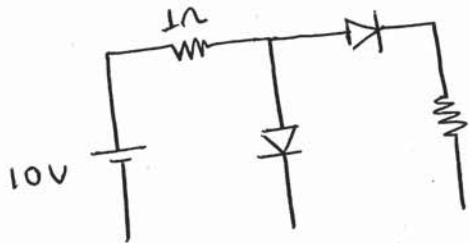


$$I_x = \frac{10-0}{1} = 10A \quad I_{D2} = \frac{0-5}{1} = -5A < 0 \rightarrow D_2 \text{ is OFF}$$

KCL at node a $I_x = I_{D1} + I_{D2}$

$$I_{D1} = 10 - (-5)$$

$$I_{D1} = 15A > 0 \rightarrow D_1 \text{ is ON}$$

Conclusion:-

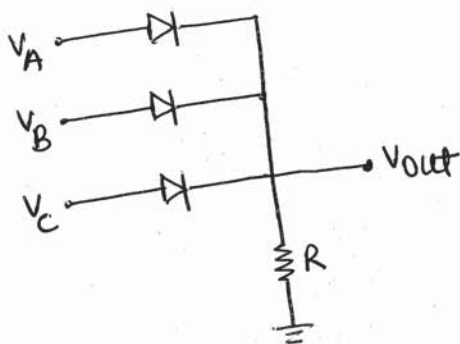

$$V_A = 5V, V_B = 3V, V_C = 1V$$

Failure of KVL in the short circuit test.
It violates KVL

$$V_{out} = 5V$$

Procedure to check diode status using open circuit test :-



Rule 1: Assume all the diodes to be OFF

Rule 2: Indicate V_A & V_K of each diodes

Rule 3: Calculate $V_A - V_K$ difference of each diodes

Status: $V_A - V_K > 0 \quad D = ON$

$V_A - V_K < 0 \quad D = OFF$

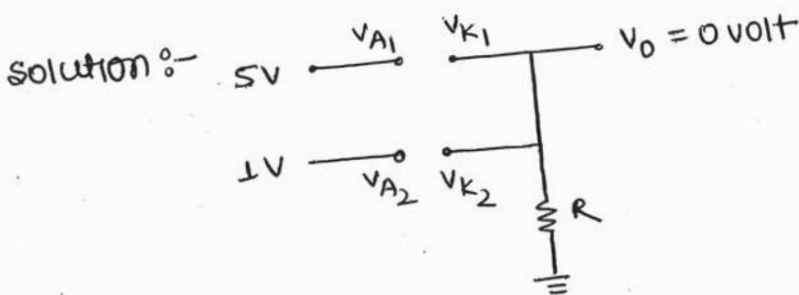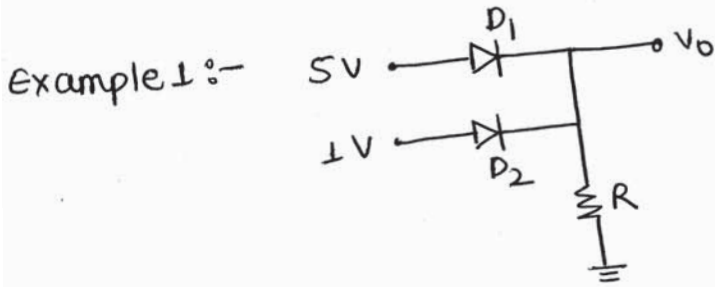


$$V_{A1} - V_{K1} = 5 - 0 = 5 > 0$$

$$V_{A2} - V_{K2} = 1 - 0 = 1 > 0$$

Two diodes ON simultaneously
then recheck condition

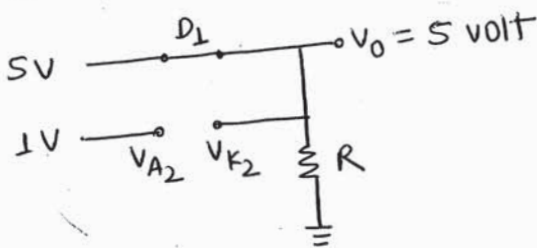Select D_1 ON first because it is more FB




$$V_{A2} - V_{K2} = 1 - 5 = -4 < 0$$

$\rightarrow D_2$ become OFF

Highest voltage will be ON first.

V-I characteristic of ideal diode :-

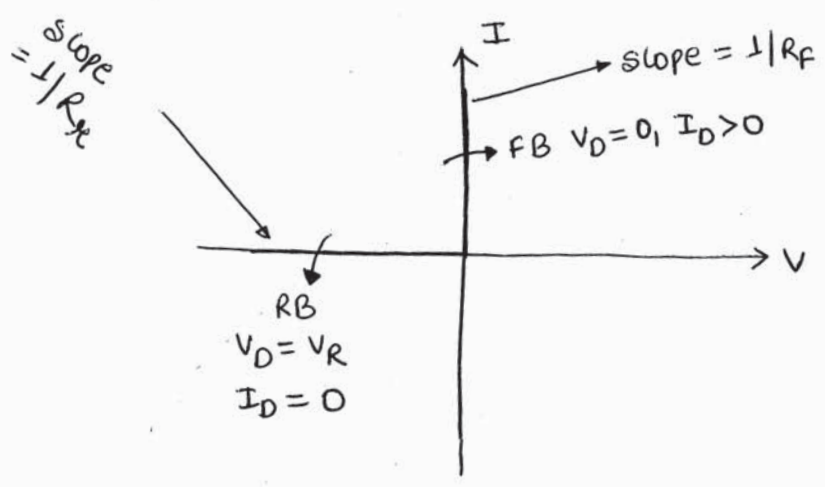

Indication : R_F = forward diode resistance
 R_R = Reverse diode resistance

In forward bias : $\text{slope} = \frac{1}{R_F} = \infty \Rightarrow R_F = 0$ ideal diode

In reverse bias : $\text{slope} = \frac{1}{R_R} = 0 \Rightarrow R_R = \infty$ ideal diode

CVD model :-

CVD means constant voltage drop model
 Practical diode will have cut in voltage V_Y .

V_Y (si) \rightarrow 0.5V to 0.7V


$V_D = V_Y$ then $V_D = V_{D,ON}$

condition for CVD model :-


$V_A - V_K > V_{D,ON}$ then D ON

$V_A - V_K < V_{D,ON}$ then D = OFF


$V_A - V_K = V_{D,ON}$ then D just ON.

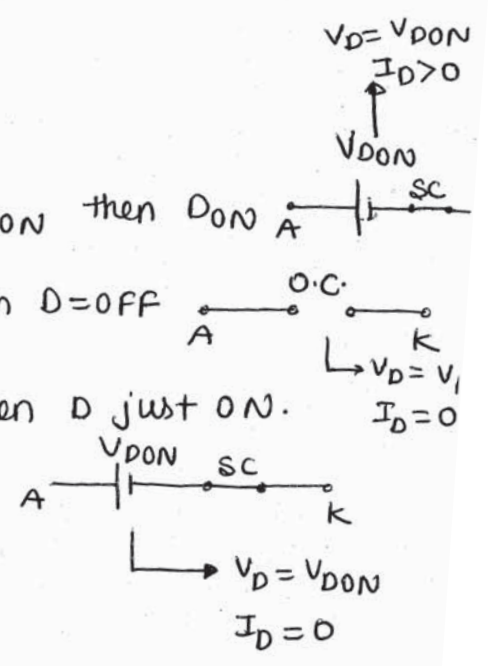

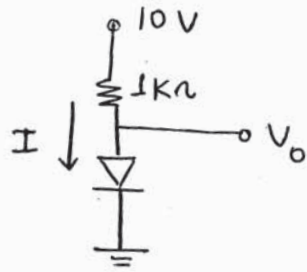EX 1 :- Check the status of diode and calculate V_o and I using Ideal & CVD model.



Solution :- Ideal condition :- [sc Test]

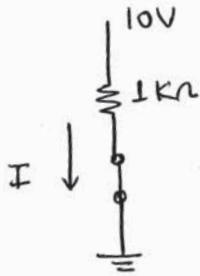


$$I = \frac{10 - 0}{1K}$$

$$= 10\text{mA} > 0 \text{ then } D \text{ ON}$$

$$V = 0, I = 10\text{mA}$$


CVD condition :- [sc Test]

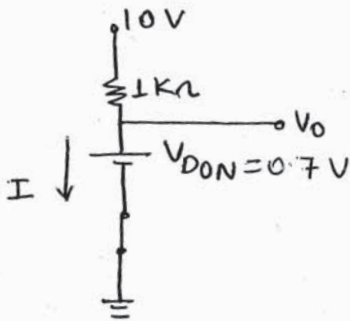


$$I = \frac{10 - 0.7}{1K} = 9.3\text{mA} > 0 \text{ then } D \text{ ON}$$

$$V_o = 0.7\text{VOLT}, I = 9.3\text{mA}$$

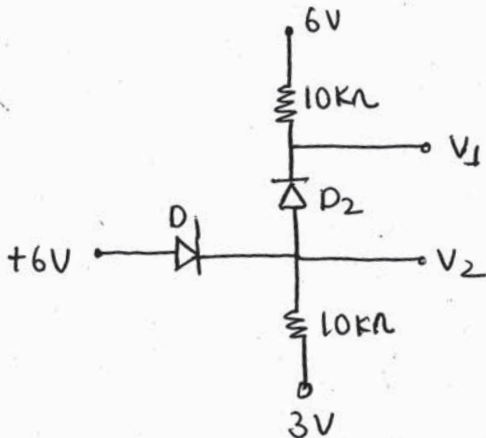Q: N: 14 The voltage at V_1 & V_2 of the arrangement shown in figure will be respectively $V_1 = 0.6$ volt



Solution:-

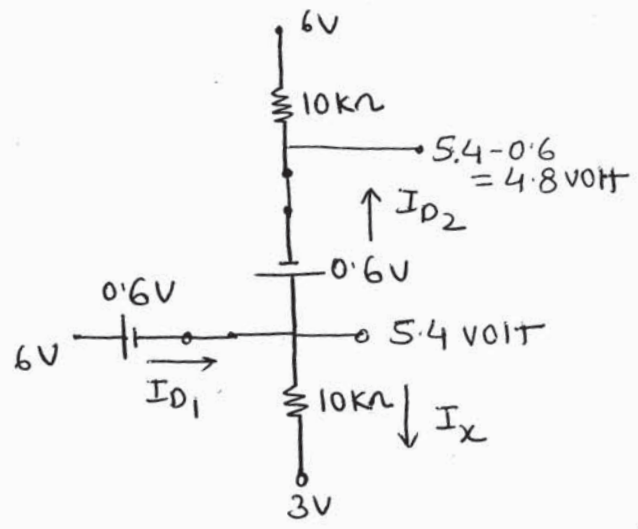

$$I_x = \frac{5.4 - 3}{10K} = 0.24 \text{ mA}$$


$$I_{D2} = \frac{4.8 - 6}{10K} = -0.12 \text{ mA} < 0$$

↳ D_2 is in OFF condition


KCL @ 5.4V


$$I_{D1} = I_{D2} + I_x = -0.12 + 0.24 = 0.12 \text{ mA} > 0$$

↳ D_1 is in ON condition

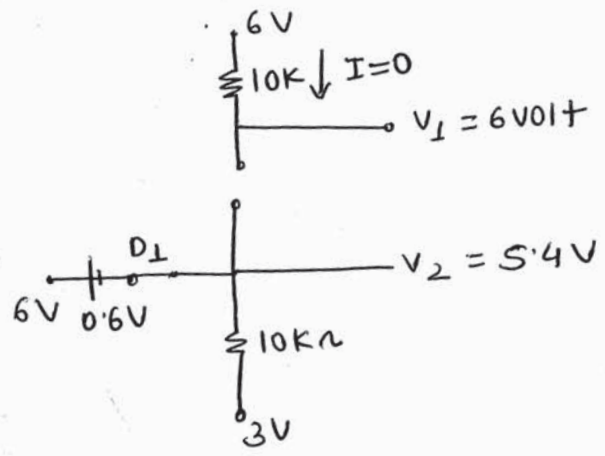

V-I characteristic of CVD model :-

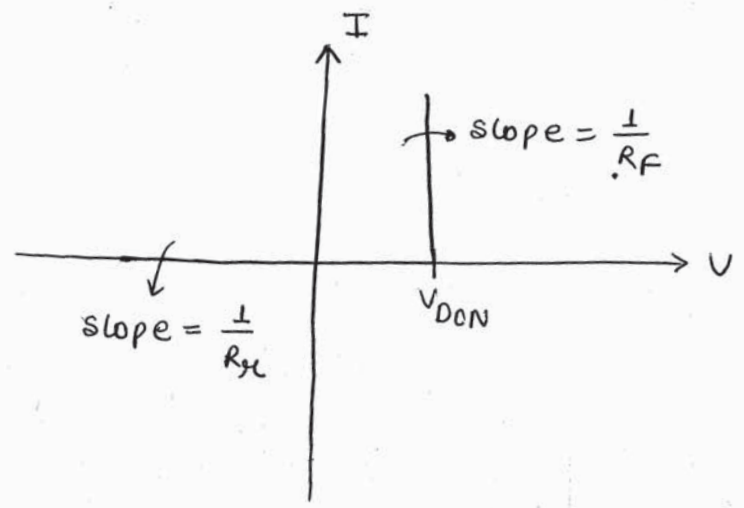

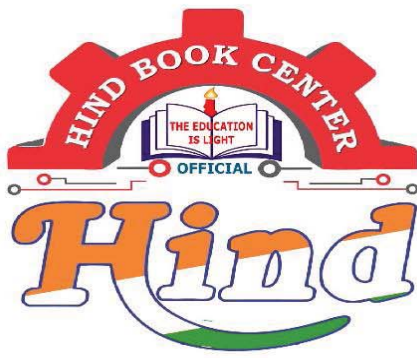

Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
07.POWER SYSTEM 1
BY- BALA JI SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

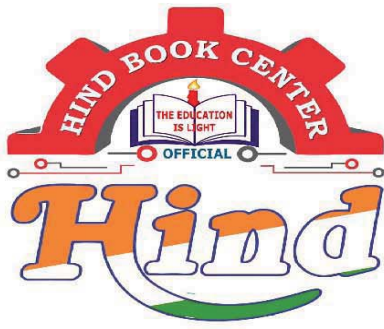Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Standard voltages used in India :-

HVAC RMS line to line voltage / line voltage (kV) :

Transmission Network voltage (kV) -

- 1200 kV (maximum in India) Maharashtra
- 765, 400
- 220, 132
- 66

Distribution Network voltages (kV) -

- 33 kV, 11 kV

Industrials uses - 6.6 kV, 3.3 kV, 1.1 kV, 400V

Houses uses - 230V (phase voltage)

Frequency $f = 50 \text{ Hz}$

HVDC $\pm 500 \text{ kV}, \pm 800 \text{ kV}, f = 0 \text{ Hz}$

Q.N:- The rated voltage of a 3-phase power system is -
- RMS line to line voltage

All India Installed capacity sector : 382.730 GW

Coal : 209294.5 MW

Gas : 24924 MW

Nuclear : 6780 MW

Hydro : 46209.22 MW

Diesel : 509.71 MW


Renewable Energy source : 95012.59 MW

WR : 74320 MW by coal largest power utilisation
NER : 770 MW by coal smallest

Thermal : Coal + Lignite + Gas + Diesel

30th June 2021 → maximum power consumed by 193 GW at 12:46 pm

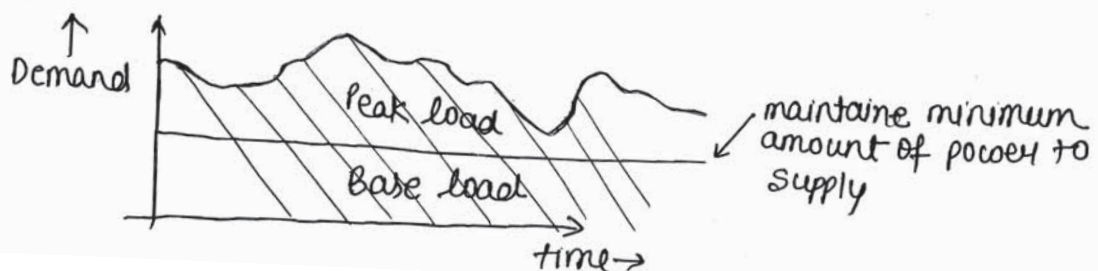
variable load curve : All India Demand (GW) v/s time



Base load -: Thermal plant

Next to peak load : Geas, wind, solar

Peak load -: Hydro plant

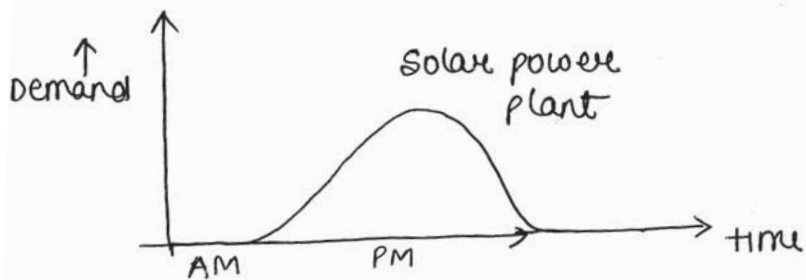

1 kWh = 1 unit

2019-20 1208 kWh per capita consumption

Objectives of power system :-


(i) Cost of electric energy must be low.

- Economic factors
- Economic load dispatch

(ii) Reliable power supply i.e; no interruption of power supply

- power generation methods
- Transmission
- Distribution
- Load flow studies

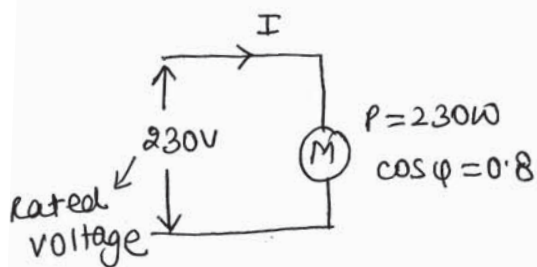(iii) Maintain constant voltage i.e; supply rated voltage to consumer



$$P = VI \cos \phi$$

$$I = \frac{P}{V \cos \phi} = \frac{230}{230 \times 0.8} = 1.25 \text{ A}$$

suppose supply voltage get reduce to $V = 200$ volts then current drawn by motor will be

$$I = \frac{230}{200 \times 0.8} = 1.4375 \text{ A}$$

$$\% \text{ increase in current} = \frac{1.4375 - 1.25}{1.25} \times 100 = 15\%$$


current drawn by motor is high value. this will causes overheating

To get constant voltage — voltage / reactive power control

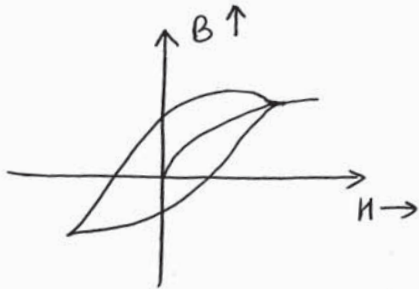(iv) Maintain Rated frequency

$$f = 50 \text{ Hz} \pm 1\% \quad (49.5 \text{ to } 50.5) \text{ Hz (ideal case)}$$

$$= 50 \text{ Hz} \pm 3\% \quad (48.5 \text{ to } 51.5) \text{ Hz (practical case)}$$



power T/F: $V = 4.44 f \Phi_m N$

$$\downarrow f \propto \Phi \uparrow \rightarrow \text{causes core saturation}$$

for this \rightarrow load frequency control

(v) Faster fault identification and clearance of fault in minimum time

- fault analysis
- protection

(vi) Stable generation has to be maintained

- stability

(viii) Flexible power transfer

- power cable

Panther	— 132 KV
Zebra	— 220 KV
Moose	— 400 KV

- ° Transmission line Parameters & Performance °-

By using transmission line, electric power is transfer from the remote generating station to the load centre (electric power utilised).

Material of Transmission line °-

ACSR - Aluminium conductor steel Reinforced

steel is used at the centre because it has higher mechanical strength to withstand and carry large weight of ACSR conductor.

4 layer ACSR (37-30|7)
 strands ← ↓ ↓
 Al steel

5 layer ACSR (61-54|7)
 strands ← ↓ ↓
 Al steel

No. of strands : $N = (3x^2 - 3x + 1)$

Total Dia $D = (2x - 1)d$

$x =$ layer number

$d =$ dia of each strands

Technical name of ACSR :- Animal like, Zebra, Panther, Moose, Dog etc is used for Aluminium for European standard and bird name like Swan, Sparrow, Raven, Pigeon etc is used as for US standard.

Power carrying capacities at 65°C :-

At 132 KV with 'Panther' ACSR = 75 MVA

At 220 KV with 'Zebra' ACSR = 200 MVA

At 400 KV with 'Moose' ACSR = 500 MVA

$$3\phi T/L \Rightarrow \sqrt{3} V \cdot I \cdot \cos\phi = P_{3\phi}$$

$$\sqrt{3} \times 400 \times 10^3 \times I \times 0.95 = 500 \times 10^6$$


$$I = 759.67 \text{ A carrying current by Moose}$$

Tower configuration :-


3 bundle conductor not practically used due to mechanical strength.

conductance (G) :- The leakage current flowing through the supporting insulator is represented by the conductance parameter. Its value is very small and hence neglected in case of short & medium line and consider in the long transmission.

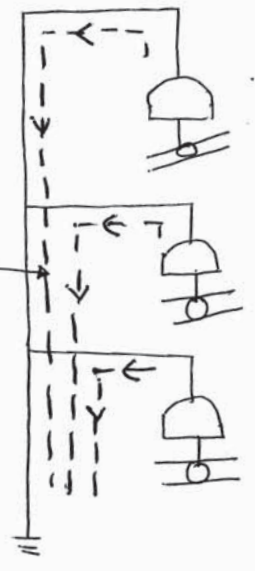
Electrical equivalent of leakage current \Rightarrow conductance (G)



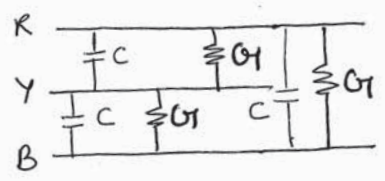leakage current due to small value of resistance in insulator (Negl.)



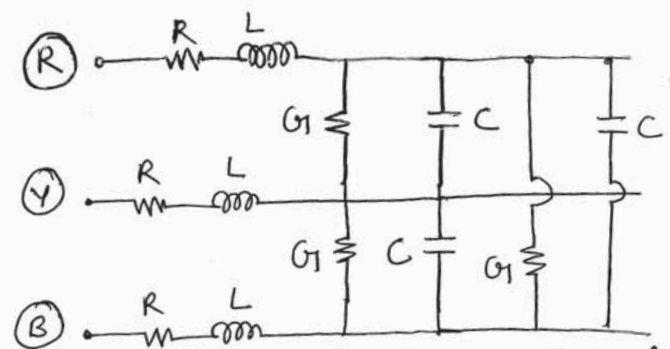
series element \Rightarrow R & L
shunt element \Rightarrow C & G




-: Electrical eq^t of x-mission line :-

Resistance :-

HVAC :-

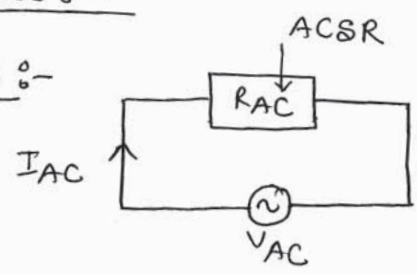


HVDC :-

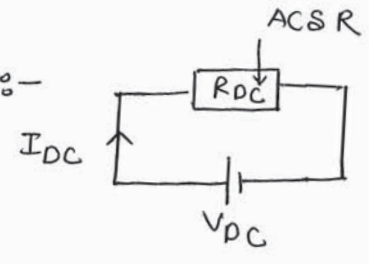


$R_{AC} > R_{DC}$

due to (i) skin effect
(ii) proximity effect

$R_{AC} = 1.5 R_{DC}$

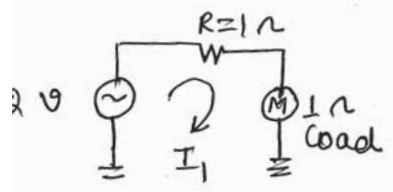

$I_1 = \frac{2}{1+1} = \frac{2}{2} = 1A$

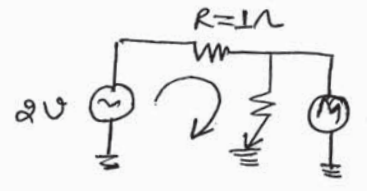

$I_2 = \frac{2}{1} = 2A$

$I_2 = 2I_1$ during short ckt condition

short ckt rating : KA/s [maximum current able to withstand during fault]


RTS : KN

(i) skin effect :-

① Accumulation of the current on the surface of conductor is called skin effect

⊙ outwards current

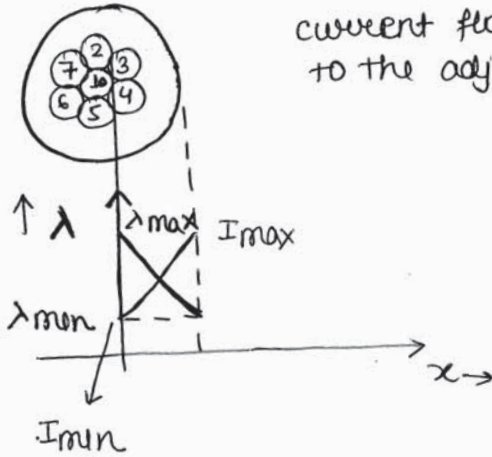current flowing in the conductor producing flux to the adjacent of conductor




λ_{max} i.e; L_{max} then $X_L \uparrow$

$$\downarrow I = \frac{V}{X_L \uparrow}$$

λ_{min} i.e; L_{min} then $X_L \downarrow$

$$\uparrow I = \frac{V}{X_L \downarrow}$$


HVDC :

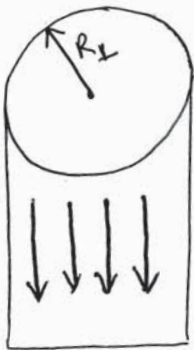

uniform current is flowing because there is no rate of change of flux.

$$R_{DC} = \frac{\rho l}{\pi R_1^2}$$

HVAC :

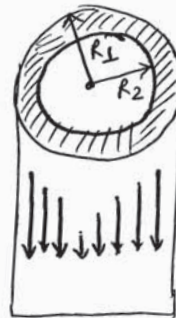

$$R_{AC} = \frac{\rho l}{\pi (R_1^2 - R_2^2)}$$


② Due to skin effect, effective area of current flowing path is reduced which causes $R_{AC} > R_{DC}$ in HVAC system.

③ skin effect depends on f, σ, μ_r and size of the conductor.

④ skin effect is more in communication line because frequency is in MHz range and this effect is neglected in power lines because the frequency is less (50Hz) only.

f = supply frequency, μ_r = Relative permeability, σ = conductivity

Skin depth (δ) :-

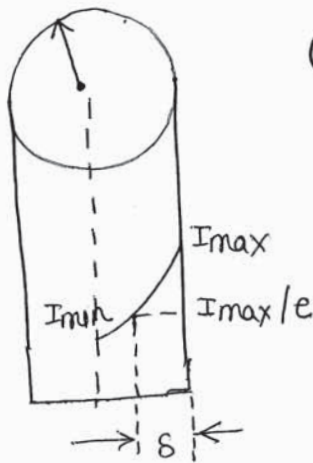


(a) The depth of the conductor at which the current is drop to $(1/e)$ time of the maximum current & that depth is called as skin depth.


$$\delta = \frac{1}{\sqrt{\pi f \mu_0 \mu_r \sigma}} \propto \frac{1}{\text{skin effect}}$$

- (b) when skin depth is less then more accumulation of current on the surface of conductor, then skin effect will be more
- (c) In HVDC, no skin effect because $f = 0$

Proximity effect :-

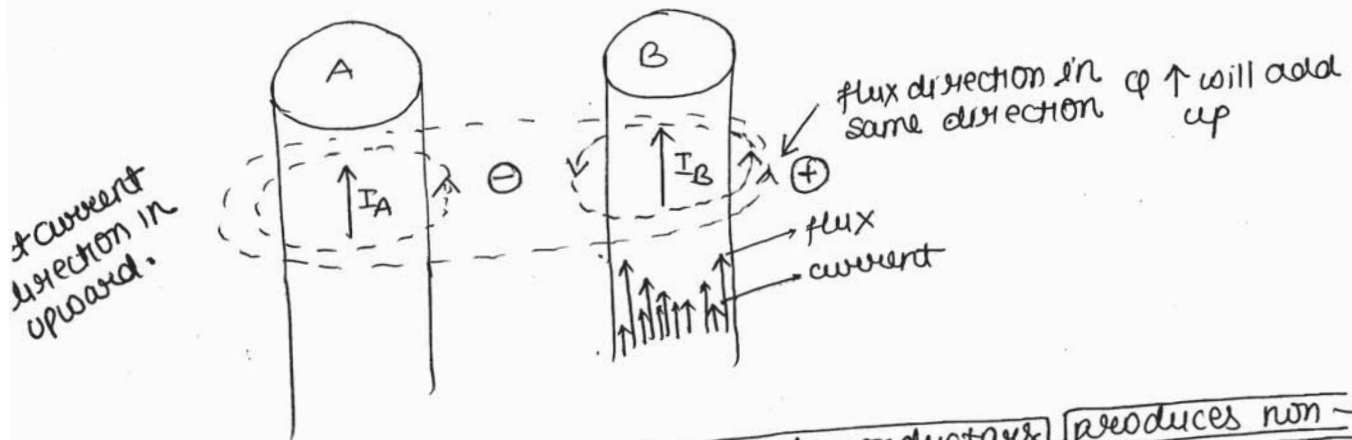

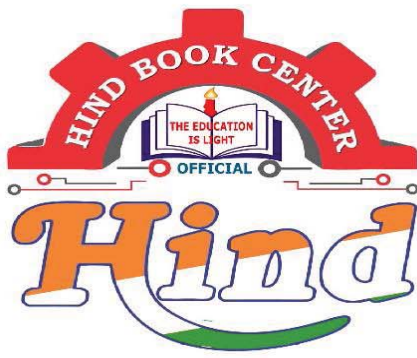- (a) The current flowing in the adjacent conductors produces non-uniform flux linkage which will cause non-uniform current flow so, that the effective area of current flowing path is reduce which causes $R_{AC} > R_{DC}$ (we are not able to use whole area).
- (b) Proximity effect depends on f, μ_r, σ & distance between the conductor.
- (c) This effect is more in power cable and less in overhead transmission line because .



Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
08.POWER SYSTEM- II
BY- BHOOPENDR SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

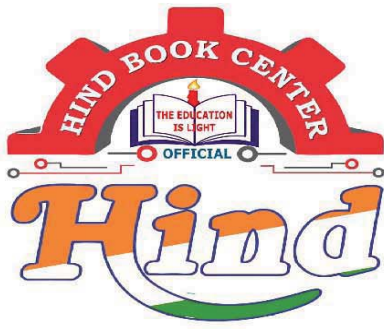Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE


Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Power Analysis of AC circuit :-

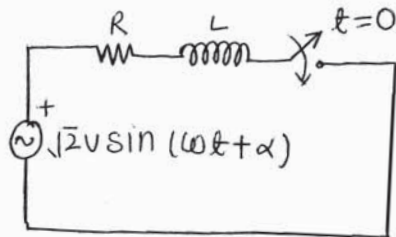(i) A circuit which is in steady state corresponding to a given sinusoidal excitation is called an AC circuit.



Not an AC circuit

because it is in transient state

∴ $i(t) = i_{SS} + i_{TR}$


i_{SS} = steady state response depends upon the source

i_{TR} = Transient response depends upon the circuit itself

$i(t) = \sqrt{2} I \sin(\omega t + \beta) + A e^{-t/\tau}$

∴ Responses are non-sinusoidal

$t \rightarrow \infty$ (SS)

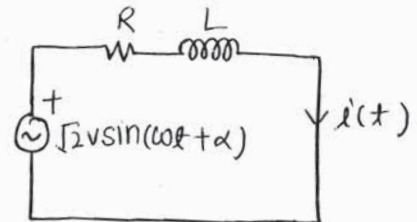

An AC circuit


$i(t) = \sqrt{2} I \sin(\omega t + \beta)$

Responses are sinusoidal and having same freq.


(ii) All the responses of an AC circuit are sinusoidal with frequency equal to the source frequency.

(iii) The magnitude (RMS value) and phase of a response in an AC circuit is computed using phasor technique.

EX:-

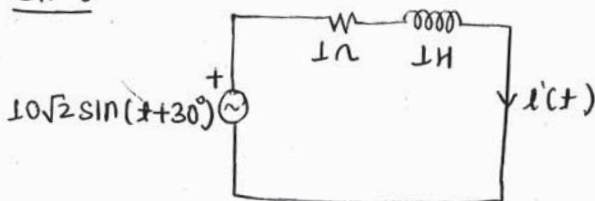

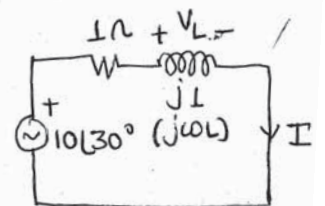Phasor domain eq^t ckt
ref. waveform = sin t



Reference waveform is selected such that frequency of ref. waveform should be equal to the frequency of source.

In phasor diagram equivalent ckt we have to take rms value.

$V_m = 10\sqrt{2} \Rightarrow V_{RMS} = 10$

	Time domain	Phasor domain	Frequency domain
Inductance	Henry (H)	jX or $j\omega L$	sL
Capacitance	Farad (F)	$1/(j\omega C)$	$1/sC$
Resistance	R	R	R

$$I(t) = \frac{10 \angle 30^\circ}{1 + j1} = \frac{10}{\sqrt{2}} \angle -15^\circ = 10 \sin(t - 15^\circ)$$


\downarrow
RMS value
 \downarrow
Maximum value

By applying voltage division rule

$$V_L = 10 \angle 30^\circ \left(\frac{j1}{1 + j1} \right) = \frac{10}{\sqrt{2}} \angle 75^\circ = 10 \sin(t + 75^\circ)$$

Now power analysis of an AC circuit

(iii) (find it) \vec{I} → absorbed

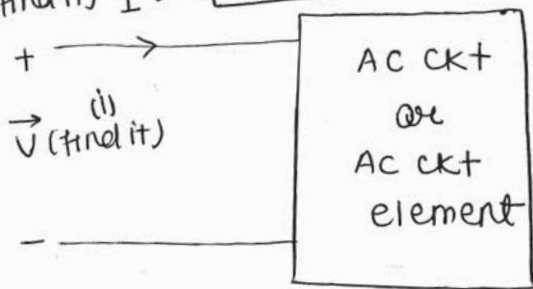

complex power absorbed by AC CKT or element

$$S = \vec{V} \vec{I}^* \quad \text{(iii)}$$

$$= P + jQ$$

(iv) then;

P = Active power / useful power / Avg. power / power absorbed by AC CKT or AC CKT element (watt)

Q = Reactive power / lagging VAR absorbed by the AC CKT element or AC CKT. (VAR)


By default Active power

$P > 0 \rightarrow$ CKT absorbed active power

$P < 0 \rightarrow$ CKT delivers active power

$Q > 0 \rightarrow$ CKT. absorbed Reactive power / lagging VAR
or
CKT delivers leading VAR

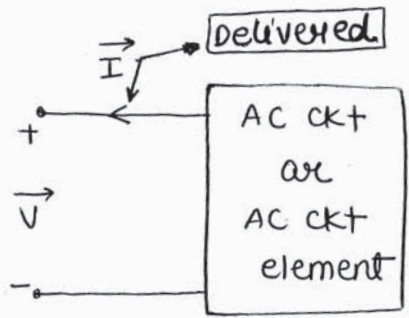$Q < 0 \rightarrow$ ckt delivers Reactive power / lagging VA or
 or
 ckt absorbs leading VA.



complex power delivered by AC ckt or AC ckt element
 $S = VI^* = P + jQ$

$P =$ Active power / useful power / Average Power / Power delivered by AC ckt or AC ckt element


$Q =$ Reactive power / lagging VA delivered by the AC ckt element or AC ckt.

$P > 0 =$ ckt delivers active power
 $P < 0 =$ ckt absorbs active power

$Q > 0 =$ ckt. delivers Reactive power / lagging VA or
 or
 ckt absorbs leading VA

$Q < 0 =$ ckt. absorbs Reactive power / lagging VA or
 or
 ckt delivers leading VA

EX-0

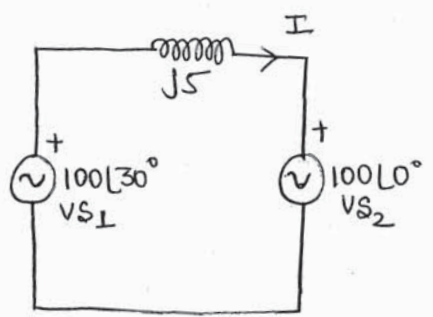

$$I = \frac{100\angle 30^\circ - 100\angle 0^\circ}{j5}$$

$$= 10.35\angle 15^\circ$$

complex power absorbs by VS_2


$$S = (100\angle 0^\circ) (10.35\angle 15^\circ)^* = 1000 - j268$$

VS_2 : absorbs 1000W and delivers 268 VA

complex power delivered by VS_1

$$S = 100\angle 30^\circ (10.35\angle 15^\circ)^* = 1000 + j268$$



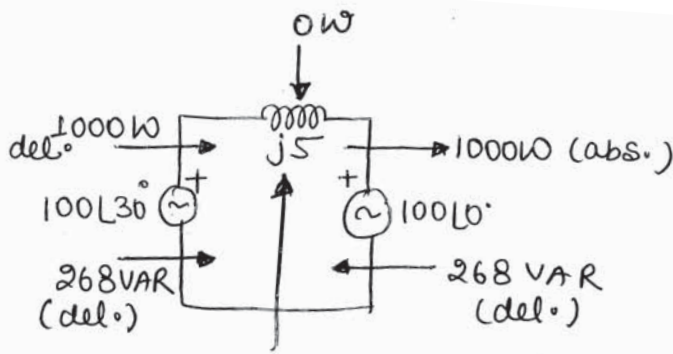
VS_1 : delivered 1000W and delivers 268 VA



536 VAR (abs.)
 = 268 VAR + 268 VAR & [Active power = 0 (always)]


NOTE:- In power system active power always flows from leading voltage source towards the lagging voltage source where as reactive power generally flow from voltage of high magnitude towards voltage of low magnitude.

EX:-

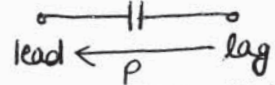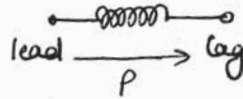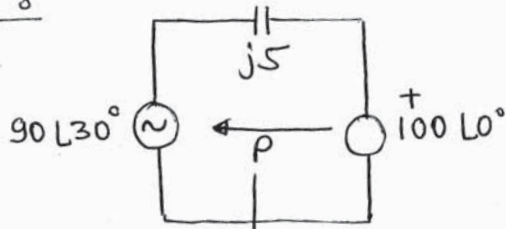

But in power system in series capacitor is not present i.e; not power system ckt.

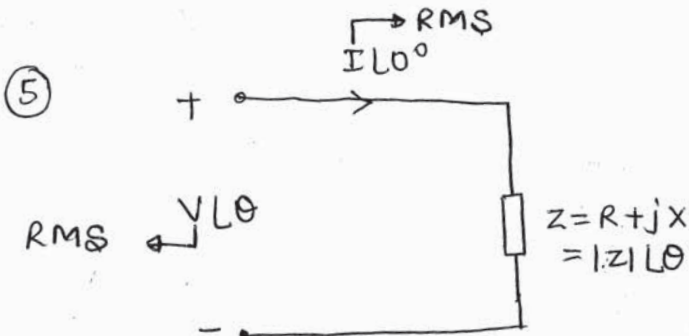i.e; flowing from lagging to leading voltage source because it is not power system ckt. \therefore the series branch of power system is always inductive in nature.




$x = +ve \rightarrow$ inductance
 $x = -ve \rightarrow$ capacitance

$Y = \frac{1}{Z} = G + jB$

$B = -ve \rightarrow$ inductance
 $B = +ve \rightarrow$ capacitance

$|Z| = \sqrt{R^2 + X^2}$

$\theta = \tan^{-1} \frac{X}{R}$

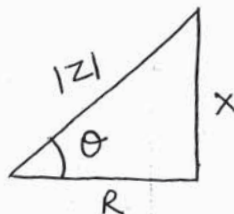

$\cos \theta = \frac{R}{|Z|}$

$\sin \theta = \frac{X}{|Z|}$



$\vec{V} = \vec{I} \vec{Z}$
 $= I L 0^\circ Z L \theta$
 $= I Z L \theta = V L \theta$

So, complex power absorbed by $z = R + jX$

$$S = P + jQ = (V L \theta) (I L \theta)^* = VI \cos \theta + j VI \sin \theta$$

$$P = VI \cos \theta = VI \frac{R}{|Z|} = \boxed{I^2 R} \quad \text{RMS value}$$

$$Q = VI \sin \theta = VI \frac{X}{|Z|} = \boxed{I^2 X} \quad \text{RMS value}$$

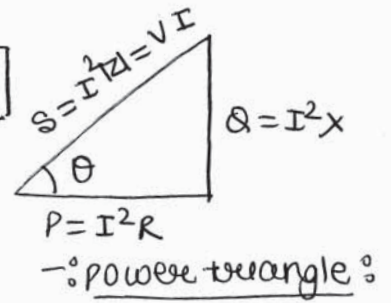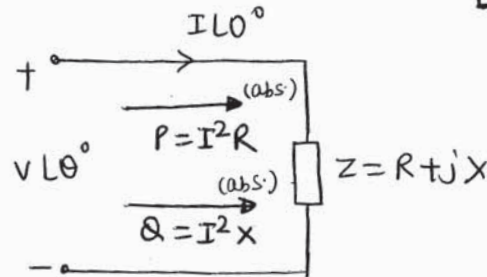





$$p.f. = \cos \theta = \frac{P}{S}$$

$R \geq 0 \rightarrow P \geq 0$ so, $z = R + jX$ can't deliver active power.

$X > 0$ (inductive) $\rightarrow Q > 0$ i.e; inductive Impedance absorbs Reactive power / lagging VAR
 (or) inductive Impedance delivers leading VAR


$X = 0$ (Resistive) $\rightarrow Q = 0$

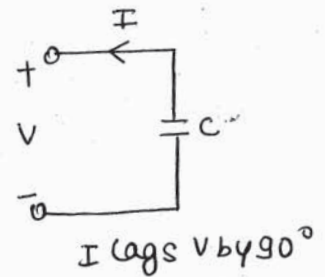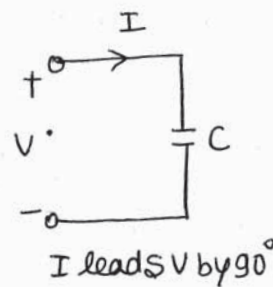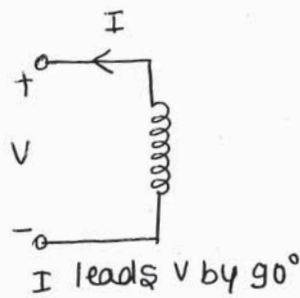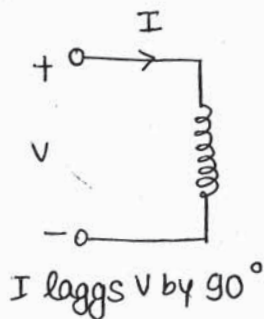$X < 0$ (capacitive) $\rightarrow Q < 0$ i.e; capacitive impedance delivers Reactive power / lagging VAR
 (or) capacitive Impedance absorbs leading VAR



(By default we take absorb current always)



EX-0

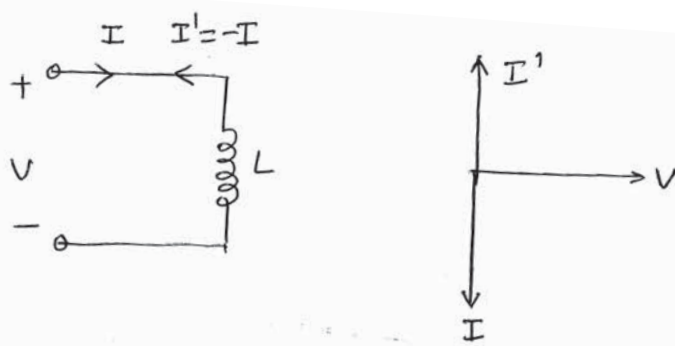

For I (अन्दर जाने वाली) current is lagging then it always absorbs lagging VAR.

For I' which is leads by V then it always delivers leading VAR.

NOTE-0

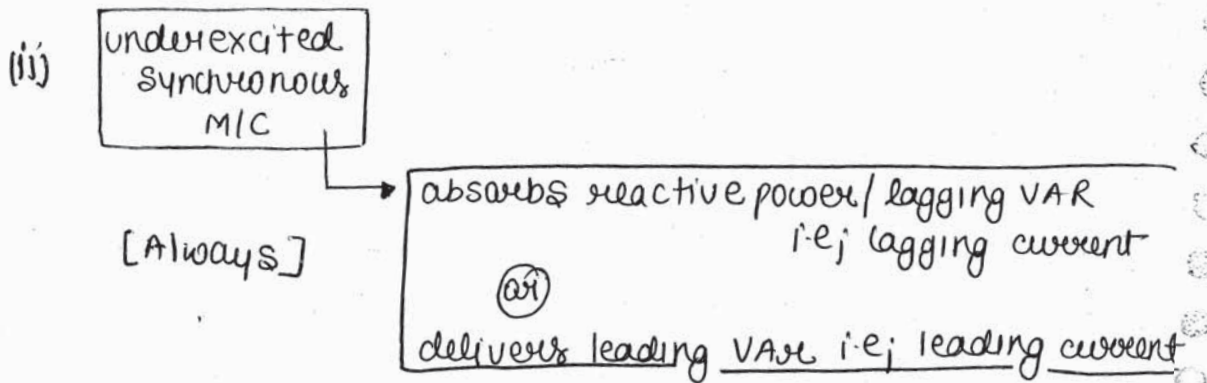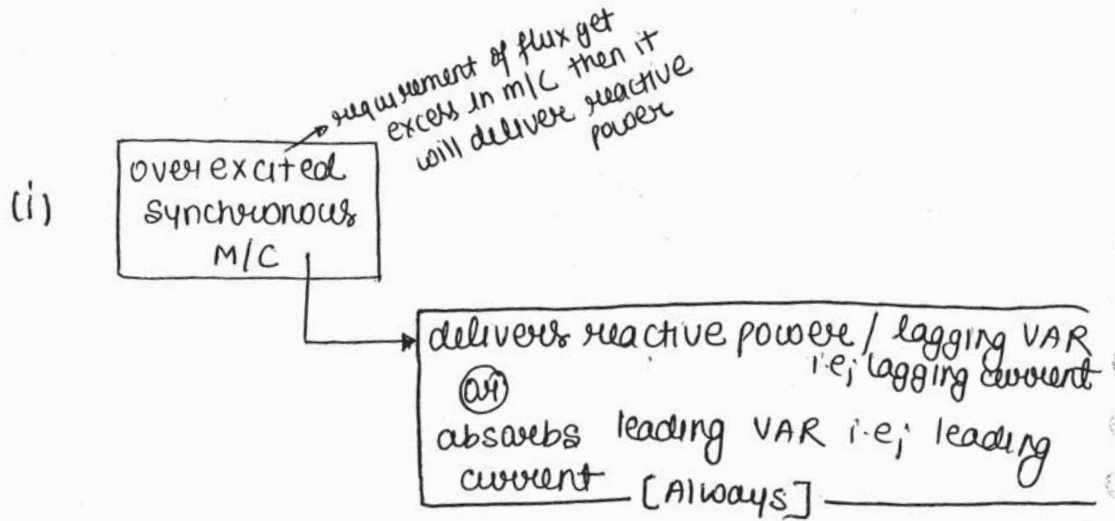

now; Motor → absorb the current & current may be leading or lagging in nature

Generator → delivers the current & current may be leading or lagging in nature


over excited syn. motor → motor absorbs the current i.e; absorbs leading VAR

we can say that $Pf \equiv$ leading

Over excited sync generator \rightarrow Generator delivers the current i.e; delivered lagging VASE i.e lagging current

we can say that $P.f \equiv$ lagging


#

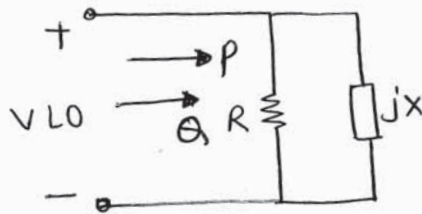

$$P = \frac{V^2}{R} \rightarrow \text{RMS value}$$

$$Q = \frac{V^2}{X} \rightarrow \text{RMS value}$$

Ex:-

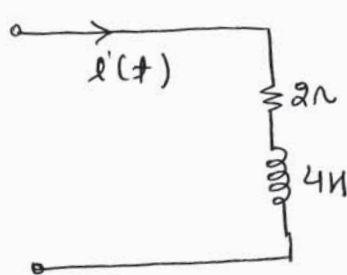

$$i(t) = 10 \sin(\omega t + 30^\circ)$$

$P = ? \quad Q = ?$

$$P = I^2 R = \left(\frac{10}{\sqrt{2}}\right)^2 \times 2 = 100 \text{ W}$$

$$[X = \omega L]$$

$$\omega = 2, L = 4$$

$$Q = I^2 X = \left(\frac{10}{\sqrt{2}}\right)^2 \times (2 \times 4) = 400 \text{ VAR}$$

$I =$ RMS value

Balance 3- ϕ system / concept of phase sequence :-

A polyphase system is said to be balance if


- (i) The magnitude of corresponding quantity are equal in each phase.
- (ii) The phase difference b/w the corresponding quantities is given by

$\theta = \frac{360^\circ}{n} ; n \neq 2$
$\theta = 90^\circ ; n = 2$

Q.N:- The current in 2-phases of a two phase system is given below

$$i_a = \sqrt{2} I \cos(\omega t - \phi_1) \quad i_b = \sqrt{2} I \sin(\omega t - \phi_2)$$

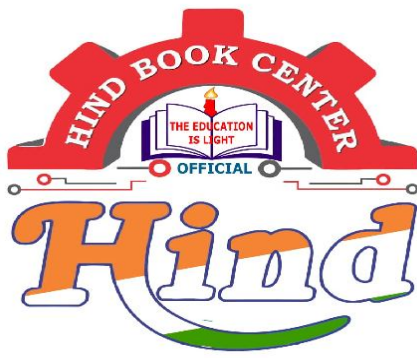Find the relationship b/w ϕ_1 and ϕ_2 so that the two phase system is balance system.



Hindbookcenter



Hind Book Center & Photostat


MADE EASY

**Electrical Engineering
Toppers Handwritten Notes
Electrical Machine
By-Murli Sir**

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

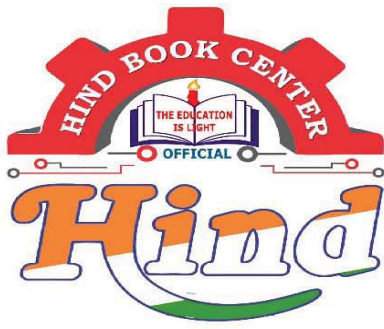**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393**



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -


MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

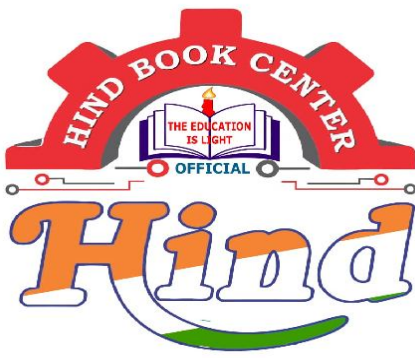

Hindbookcenter



Hind Book Center & Photostat

MADE EASY

Electrical Engineering Toppers Handwritten Notes


INDUCTION MACHINE

By-Murli Sir

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

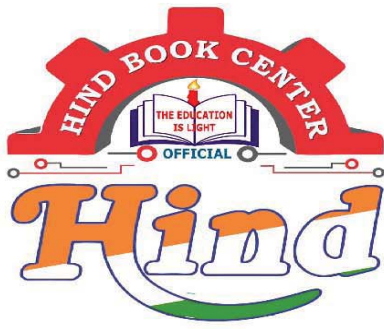Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

-: Induction machine :-

Due to complex construction, commutation problems, maintenance DC m/c find lesser practical applications.

while AC motor has simple construction, less maintenance hence these are most popular (85% motors)

- (i) Induction generator
- (ii) Induction motor


Rotating Magnetic field (RMF) :-

In IM, the flux is not stationary, it is rotating.

The basic requirement to produce the rotating magnetic field is

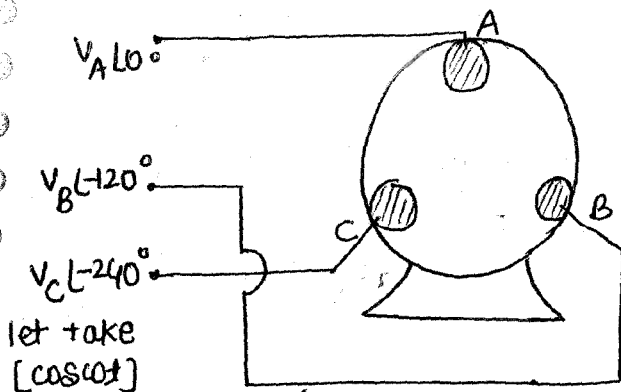- (i) 3 ϕ supply (120° phase displacement $(\omega \cdot t \cdot \text{time})$)
 - (ii) 3 ϕ winding (120° phase displacement $(\omega \cdot t \cdot \text{space})$)
- } Balance

If we want to generate 3-ph voltages which has 120° phase displacement we have to design a winding which has exactly 120° space displacement, the space displacement which we provide in the winding will create time displacement in the voltages which are induced.



Balance winding i.e; Number of turns are equal in all the winding.

Balance supply i.e; $|V_A| = |V_B| = |V_C|$ & 120° phase displacement

$$\text{mmf} = NI$$

$V_A L-0^\circ$	\longrightarrow	$I_A N_A$	\longrightarrow	F_A	\longrightarrow	Φ_A
$V_B L-120^\circ$	\longrightarrow	$I_B N_B$	\longrightarrow	F_B	\longrightarrow	Φ_B
$V_C L-240^\circ$	\longrightarrow	$I_C N_C$	\longrightarrow	F_C	\longrightarrow	Φ_C

$$\text{net mmf produce} = \vec{F}_A + \vec{F}_B + \vec{F}_C$$

$$\text{net flux produce} = \vec{\Phi}_A + \vec{\Phi}_B + \vec{\Phi}_C$$

Now, $I_A = I_m \cos \omega t$

$$N_A = N \cos \theta$$

$$I_B = I_m \cos (\omega t - 120^\circ)$$

$$N_B = N \cos (\theta - 120^\circ)$$

$$I_C = I_m \cos (\omega t - 240^\circ)$$

$$N_C = N \cos (\theta - 240^\circ)$$

where ωt = time displacement angle (ele.)

θ = space displacement angle (ele.)

$$F_A = I_A N_A = I_m \cos \omega t \cdot N \cos \theta$$

$$F_B = I_B N_B = I_m \cos(\omega t - 120^\circ) \cdot N \cos(\theta - 120^\circ)$$

$$F_C = I_C N_C = I_m \cos(\omega t - 240^\circ) \cdot N \cos(\theta - 240^\circ)$$

$$\cos A \cdot \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Net / Resultant mmf $F_{net} = F_A + F_B + F_C$

$$F_{net} = I_m N [\cos \omega t \cdot \cos \theta + \cos(\omega t - 120^\circ) \cdot \cos(\theta - 120^\circ) + \cos(\omega t - 240^\circ) \cdot \cos(\theta - 240^\circ)]$$

$$= I_m N \left[\frac{1}{2} \{ \cos(\omega t + \theta) + \cos(\omega t - \theta) \} + \frac{1}{2} \{ \cos(\omega t - 240^\circ + \theta - 120^\circ) + \right.$$

$$\left. \cos(\omega t - 120^\circ - \theta + 120^\circ) \} + \frac{1}{2} \{ \cos(\omega t - 240^\circ + \theta - 240^\circ) + \cos(\omega t - 240^\circ - \theta + 240^\circ) \} \right]$$

$$= \frac{I_m N}{2} \left[\begin{aligned} &\cos^*(\omega t + \theta) + \cos(\omega t - \theta) + \cos^*(\omega t + \theta - 240^\circ) + \cos(\omega t - \theta) \\ &+ \cos^*(\omega t + \theta - 480^\circ) + \cos(\omega t - \theta) \end{aligned} \right] \quad [* + * + * = 0]$$

$$F_{net} = \frac{I_m N}{2} [3 \cos(\omega t - \theta)]$$

$$F_{net} = \frac{3}{2} I_m N \cos(\theta - \omega t)$$

(or)

$$F_{net} = \frac{3}{2} F_m \cos(\theta - \omega t)$$

i.e; The net mmf wave is cosine or sine, it is travelling w.r.t. space & time both. So; it is function of space angle and time angle. If we don't have the two combination which are 3- ϕ supply (120° E phase displacement) and 3-ph windg (120° E phase displacement w.r.t. space) then mmf wave don't come like this.

$$\text{speed} = \frac{\text{Distance}}{\text{Time}}$$

Imagine mmf wave has some velocity or speed and displacement w.r.t.

$$\text{speed} = \frac{\omega t}{t} = \omega \text{ Elect-rad/sec}$$

$$N = rpm$$

$$N/60 = rps$$

$$\omega = 2\pi f \text{ elet-rad/sec}$$

$$\omega_m = \frac{2\pi N}{60} \text{ mech-rad/sec}$$

$$\theta_e = \frac{P}{2} \theta_m$$

similarly, $\omega_e = \frac{P}{2} \omega_m \Rightarrow 2\pi f = \frac{P}{2} \cdot \frac{2\pi N}{60}$


$$f = \frac{PN}{120}$$

so, $N = \frac{120f}{P}$

we know that $F_{net} = \frac{3}{2} F_m \cos(\theta - \omega t)$

let $\omega t = 0$ then $F_{net} = \frac{3}{2} F_m \cos \theta$

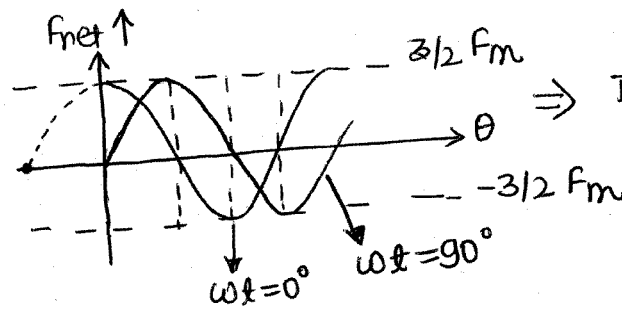let $\omega t = 90^\circ$ then $F_{net} = \frac{3}{2} F_m \sin \theta$



Travelling or moving with constant ampli. w.r.t. space

If

$I_A = I_m \cos \omega t$
$I_B = I_m \cos (\omega t)$
$I_C = I_m \cos (\omega t)$

$N_A = N \cos \theta$
$N_B = N \cos (\theta - 120^\circ)$
$N_C = N \cos (\theta - 240^\circ)$

Then $F_{net} = 0$ if voltage and current are co-phased.


NOTE:- By reversing the phase sequence the direction of movement of mmf is also reverse.

Another approach:-

$$\phi_A = \phi_m \sin \omega t$$

$$\phi_B = \phi_m \sin (\omega t - 120^\circ)$$
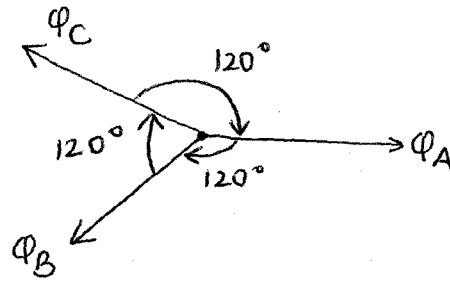
$$\phi_C = \phi_m \sin (\omega t - 240^\circ)$$




At $\omega t = 0^\circ$

$$\phi_A = 0$$

$$\phi_B = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_C = \frac{\sqrt{3}}{2} \phi_m$$

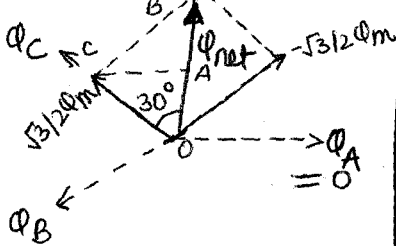

$OB = 2OA$, $\angle AOC = 30^\circ$
from ΔOAC

$$\cos 30^\circ = \frac{OA}{OC}$$

$$OA = OC \cos 30^\circ$$

$$= \frac{\sqrt{3}}{2} \phi_m \cdot \frac{\sqrt{3}}{2}$$

$$OA = \frac{3}{4} \phi_m$$

$$OB = \phi_{net} = 2OA$$


$$\phi_{net} = \frac{3}{2} \phi_m$$

At $\omega t = 60^\circ$

$$\phi_A = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_B = -\frac{\sqrt{3}}{2} \phi_m$$

$$\phi_C = 0$$

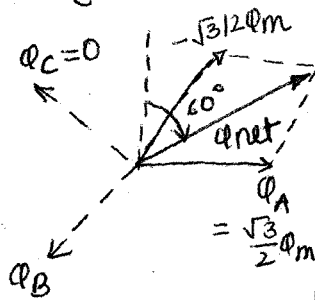


$$\phi_{net} = \frac{3}{2} \phi_m$$

At $\omega t = 120^\circ$

$$\phi_A = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_B = 0$$

$$\phi_C = -\frac{\sqrt{3}}{2} \phi_m$$

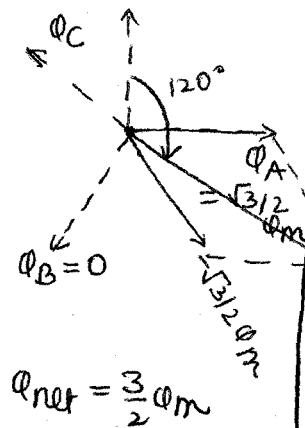


$$\phi_{net} = \frac{3}{2} \phi_m$$

At $\omega t = 180^\circ$

$$\phi_A = 0$$

$$\phi_B = \frac{\sqrt{3}}{2} \phi_m$$

$$\phi_C = -\frac{\sqrt{3}}{2} \phi_m$$

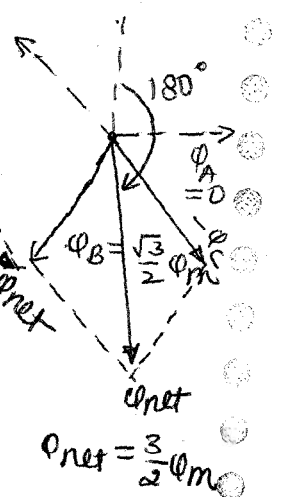

$$\phi_{net} = \frac{3}{2} \phi_m$$

synchronous



i.e; time (moving together with time)


when flux rotate in the m/c then that flux speed will be synchronous speed. It depends on two factors which are frequency and number of pole.

$$\phi_{net} = \frac{3}{2} \phi_m$$

$$N_s = \frac{120f}{p}$$

Characteristics of RMF :-

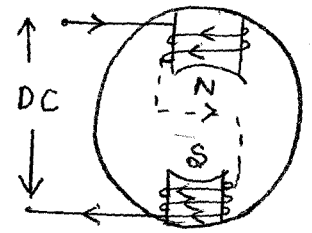
- (i) **RMF** has **constant value** ($1.5 \phi_m$)
- (ii) **RMF** revolves with $N_s = 120f/p$



[To know North pole or south pole we have to apply **Right hand rule**.]

If we reverse the polarity of battery then current direction gets change then $N \rightarrow S$ and $S \rightarrow N$. So, when reversal action is not happening then DC supply is having $f=0$ due to which pole is not going to change in any manner.


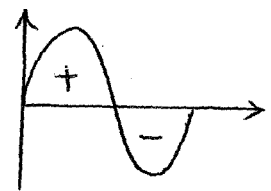
when we talking about AC supply with $f=50\text{Hz}$ i.e; 1 cycle in 1 sec



so in +ve cycle the polarity of pole is same as before but in -ve cycle $N \rightarrow S$ & $S \rightarrow N$. (or) North at top \rightarrow bottom
South at bottom \rightarrow top

$$N_s \propto \frac{1}{p}$$

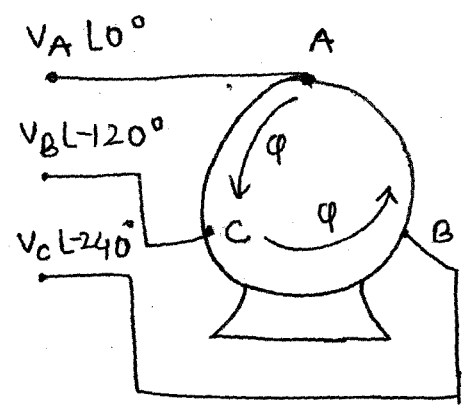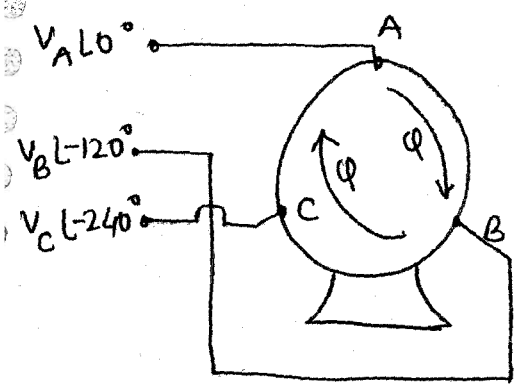(iii) **RMF flows** from **leading phase to lagging phase**. Its **direction of rotation** can be **reversed** by **reversing any two phase sequence of supply**.



Construction details of Induction machine :-

- (i) Stator
 → Frame
 → core
 → 3-ph winding

↓
Stationary part

- (ii) Rotor
 → squirrel cage
 → slip ring or wound rotor

↓
Rotating part


- (iii) Air gap
 → least possible

$$\text{Flux} = \frac{\text{MMF}}{\text{Reluctance}}$$
(0.3mm to 4mm)

Frame :- Frame offers mechanical protection to the m/c.

core :- core is laminated structure [Si-steel lamina 0.35-0.5 mm thickness]

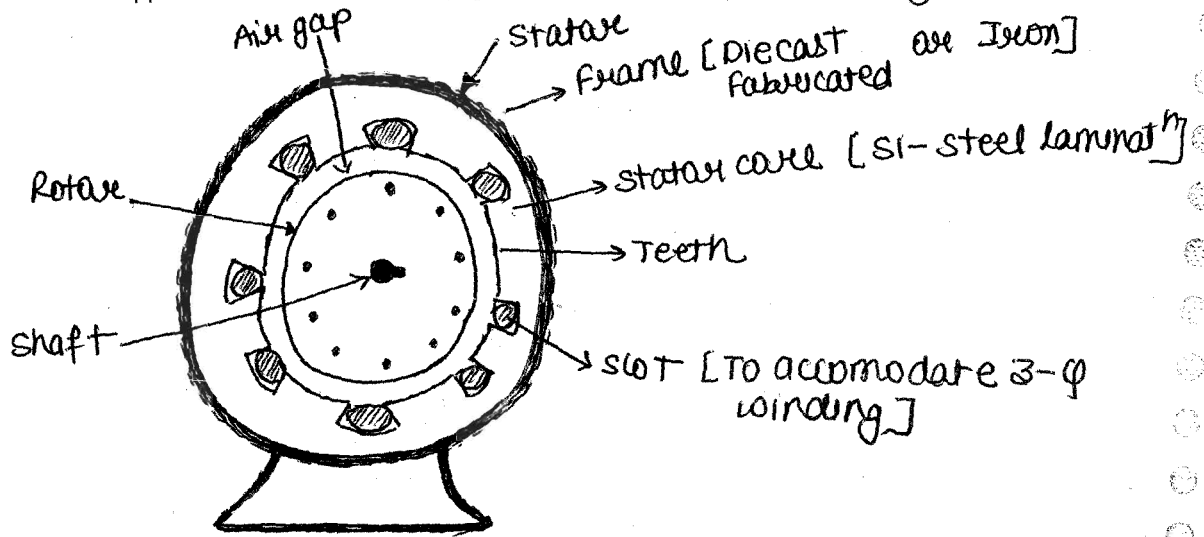
Slot :- slot offers mechanical protection to the winding.



Type of slots :-

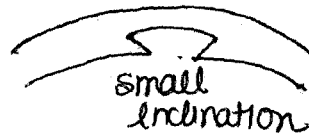- (i) open slot (ii) closed slot (iii) semi-open / semi closed slot

NOTE:- In slot, there is small inclination to avoid creeping of armature winding i.e., due to mechanical vibration the winding which is placed in slot may come out. that process is known as creeping.



NOTE:- Sometime in slot, wedge is also form because after placing the winding in slot, some strip is to placed so that they are supporting it [compulsary in rotating m/c]



NOTE:- In rotating electrical m/c we never see CRGO core type of structure because in this flux is rotating in air gap also. So, Si-steel lamination is enough for it.

To make flux as maximum as possible for that we have to maintain reluctance to be minimum as much as possible for this we have to maintain least possible air gap. (0.3mm to 4mm)

In small m/c : Air gap = 0.3mm
 large m/c : Air gap = 4mm


Air gap \uparrow \rightarrow $I_m \uparrow$
 \rightarrow Drawback

NOTE:- Yoke & frame both are different to each other. In D/C machine the flux is passing through yoke only

\Rightarrow Casting is process considering molten metal. on moulding it gets its shape. & fabrication is solid metal only.

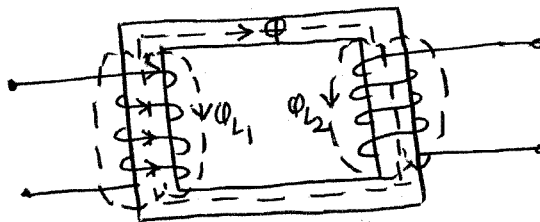(i) open slot :-

- Easy to place the winding in slot
- owing maintenance, repair or routine service, it is so easy.
- simple design
- leakage flux %




\Rightarrow If flux is linking with two winding then it is useful flux because it is transferring the energy

\Rightarrow If flux is linking ^{& leaking} with only one winding then it is not participating in the transferring the energy. [wasted]

Link
 - % Reluctance
 more Air gap then Reluctance will be higher.

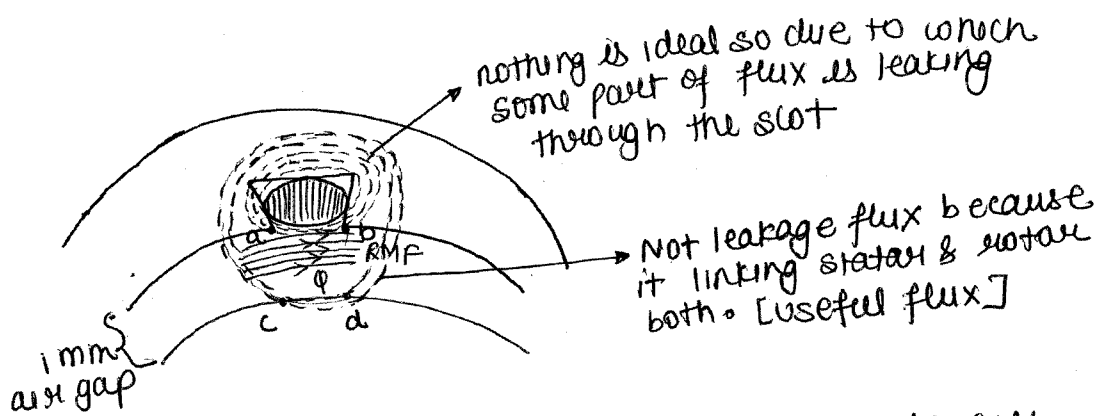Leak
 - % Reactance
 more leakage of flux then Reactance will be also more



The gap between a and b is not air gap but it accounts air gap. but the air gap will be between stator and rotor. The air gap between a and b is within the stator. So, air gap is radial length between a & c, b & d. But during resultant/net air gap, the gap between a & b will be consider.

leakage path is between a to b. when we reduce the air gap i.e; 1mm \rightarrow 0.5mm then maximum no. of line in comparison with before become linkage flux because while leaking the flux it gets link.

So, lesser the air gap we have excellent flux linkage i.e; more useful flux. & vice-versa.


Imagine rotor are touching the stator then leakage flux will be minimum. But rotor will not rotate. So, we need mechanical clearance between stator and rotor part. So we maintain as much as last possible.


Between a & b, air gap is exists & we know that air gap offer reluctance to the flux [leakage]

Reluctance $\uparrow \rightarrow$ flux \downarrow [leakage] then leakage reactance \downarrow
lagging p.f will also \uparrow then p.f \downarrow .

In closed slot type between a & b, si-steel is exists, which offering high permeability. so it encourage the leakage so, leakage flux will be higher through the stator. & leakage reactance will be higher. due to this lagging p.f. will be low.

then p.f \uparrow .

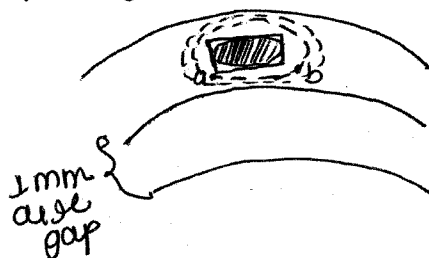

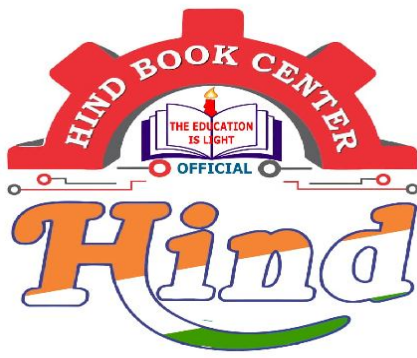

Hindbookcenter



Hind Book Center & Photostat


MADE EASY

**Electrical Engineering
Toppers Handwritten Notes
Synchronous Machine
By-Murli Sir**

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

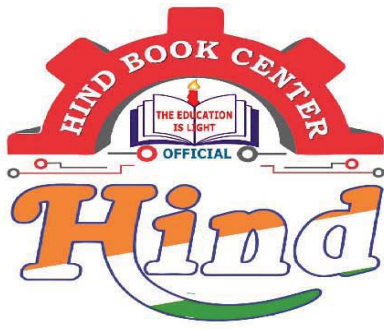**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393**



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS


HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

SYNCHRONOUS MACHINES

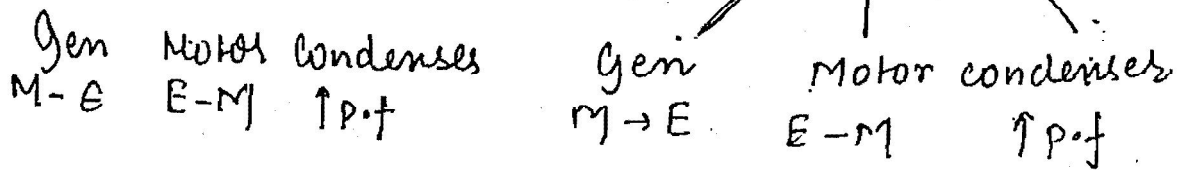

- Commonly used generator in Power Plants universally, also called as alternator as it generates ac voltage which is stepped up to much higher value and transmitted through X-lines.
- They run at a standard speed called as synchronous speed for given freq and No of poles
- These are doubly excited type because rotor is excited by dc supply as well as additional mechanical i/p is given across the rotor
- Principle of operation is according to Faraday Law.
- If a commutator is dropped from a dc generator and if two slip rings are used to collect it is a generator if it is rotated at synchronous speed it can be called as synchronous generator but with rotating armature and stationary field structures.
- In dc generator winding (armature should rotate) for commutator action. In alternators there is no such commutator therefore it is not necessary that the armature should be a rotating member; it can be either rotating or stationary.
- Small rating alternators < 5kVA only may have rotating armature but practically synchronous generators of large rating commonly contain

stationary armature rotating field structure.

Advantages of Stationary Armature:-

eg 500 MVA
11 kV

$$I = \frac{500 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 26243 \text{ A}$$

* Excit. Voltage is DC

125 - 500 V DC

1 MW power $I = \frac{1000000}{500} = 2000 \text{ A}$

1) Simple Design:- To collect large current from rotating part, becomes very complicated practically and expensive because (3+1) slip ring with HV insulation and high current carrying capacity.

2) Insulation is effective if armature is on stationary part:- Stationary slots will offer better insulation as well as they offer more space.

3) Efficient Cooling:- It is easy to provide air passage, cooling tubes, water/hydrogen cooling on a stationary part.

4) More O/P:- As the rotor is lighter in weight supports high speeds so for a given size it gives more O/P with more speed.

5) Right Construction:- As the winding is on stationary part it has more dynamic balance against electromagnetic stresses during S.C.

Due to more width of slot and teeth they are stronger.


- b) Leakage Reactance:- will be less because stator offers more width in the slots and contains more cu per slot. If it is on rotor depth will be high due to less space which produces more leakage reactance


CONSTRUCTION DETAILS:-

- Like all other rotating electric machines it contain stationary part Stator, Rotating part Rotor with an air gap.
- The stator basically contain core and windings, rotor contains poles and field winding.

STATOR:-

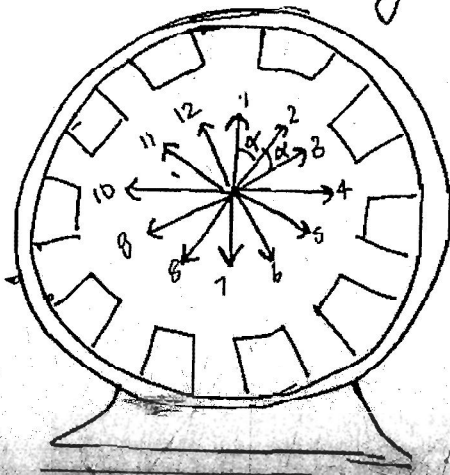- It contains an outer frame made up of cast iron or steel only for mechanical protection of the entire m/c there is a stator core made up of sheet steel (Si steel lam 0.5mm thickness) to produce least core losses.
- The stator core is punched into slots which are generally open type in practical synchronous m/c they contain 3- ϕ winding.



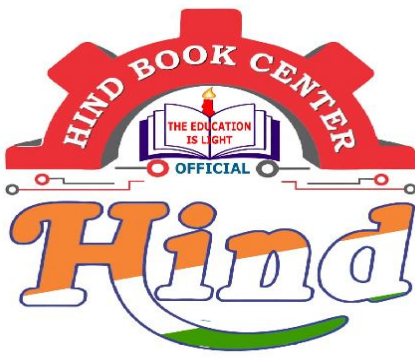

Hindbookcenter



Hind Book Center & Photostat


MADE EASY

**Electrical Engineering
Toppers Handwritten Notes
Transformer
By-Murli Sir**

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

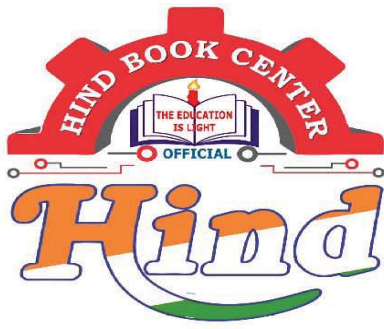**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393**



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

- TRANSFORMERS :-

Definition :

(i) Transformer is a static device which transfer AC electrical energy from one circuit to the another through the action of magnetic field.

key word :

Transfers AC electric energy - through magnetic field

circuit is generalised word for coil and winding.

A magnet is surrounded by magnetic field called flux. Flux is a life of a machine whether you take DC M/C, Induction M/C, synchronous M/C, transformer, these all are working on the flux only. So a machine work because of flux only.

All the electricity we get is through flux only.

A generator works because of flux & a motor rotates because of flux, a transformer transfer the power because of flux only.

(ii) Transformer^{mut} operate on the principle of mutual induction. b/w two or more magnetically coupled coils.


key word :- Mutual induction principle b/w two or more magnetically coupled circuits (coil/winding)

(iii) It transform AC electrical energy or power at one voltage level to another voltage level without the change in frequency & power

key word :- Transfer Electrical energy at one voltage level to another (at same F & P)

constant power means that the transformer have highest possible η in all electrical machinery/devices. Efficiency is almost 100% or in a well design transformer efficiency is close to 100%. i.e; if p power is equal to o/p power, the losses are very small & they can be neglected.

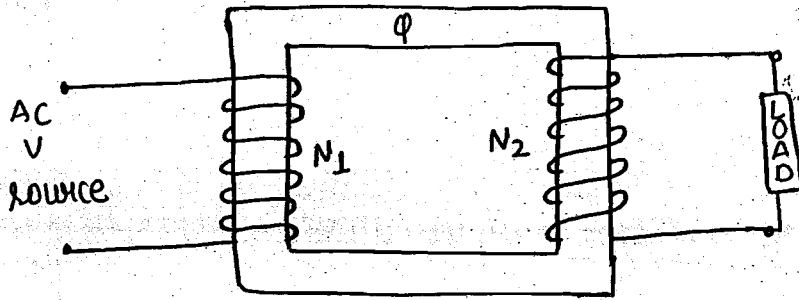(iv) magnetically coupled coils wound on common ferromagnetic core.



The connection b/w these two coils is due to the common flux in the common core. i.e; these two coils are magnetically coupled when we connect the AC power source then there will be flux in transformer. then it produce voltage in another side.

- The coil which is connected to the source is called IP winding or primary winding.
- the other winding where is load connected is called secondary or OP winding.
- If transformer having third winding then it is called as tertiary winding.
- one winding receive the power another one is delivering the power.

10 Aspects of transformer :

(i) static device i.e; no moving or rotating part, everything is stationary

Flux : stationary
conductor : stationary

(ii) Electromagnetic energy conversion device (Internally)
i.e; externally no energy conversion is occurs

IP is electrical → OP is electrical

Internally operation ⇒ Electrical → Magnetic field → Electrical

NOTE :- Transformer is not a electrical machine. It is a device. But we take like as a machine only.

Machine is a electromechanical energy conversion device.

i.e; Electrical ⇌ Mechanical

- (iii) It is singly excited device i.e; we applied voltage to only one winding of a transformer.
- (iv) constant flux device neglecting the transient change in flux.
- (v) constant power
- (vi) constant frequency
- (vii) Magnetically coupled circuits [-ve magnetic coupling in accordance to lenz's law]
- (viii) It is automatic control system [with negative feedback]
- (ix) It is phase shifting device [w.r.t. voltage]
- (x) It works only on AC

Classification of transformer :-

1. Based on No. of windings :-

If there is 1 winding \rightarrow Auto T/F

2 windings (primary & secondary)

3 windings (primary & secondary, tertiary)

2. Based on core construction :-

(a) core type transformer

(b) shell type transformer

3. Based on NO. of phases :-

(a) 1- ϕ T/F

Three 1- ϕ T/F are internally connected to 3- ϕ T/F bank.

(b) 3- ϕ T/F


4. Based on the operating frequency

(a) Power frequency T/F (25-500 Hz)

(b) Audio frequency T/F (20 Hz to 20 kHz)


5. Based on Application : Many Numerous kind of T/F

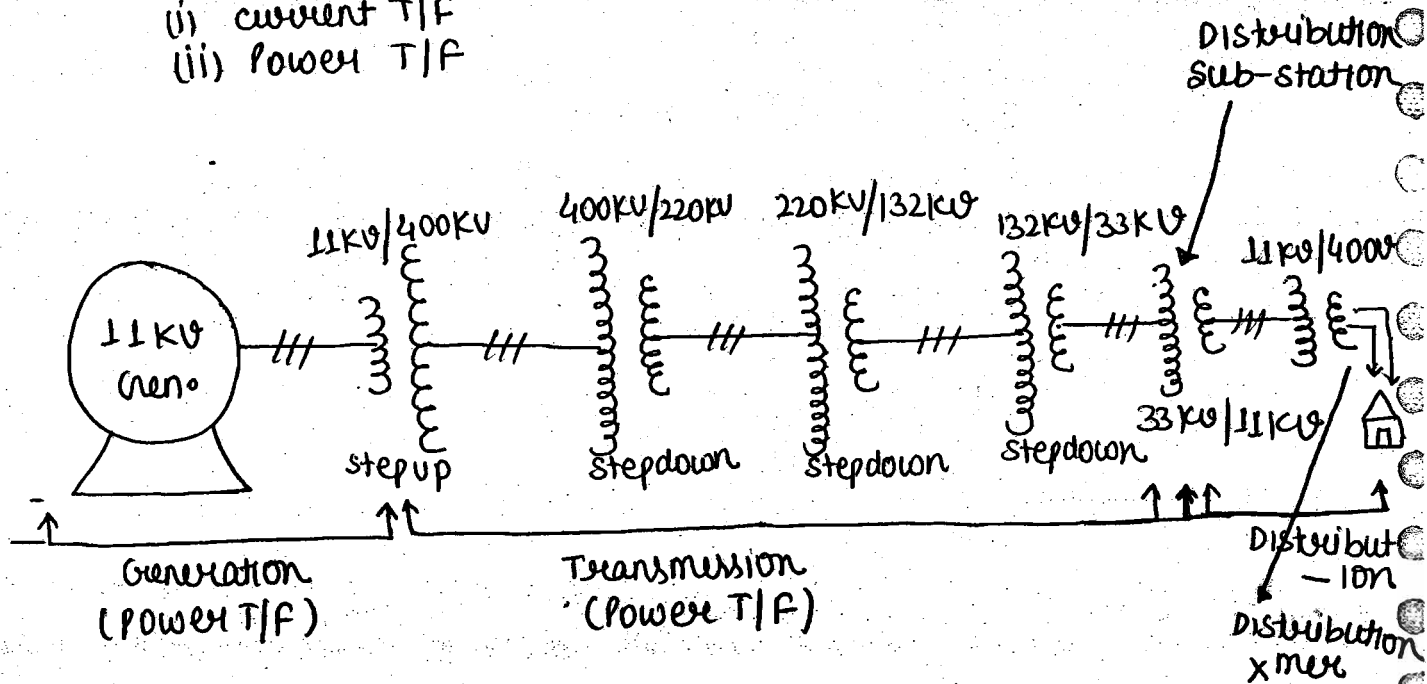- (a) Power system
 - (i) Power T/F
 - (ii) Distribution T/F
- (b) Power electronic
 - (i) Pulse T/F
 - (ii) Gate pulse triggering
- (c) Instrumentation
 - (i) current T/F
 - (ii) power T/F
- (d) Electronic & control system




NOTE:-

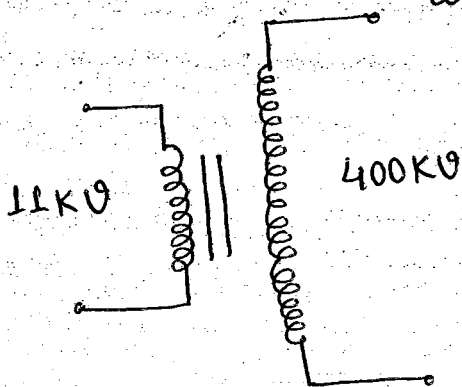Step up \longleftrightarrow Step down T/F
 can be used as



Step up mode : 11KV called primary winding.
 400KV called secondary winding.

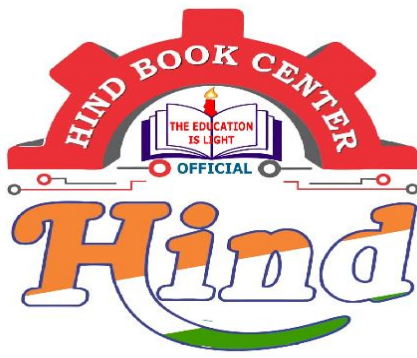Step down mode : 11KV called secondary winding
 400KV called primary winding.



Hindbookcenter



Hind Book Center & Photostat

MADE EASY

Electrical Engineering Toppers Handwritten Notes


D.C MACHINE

By-Murali Sir

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

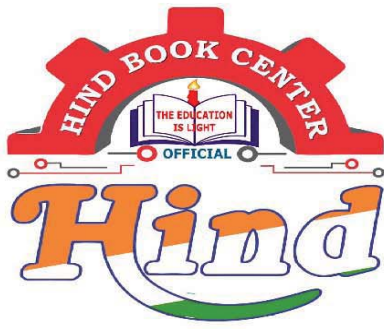Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--


Website: www.hindbookcenter.com

Contact Us: 9711475393

CHRISTIAN ØRSTED 1820 Electro magnetism :-


Relation b/w Electricity and magnetism

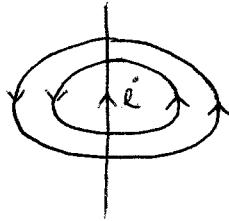There is magnetic field around a current carrying conductor



current carrying conductor producing concentric flux line [Right hand Thumb rule] By using R-H thumb rule fingers represent flux line direction and thumb in the current direction.

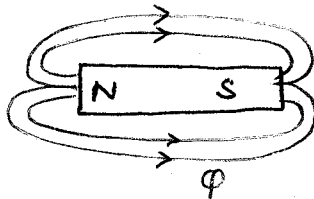Every electrical machine is working because of flux (Φ) unit-Weber



MICHAEL FARADAY (Father of Electricity) 1831 Electro Magnetic Induction :-

If current produce flux then why can't flux produce current?

NIKOLA TESLA 1880 RMF :- Rotating magnetic field

Induction & Synchronous machine is working on the basis of RMF
NIKOLA TESLA is behind AC power system.

ISSAC NEWTON 1687 Law's of motion



3rd law : Action \longrightarrow opposite reaction lenz law

The result always the opposes the cause of it.

- DC machine -

Electrical Machine :-

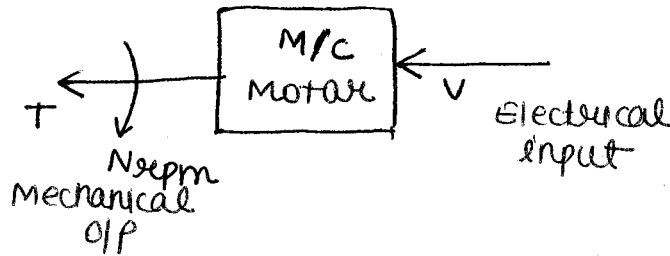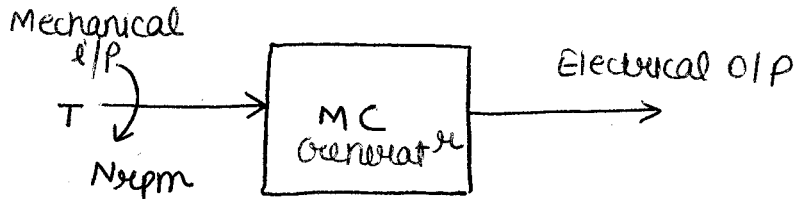Electro-Mechanical Energy conversion device




Electro mechanical : Reversible process [Pump storage Plant]

To maintain the load factor, under light load condition acting like motor as well as making the water go back for ready the dam for peak load condition acting as generator.

Generator :-

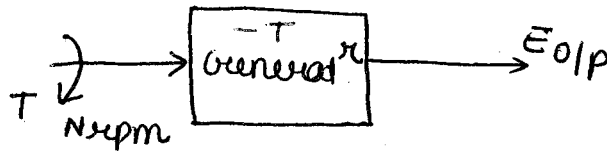we are supplying torque then generator is rotating in one direction, when the generator is giving electrical o/p then in the generator another torque is produce. so in the generator voltage is produced as well as torque is also produce this torque which is produce in generator is exactly oppose the torque what we are giving.



'-' sign denotes the opposite direction

Motor :- when m/c is working as motor, we are giving some voltage then in m/c another voltage is developed which is exactly opposite to supply voltage.



M/C $\begin{cases} \rightarrow G: V \ \& \ T \ \text{generated} \\ \rightarrow M: T \ \& \ V \ \text{generated} \end{cases}$

Energy is never generated, so, Generator can't generate any by itself unless we rotate the generator

When a m/c is acting like generator mode or motor mode two things are commonly happen (V & T) that's why DC mach can be used as motor as well as Generator

Transformer is NOT a electrical machine because there is no electro-mechanical energy conversion happens in it. In transformer more electro-magnetic conversion takes place internally.


DC Generator :-

construction details of DC generator is exactly similar to DC motor, difference in characteristic and application.

DC generator, is rotating electrical m/c which is designed to take the advantage of electromagnetic induction in order to convert mechanical energy into DC electrical energy.

Faraday's law of Electro magnetic Induction :-

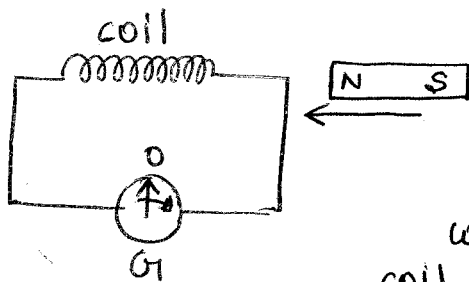The phenomenon of producing induced emf in a conductor through a change in magnetic field.



When the magnet is stationary then [near the coil] galvanometer is deflecting zero.

When the magnet is moved near to the coil or inside the coil then galvanometer is deflecting in one direction. If movement is fast then more deflection, if it is slow then less deflection. i.e; there will be change in the magnetic field due to movement now change in magnetic field is responsible to produce induced emf in the coil.


Whenever a conductor cuts a magnetic flux, a dynamically induced emf in the conductor

Fleming's law: The magnitude of induced emf is directly proportional to rate of change of flux linkages.

Flux: ϕ webers conductor: N Flux linkage $e(\lambda) = \phi \cdot N$

Flux linkage means the interaction between flux and conductor

\downarrow magnet \downarrow cu wire

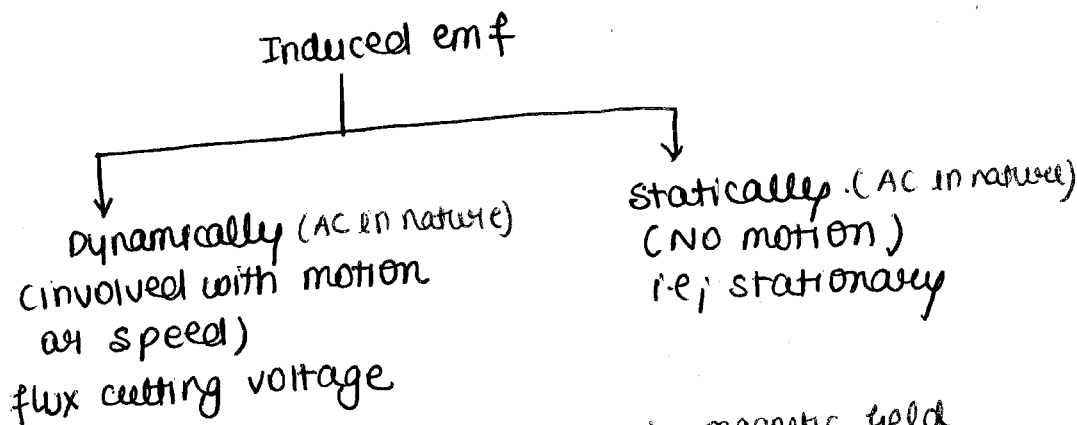


Flux:-

- (a) Time in varying flux | steady magnetic field
- (b) Time varying flux

In time in varying flux, the flux is not varying w.r.t time

Ex:- Permanent magnet

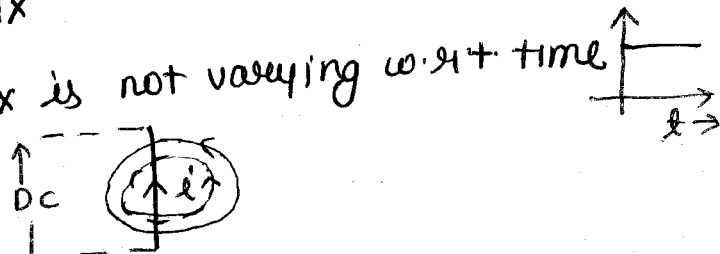

When we give ^{AC} supply to conductor then we get continuously time varying current which obviously produce time varying flux in it.

$$e = \frac{d\lambda}{dt} \text{ volts}$$

$$= \frac{d(N\phi)}{dt} = N \frac{d\phi}{dt}$$

$$e = N \frac{d\phi}{dt} \text{ volts}$$

$$e = -N \frac{d\phi}{dt} \text{ volts}$$

\downarrow - sign represent lenz's law

$$e = \overset{L}{N \frac{d\phi}{di}} \times \frac{di}{dt}$$

$$e = -L \frac{di}{dt} \text{ volts}$$

conductor behaves like inductor.

When there is rate of change of flux linkages conductor behaves as an inductor. Inductor will oppose the change in current. So to communicate the opposition factor we put negative sign. This negative sign doesn't represent any polarity or motion in DC M/C.


→ If the flux is time invariant in nature, it requires relative motion between flux and conductor for effective rate of change of flux linkages (one should rotate w.r.t. other)

→ If the flux is time varying then it automatically produces voltages with stationary conductor because of inherent rate of change (No need of relative motion)

Three mode of flux linking :-

① Flux : Flux is stationary and nature is time invariant.
 conductor : Rotating

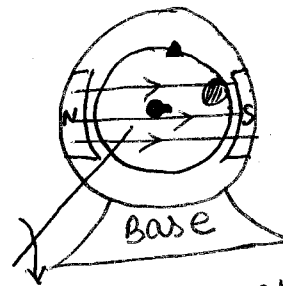magnet : stationary then flux will be stationary & having time invariant nature



Place a conductor on rotating part & don't rotate the rotating part then there is flux and conductor but missing the rate of change of flux linkage


If we want to create rate of change of flux linkage in time invariant flux then we require one should rotate w.r.t. other. i.e. either flux or conductor any one should rotate of flux linkage occurs produce induced emf. → rate of change

Ex: DC machine (Dynamically induced emf)

↳ Rotation is involved

② Flux : Flux is rotating and nature is Time invariant
 conductor : stationary

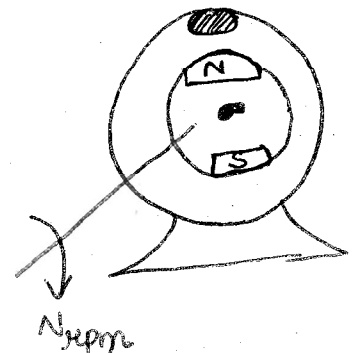In this when we start rotating then magnet is also rotate due to which flux is rotating but flux is time invariant only.




Rate of change of flux linkage occurs in conductor which produces dynamically induced emf.

Ex:- synchronous machines


To collect the current from stationary part is so easy.

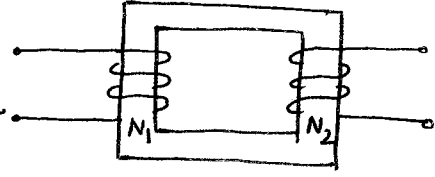(2) Flux: stationary & Time varying
conductor: stationary

DC voltage: $\rightarrow \phi$ & conductor



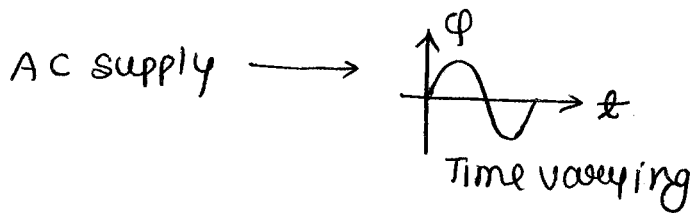is @ stationary there is no rate of change of flux linkage. never work on DC.



\rightarrow natural rate of change of flux linkage

\downarrow
enough to produce induced emf

Ex:- Transformer (Induction m/c is nothing but rotating x-mtr) (statically induced emf)





\rightarrow NO motion require

working of a simple loop generator:-

In order to produce induced emf in a conductor, require

- (a) Flux (b) conductor (c) prime mover According to FLEM

Rotate the conductor b/w magnetic field.

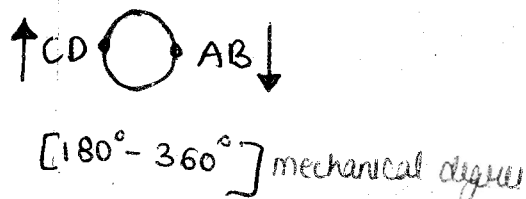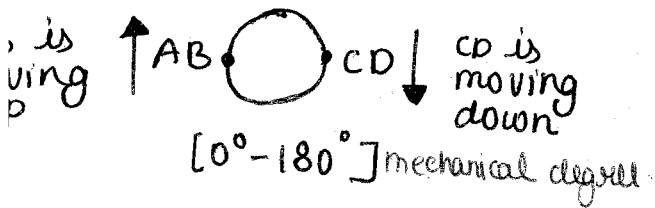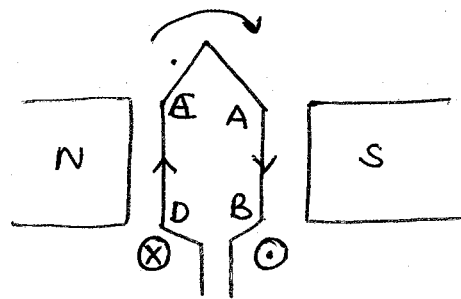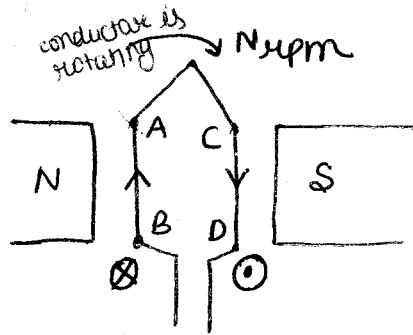

We use Fleming's right hand rule in order to know dynamically induced emf.


$$e = Blv \sin \theta$$

- B = flux density (Tesla)
- l = Active length of conductor
i.e., length who cut the flux
- v = peripheral velocity = $\frac{\pi DN}{60}$
- θ = angle between flux & conductor
- D = Diameter of armature


Fleming right hand's rule :-

Forefinger \rightarrow Flux Thumb \rightarrow Motion force

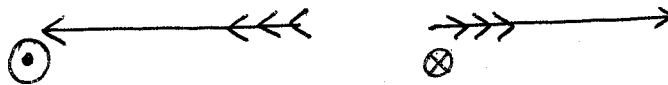
Middle finger \rightarrow Direction of current or induced voltage in conductor [To know]



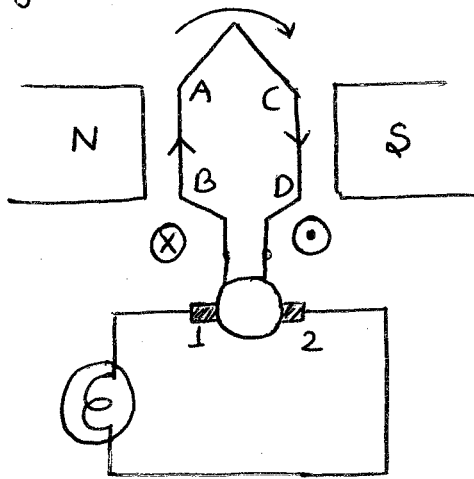When bulb is connecting to it then bulb is also get rotated which is problem for the designing purpose. For to be stationary the load we need idea which is sliding contact. But if we use one ring then it short circuit the coil.



So, we go for two ring concept

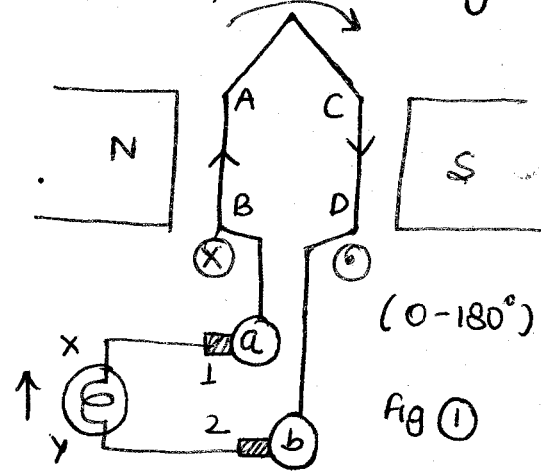

current direction \rightarrow \underline{BACD} $\underline{b2yxaB}$

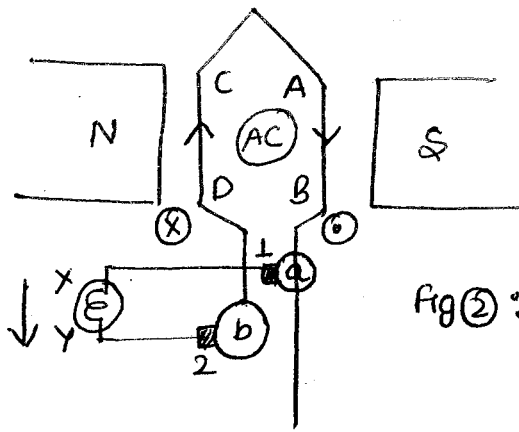


Fig 2:


current direction: \overrightarrow{DCABAD} \perp \overrightarrow{XY} $\overrightarrow{2bD}$
 Bidirectional current in coil i.e. AC

in the coil: AC

in the bulb: AC


i.e. this is AC generator.

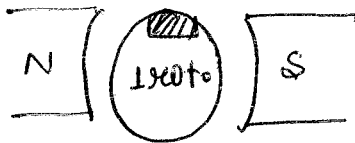AC is collected as AC when connect two ring or slip ring.





when conductors make one rotation then conductors will pass south pole and then also north pole. so, if south pole produce one pulse then north pole produce opposite. [There is no rule is south pole producing + or -ve & north pole producing +ve or -ve]

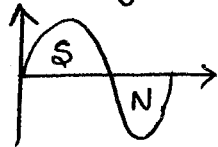one pulse then north pole produce opposite. [There is no rule is south pole producing + or -ve & north pole producing +ve or -ve]



with 2 pole: 1 cycle in one rotation

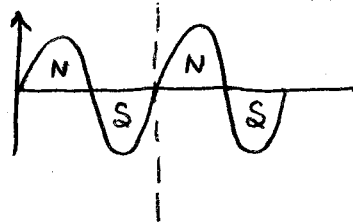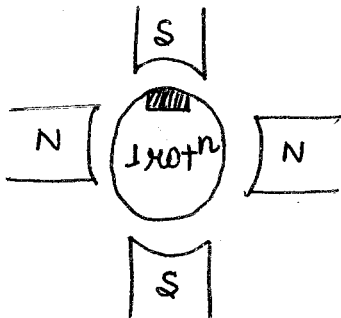

with 4 pole: 2 cycle in one rotation

with P pole: $P/2$ cycle/rotation

no. of cycles/rotation = $P/2$

no. of rotation/sec = $N/60$


N is in rpm.

$$\frac{\text{cycles}}{\text{rotation}} \times \frac{\text{rotation}}{\text{sec}} = \frac{P}{2} \times \frac{N}{60}$$

$$f = \frac{\text{cycle}}{\text{sec}} = \frac{PN}{120}$$

or

$$N = \frac{120f}{P}$$

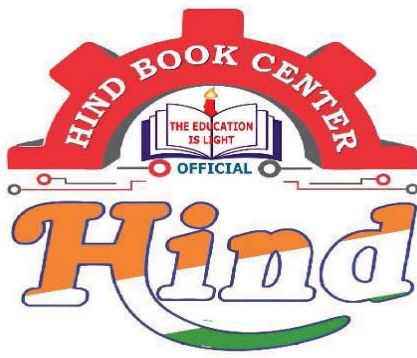

Hindbookcenter




Hind Book Center & Photostat

MADE EASY
Electrical Engineering
Toppers Handwritten Notes
13.POWER ELECTRONICS
BY- JAGDISH SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

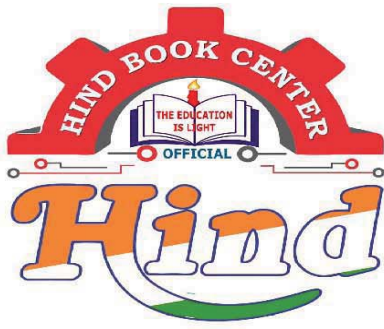Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Topics:

- (i) Power semiconductor devices
- (ii) phase controlled rectifiers (AC-DC) and Apple's charging battery DC drive solar cell

power semiconductor devices :-

- | | |
|----------------------|-------------|
| (i) Power diode | (vi) GTO |
| (ii) SCR (thyristor) | (vii) TRIAC |
| (iii) LASCR | (viii) DIAC |
| (iv) ASCR | |
| (v) RCT | |

power transistor ($f \uparrow$)

- ③ → power BJT
 - ① → power MOSFET
 - ② → IGBT
- ↳ switching frequency order

Cycloconv. $\Leftarrow AC \rightarrow DC \rightarrow DC \rightarrow AC$

Power electronics :-

Static V-I characteristics and firing/gating circuits for thyristor, MOSFET, IGBT; DC to DC conversion: Buck and Buck-Boost converters; single and three phase configuration of uncontrolled rectifiers; voltage and current commutated thyristor based converters; Bidirectional ac to dc voltage source converters; Magnitude and phase of line current harmonics for uncontrolled and thyristor based converters; Power factor and distortion factor of ac to dc converters; VSI, CSI, PWM.

Topics :

- (i) Power semiconductor devices
- * (ii) Phase controlled Rectifiers ($AC \rightleftharpoons DC$)
and application : charging Battery : DC drive
: Solar cell : HVDC

Solar energy can be stored in the form of DC system but our utility system are in AC system. so conversion is needed and this is possible by using phase controlled Rectifier. (converter).

Suppose we want to control the DC machine then phase controlled Rectifier is used.

- * (iii) Switched mode DC \rightarrow DC converters (choppers)
- * (iv) Switched mode DC \rightarrow AC converters (inverters)


(v) AC drive
only for ESE

(vi) Resonant converters

(vii) High frequency T/F and Inductors for PE Application.


(viii) SMPS

Power electronics :- ?

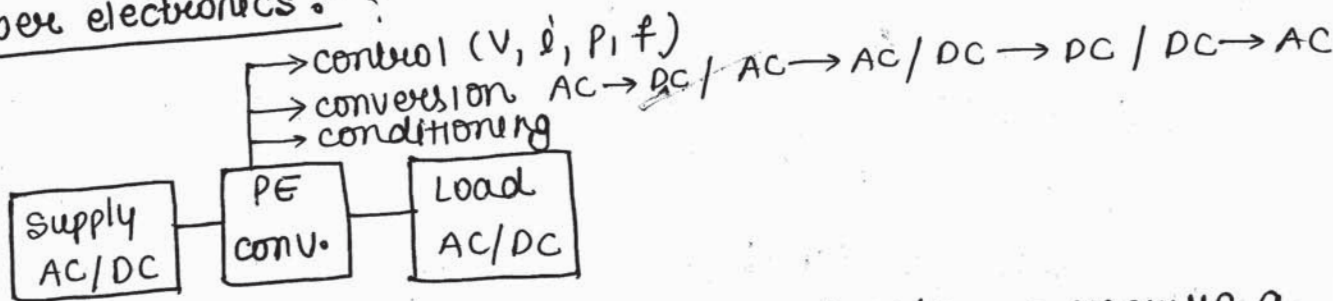


Due to the mismatching of power in both side we require a device which is known as power converters.

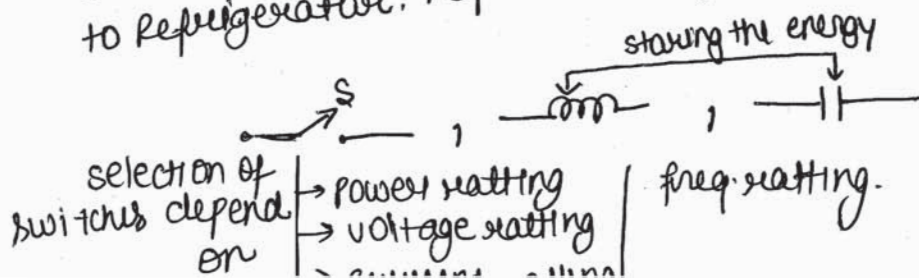Between the sensitive load & power supply we use power electronic converter so to minimize the voltage fluctuation. EX-: stabilizer to refrigerator. i.e; conditioning of electrical power



~~Not used~~
↳ Not used because power dissipation element.

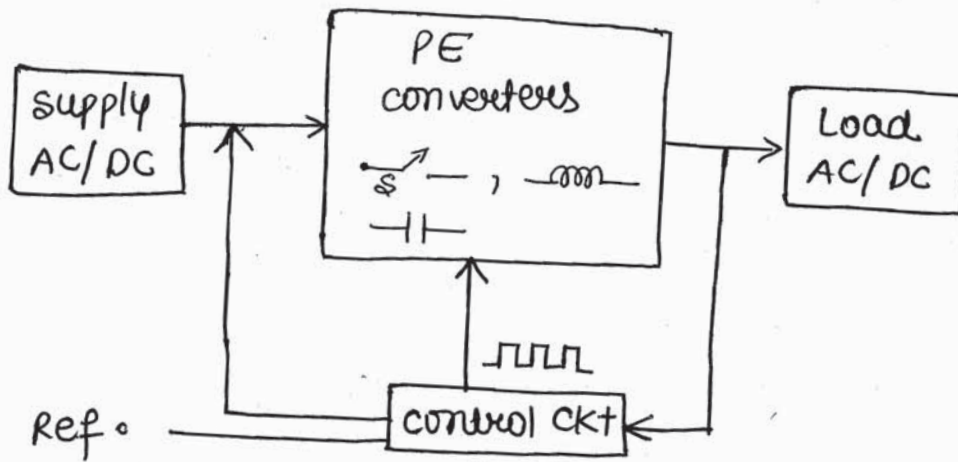(ON/OFF) control the switches we need control ckt and it is low power circuit or signal level ckt. here we can use resistive element.



Power electronic deals with control, conversion and conditioning of electric power using semiconductor devices & these SC devices should operate with high efficiency. In power electronic, semiconductor devices are mainly used as switches.

In this devices there will be two terminal Anode (A) & cathode (K). But some of the devices are also having Gate terminal also.

Suppose diode is only having two terminal Anode & cathode not having gate (G) terminal that's why diode is uncontrolled device.

cycloconverter : ω_0, ω_s
AC \rightarrow AC

High power & low speed
in drive

Semiconductor switches :-


(i) uncontrolled switch : (eg) $A \rightarrow \text{Diode} \rightarrow K$, DIAC

In the diode device there is no gate terminal so the ON/OFF state of diode will not decide then who decide the ON/OFF state of device? Nature of the ckt will decide it.

(ii) semicontrolled switch : (eg) $A \rightarrow \text{SCR} \rightarrow K$, TRIAC

In SCR, the anode & cathode terminal is connected to the supply & load respectively & Gate terminal is only decide the ON state but we can not decide the turn OFF time by using Gate terminal.

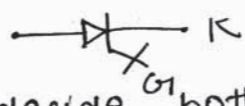(iii) Fully controlled switches: (eg) GTO




Gate is controlled terminal which decide both ON & OFF state.

when we give $+I_g$ to gate terminal then GTO \equiv ON

$-I_g$ to gate terminal then GTO \equiv OFF

(eg) BJT, MOSFET, IGBT


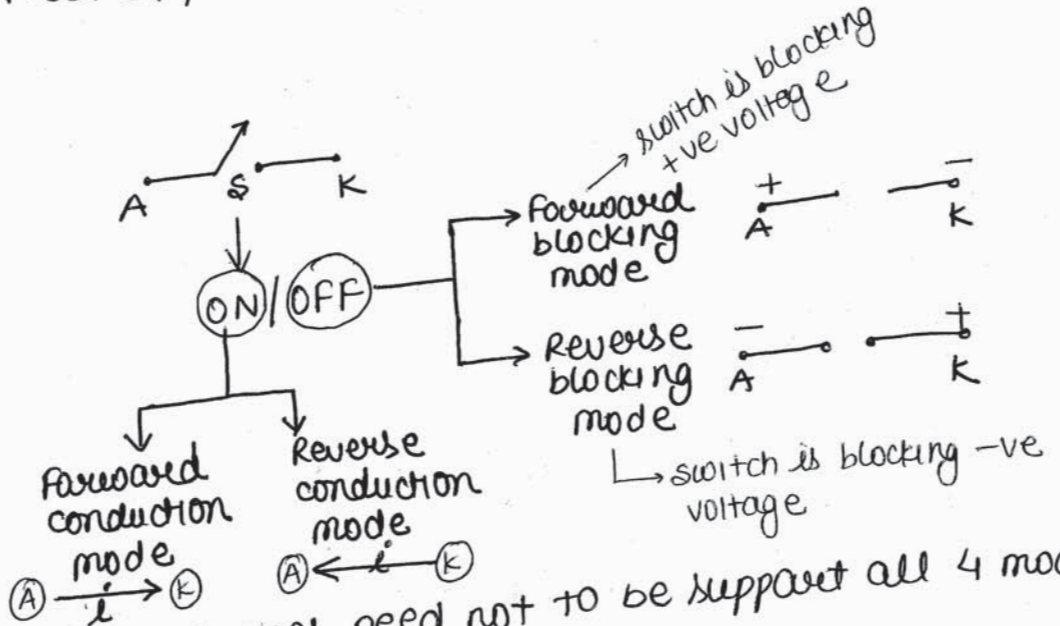


NOTE:-


All the semiconductor devices need not to be support all 4 mode.

Eg:-


Diode

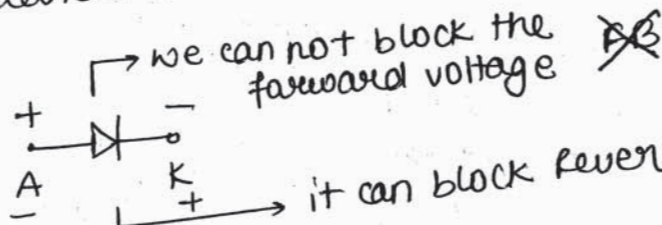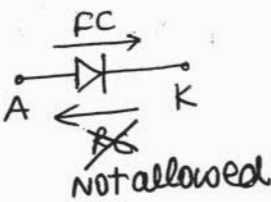

SCR

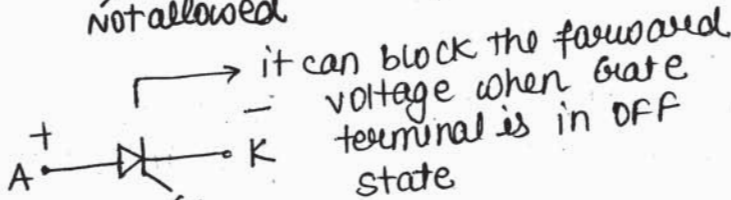


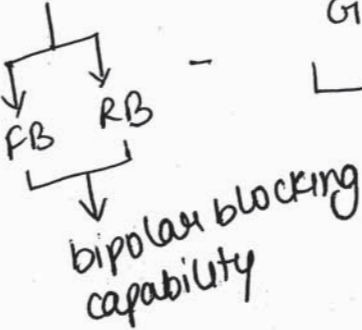
it can block the reverse voltage also when Gate=0 & current direction is only one way.



Diode	SCR
FC, RB	FB, RB, FC bipolar blocking with unidirectional current

Four - mode of an ideal switch :-

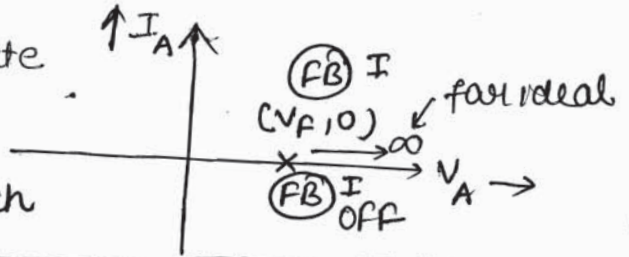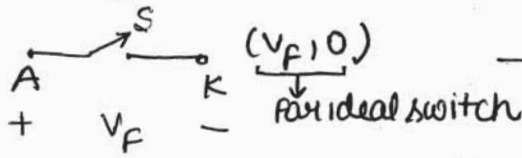
(i) Forward blocking mode : i.e., OFF state




An ideal device when blocking the forward voltage (V_F) then current passing through the device is zero Amp but in practical some leakage current flow through it due to minority current now, we are having some losses in semiconductor device even in the OFF state i.e., blocking power loss = $[V_F \times I_{leakage}]$. If it is ideal switch then it can block ∞ voltage through it. But practically it is not possible to apply ∞ voltage across it.

voltage rating : that much maximum voltage semiconductor device can block. [withstand in blocking state]

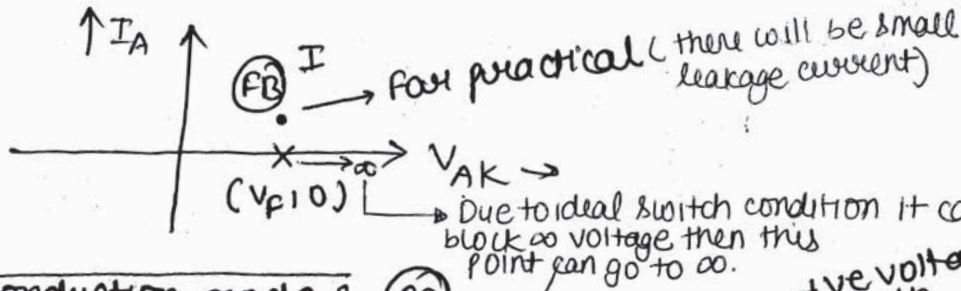
x \rightarrow ideal
o \rightarrow practical



(ii) Forward conduction mode : (FC)

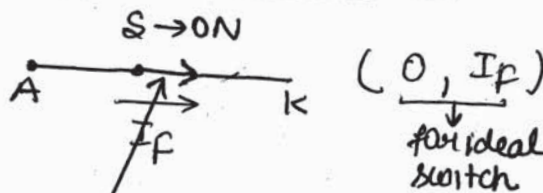

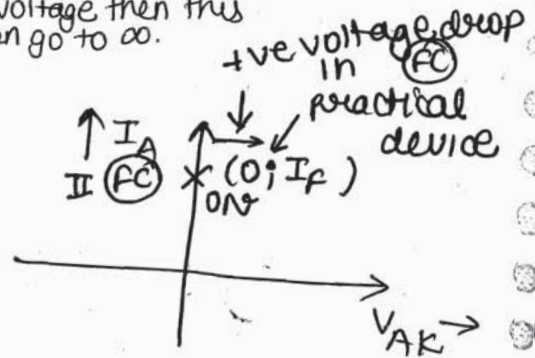voltage drop in practical case there will be conduction loss in the device
 $= (V\text{-drop}) \times I_F$





major loss among all three losses

Switching power loss : The variation of current & voltage from (FB) mode to (FC) mode there will be loss in it which is known as switching power loss.



It is depend on the switching frequency of switch (f) if

$f \uparrow$ then switching power loss \uparrow

(iii) Reverse blocking mode (RB):-

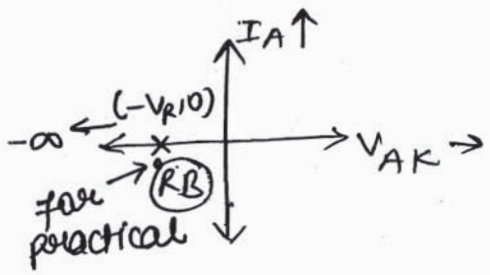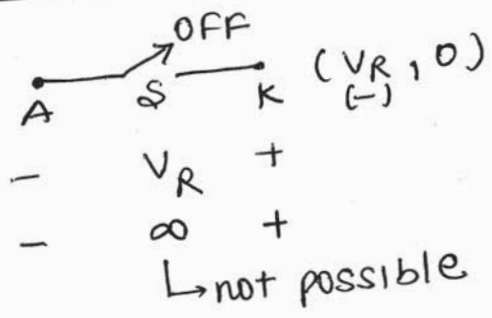





(iv) Reverse conduction mode (RC)

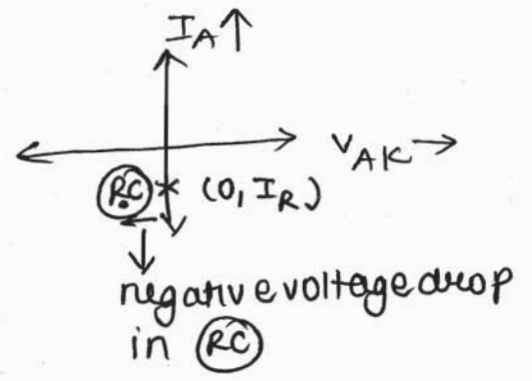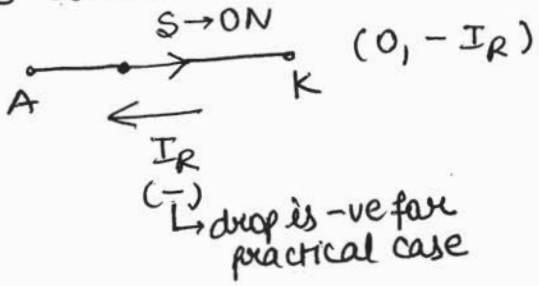

TRIAC supports all the 4 modes


AC \rightarrow AC converter
 in these converter we use that switch which support all the 4 modes.

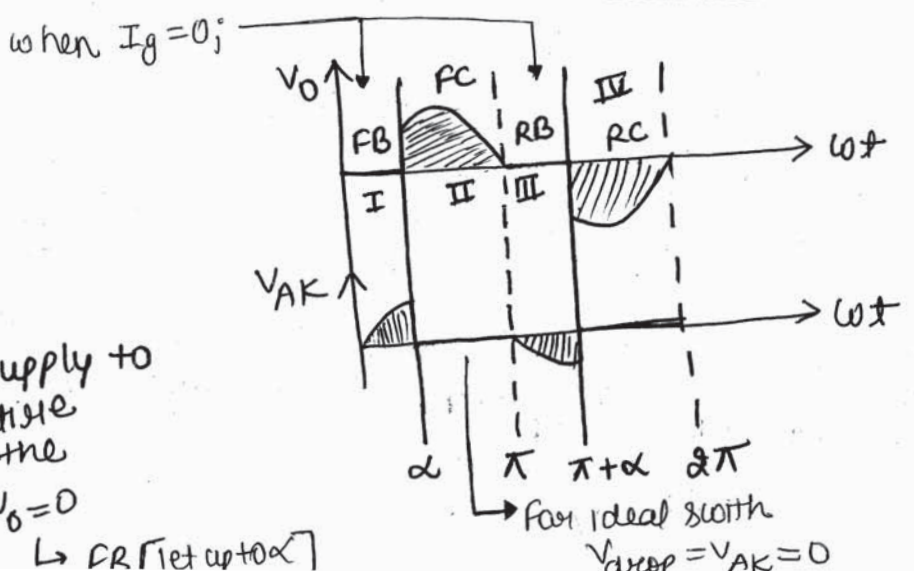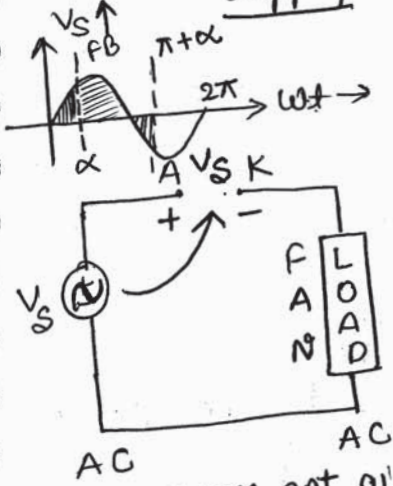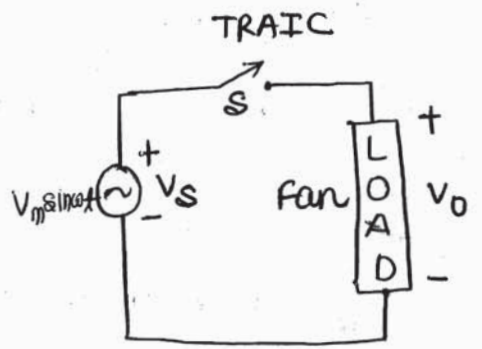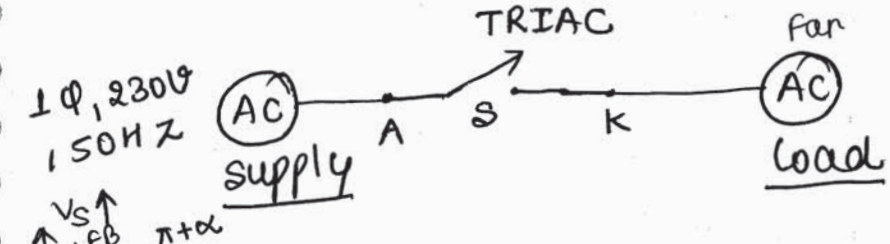eg) controlling the fan speed by regulator i.e; controlling the voltage V_{ac} without disturbing the frequency.




when we are not giving supply to gate terminal + Then entire voltage appear across the switch. ($V_{AK} = V_s$) & $V_o = 0$
 \hookrightarrow FR [et $\omega t > \alpha$]

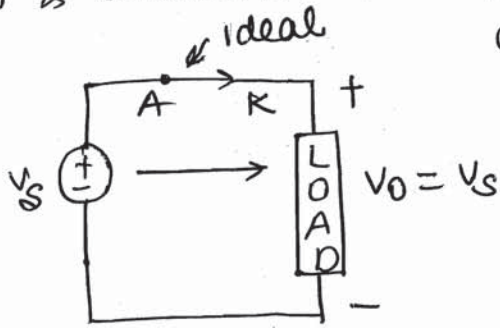II mode -> Giving Gate signal to the TRIAC then TRIAC will turn ON & conduction in the forward direction




entire supply voltage appears across the load.

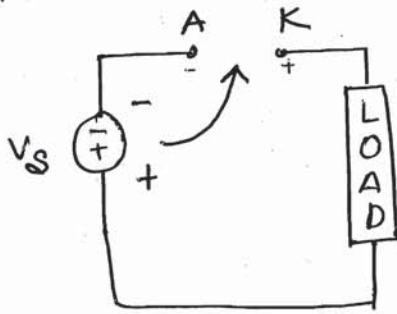III mode -> Now the supply voltage is reverse (-ve) again it blocking the reverse voltage because did not give gate signal to TRIAC. Then entire -ve voltage appear across the device.



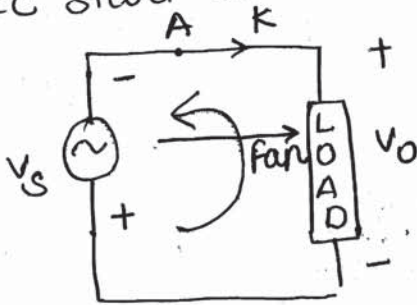IV mode -> Now, giving $-I_g$ (negative pulse) signal to the TRIAC the TRIAC start conduction in reverse direction negative voltage appear across the load.




Tell me how do we vary the voltage?

→ AC voltage is measure in the form of RMS voltage value

how do we control the RMS value.

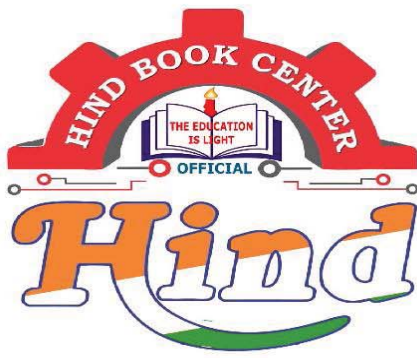control the both area ^{vogaph} symmetrically to eliminate the dc component. (or) area of both must be equal in order to eliminate the dc component. How much time we block the positive voltage same time we must block negative voltage so that both area should equal. Make sure that in AC side; DC component is always eliminated.



Hindbookcenter



Hind Book Center & Photostat

MADE EASY

Electrical Engineering

Toppers Handwritten Notes

14.MEASUREMENT & INSTRUMENTATION


BY- BALAJI SIR

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

Courier Facility All Over India
(DTDC & INDIA POST)

Mob-9711475393

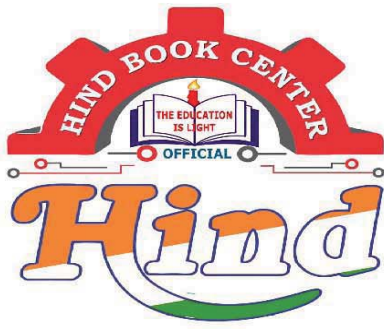

Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Electrical & Electronic Measurement & Instrumentation

Electrical (WATE + IES)

- Measurement of V
- Measurement of I
- Measurement of P
- Measurement of P.F
- Measurement of Energy
- (R, L, C) Resistance, inductance and capacitance
- Potentiometer
- Instrument transformer

Electronics (WATE + IES)

- Φ -Meter
- Digital meter
- CRO
- Error Analysis


Instrumentation (IES)

- Measurement of non electrical quantities like temp, pressure, flow
- Data acquisition system

Books


- (1) A.K. Sawney (Shawney)
- (2) Holding
- (3) Cooper

Thermal power plant

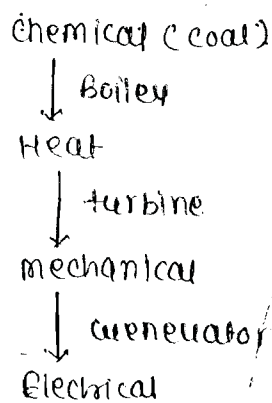

Principle - Rankine cycle.
(Reheating of steam)

- * DM - Demineralize water (Base)
- * CEP = Condensate extraction pump
- * BFP = highest temp raising pump
- * HPH = High pressure heater (step by step temp ↑ing)
- * When coal fire temp around 1200°C .
- * ECO = Economiser which takes water in 120°C and give it in 300°C .
- * BFP = Boiler feed pump
- * Inside drum there is a mechanism called turboseparator which separate water and steam.
- * HPSH = High temperature super heater (steam will pass & its temperature to 540°C)
- * HPGV = High pressure governing valve, IPGV = Intermediate pressure governing valve
- * I.T.S.H = Intermediate temperature super heater
- * ESP = electrostatic precipitation
- * ESP = collection of air particle
- * ID Fan (Induced fan) - taking flue gases from boiler.
- * for sending coal into boiler moisture has to be removed so for this we use air pre heater (APH) (moisture absorbed by hot air)
- * Transportation cost is very high for thermal plant.
- * BFP - highest pressure pump
- * Separator = remove dissolved gases
- for improving thermal of economiser is used.
- * FD fans = sending oxygen to boiler for proper combustion
(it will take atmospheric air used for proper combustion)
- * HW = Hot water

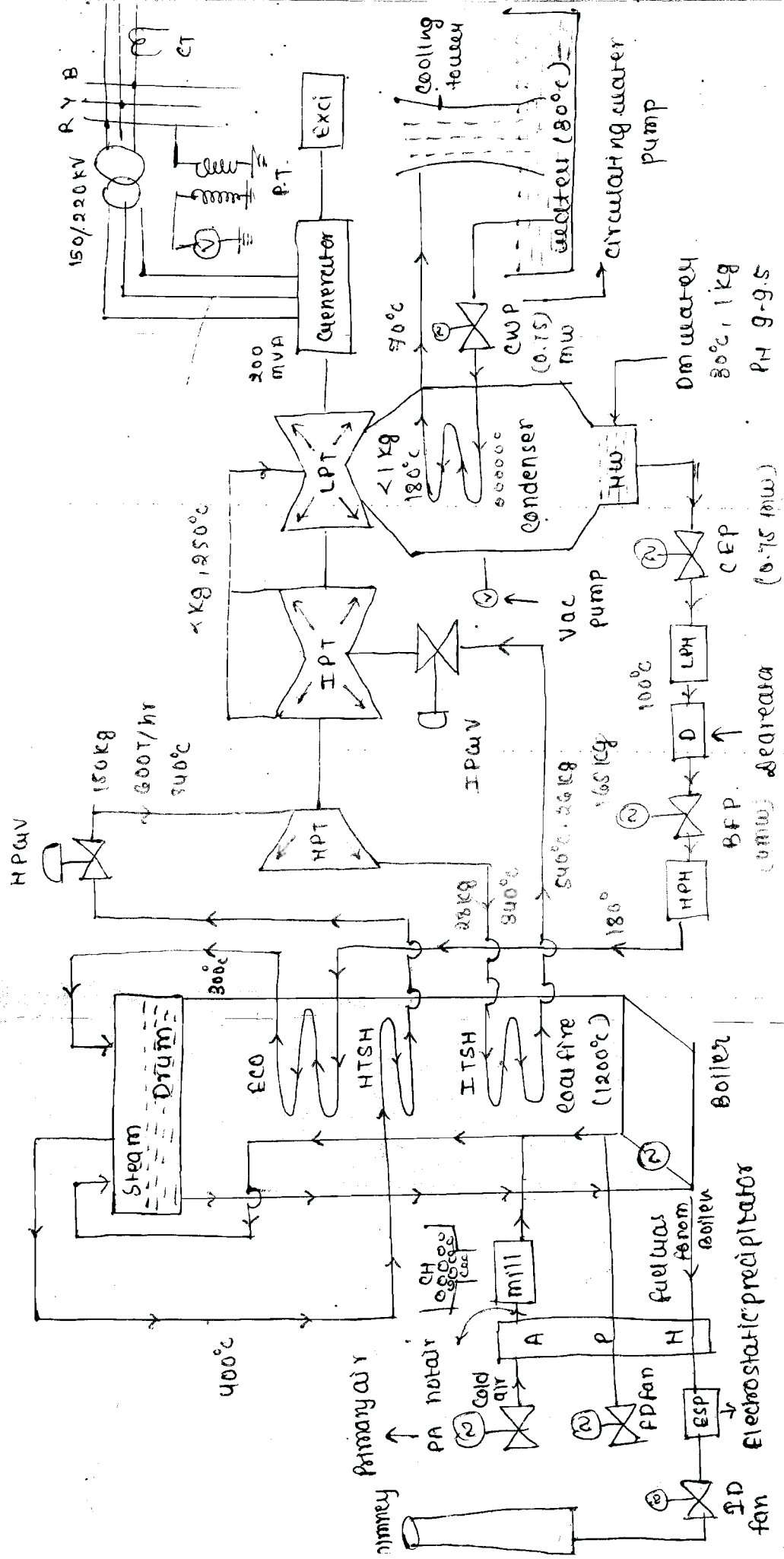

$$\eta_{\text{thermal}} = 40-45\%$$

$$= \eta_B \times \eta_i \times \eta_{\text{ch}}$$

\downarrow \downarrow \downarrow
 90% 30-40% 90%

now η due to condence heat loss

Bituminous coal used

Coal chemical / heat Energy

$$= \text{calorific value} \Rightarrow C_p \Rightarrow \text{kcal}$$

$$860 \text{ kcal Heat energy} \\ = 1 \text{ kWhr elec energy}$$

Peahtical

$$\eta_{\text{thermal}} = 40\%$$

Bituminous coal : $C_p = 1720 \text{ kcal / kg}$

$$1 \text{ kg} = \frac{1720}{860} \times 0.4 = 0.8 \text{ kw-hr}$$

$$1 \text{ kw-hr} = \frac{1}{0.8} = 1.25 \text{ kg cal}$$

Generator - 200 mw , 1 day - 24 hrs

$$\text{coal/day} = 200 \times 10^3 \text{ kw} \times 24 \text{ hrs} \times 1.25 \text{ kg}$$

$$= 6000 \times 10^3 \text{ kg} = 6000 \text{ T/day}$$


(1) C_p in kcal/kg

$$Q = \frac{P_{\text{avg}} \times T \times 860}{n_0 \times C_p}$$

2) C_p is kw-hr/kg

$$Q = \frac{P_{\text{avg}} \times T}{n_0 \times C_p}$$

Analog meter

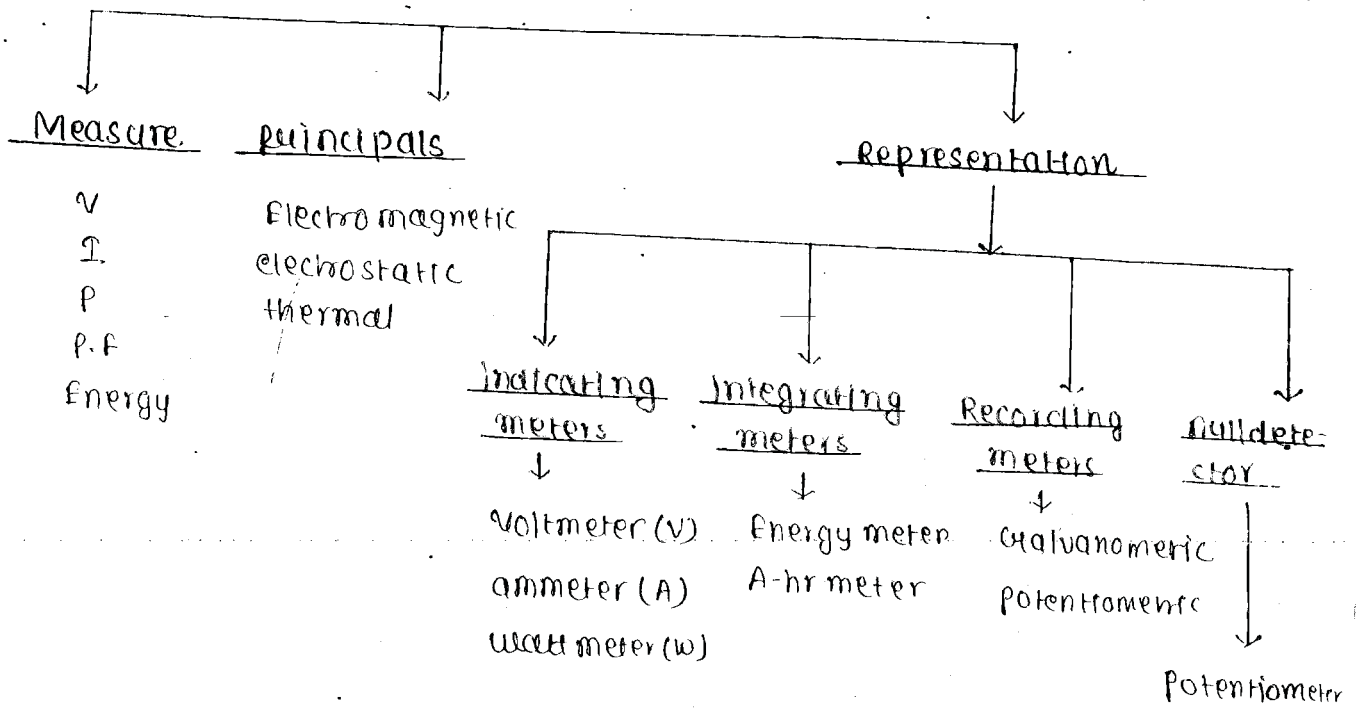


Order of the Meter

the instrument or meter should behave similar to the quantity to be measured (measurand)

Zero order instrument - when i/p changing o/p following the i/p immediately called zero order (0 time delay)

Potentiometer

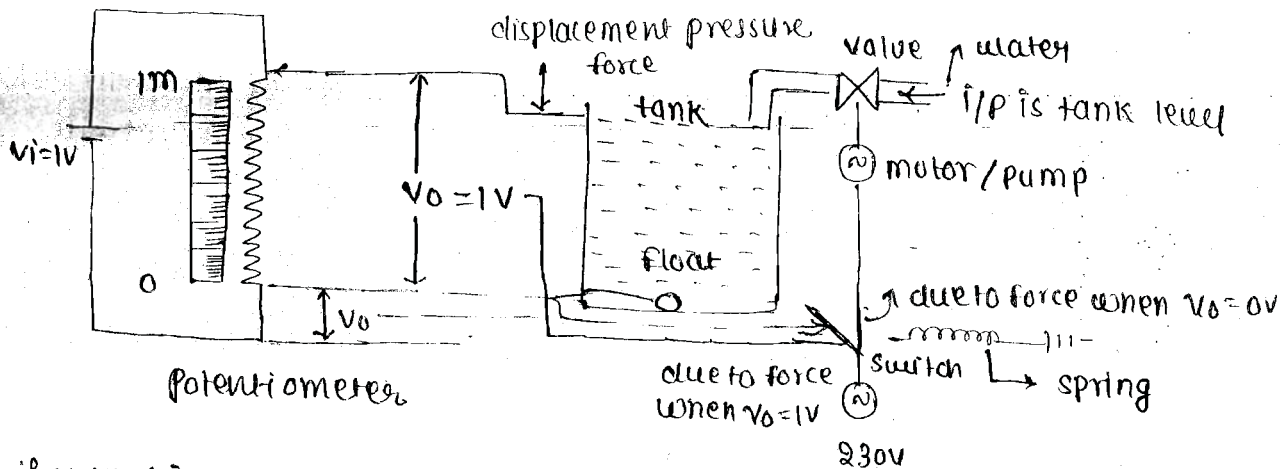

if output is proportional i/p and the o/p is changing at the same instant of i/p is changing without any time lag and time delay is called zero order system

ex. potentiometer


when tank level is full so current will flow creates magnetic field there for switch comes to open position

and when $V_o = 0V$ and motor/pump = 0 as it will experience force

1 m = 1 volt

100 cm = 1 volt


1 cm = 0.01 volt

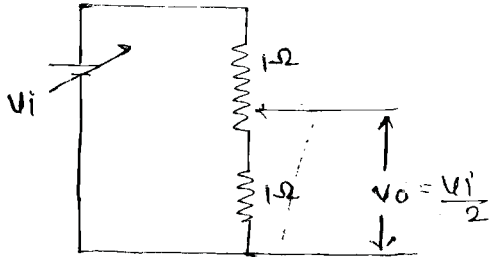


$$T(s) = \frac{V_o}{V_i} = \frac{1}{2} = K$$

= Constant

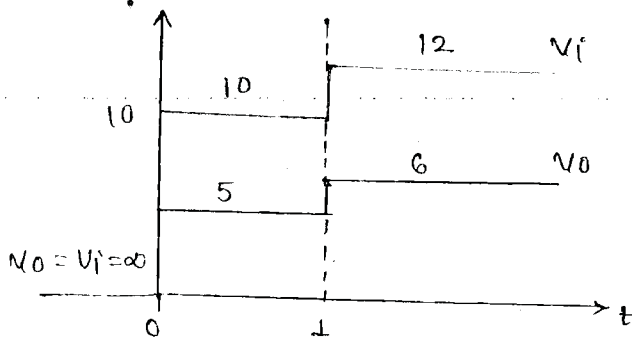$\frac{C(s)}{R(s)} = K = \text{constant}$



Practical potentiometer

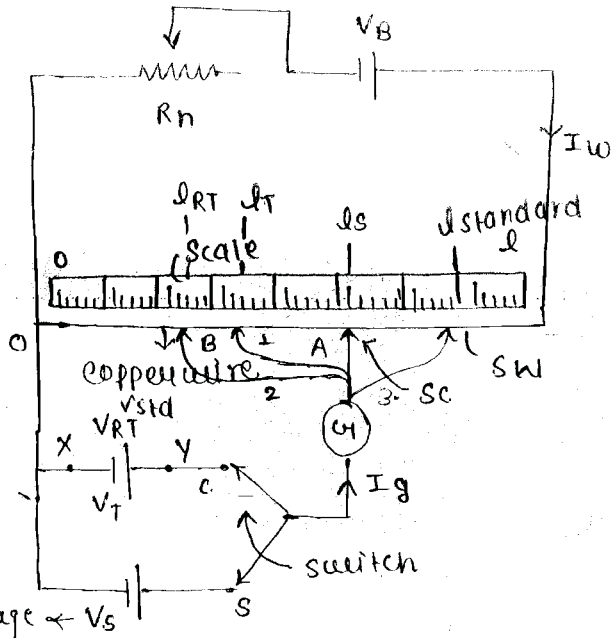

V_B = External Battery

R_h = Rheostat

I_w = working current

l = length of slide wire (m)

ρ = Resistance of slide wire (Ω/m)

ρl = total resistance of slide wire (Ω)

S_w = slide wire

S_c = sliding contact / jockey

G = Galvanometer

S = standardization

C = calibration

V_s = standard voltage source

V_T = test voltage

(Daniel cell)

standards voltage $\leftarrow V_s$

Convert centimeter scale into voltage called standardisation

Once standardize never change working current

Put galvanometer to make $I_g = 0$

then move the switch to C so V_T will draw some current $I_g \neq 0$ then will move jockey to some value where $I_g = 0$ not disturb in circuit

Application

1. Measurement of V_T :

$$I_w = \frac{V_B}{R_h + l_r}$$

Switch at S

$$I_w (l_s r) = V_S$$

$$I_w = \frac{V_S}{l_s r} \quad \text{--- (1)}$$

Switch at C

$$I_w (l_T r) = V_T$$

$$I_w = \frac{V_T}{l_T r} \quad \text{--- (2)}$$

$$(1) = (2)$$

$$\frac{V_S}{l_s r} = \frac{V_T}{l_T r}$$

$$\frac{V_S}{l_s} = \frac{V_T}{l_T}$$

l_s = length of switch at which V_S is balanced

l_T = length of switch at which V_T is balanced

balanced condition means making $P_g = 0$



will take reading when $P_g = 0$ or null therefore potentiometer is called null detector

2. Measurement of low Resistance ($< 1 \Omega$)


Classification of R

- (1) low R — $R < 1 \Omega$ — T/F, (G), (M) winding
- (2) medium R — $1 \Omega \leq R \leq 100 k\Omega$ — Heater, iron box, electronic equipments
- (3) High R — $R > 100 k\Omega$ — insulation cable, (M), (G), T/F

Representation

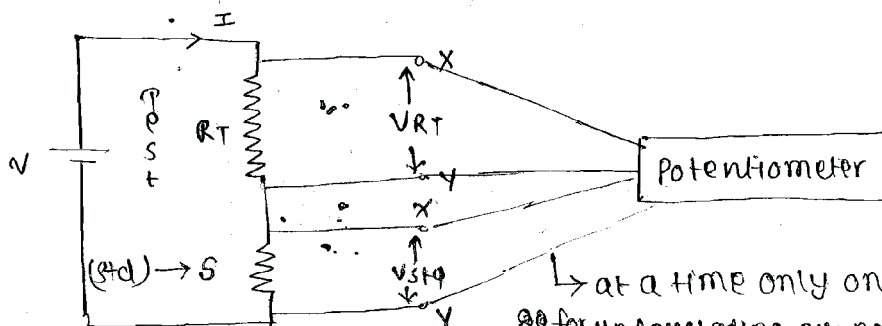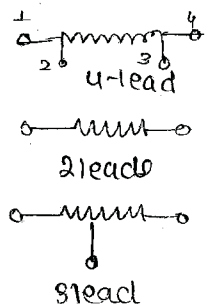

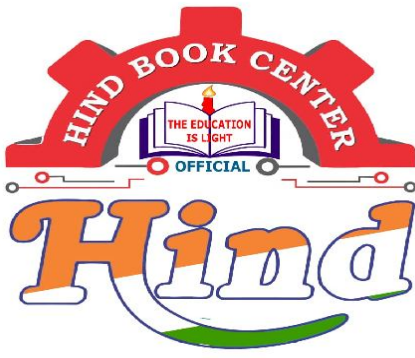at a time only one X-Y connectⁿ is there
 for understanding purpose I have shown both



Hindbookcenter



Hind Book Center & Photostat

MADE EASY

Mechanical Engineering

Toppers Handwritten Notes


General English

By- Sapna Maim

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding, & Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT
- All Notes Available & All Book Available
- Best Quality Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrance Exams

Visit us:-www.hindbookcenter.com

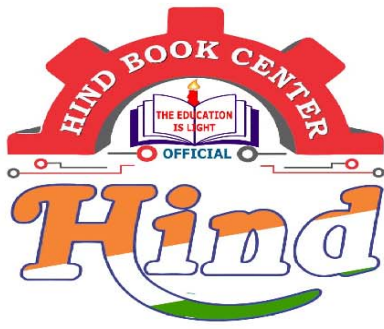Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

ENGLISH

Sapna

gate
o

Critical Reasoning
Inferential Reasoning
Logical deduction


Ludhani.Sapna@gmail.com
9911629948

Parajumbles

Reading Comprehension


gate
o

Vocabulary

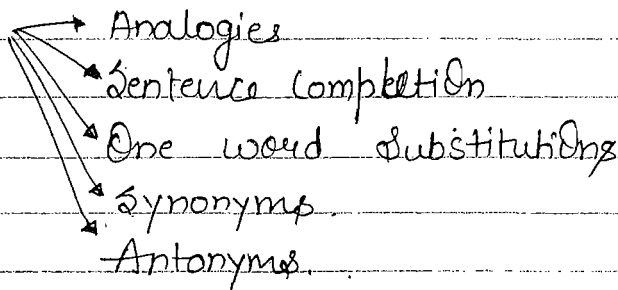

gate
o

Grammar

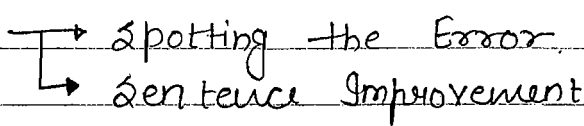

Analogy { Relationship }

Gladiator

Q. Gladiator : Arena
(warrior) (Platform)

a) Dance : Stage

b) Commuter : train

c) Teacher : Classroom

d) ✓ Lawyer : Courtroom

a) performer

b) fighter

c) opponent

d) End result $\begin{cases} \text{win} \\ \text{lose} \end{cases}$
(Traveler - Commutator)

Q. Frequency [Antonym ?]

a) Periodicity

✓ b) Rarity

c) Gradualness

d) persistence (continuity) Perseverance

↳ continuous determination

Q. Children : Pediatrician
(child specialist)

a) Adult : Orthopaedist (Bone specialist)

✓ b) females : Gynaecologist (female specialist)

c) Kidney : Nephrologist (deal with kidney & urine)

d) Skin : Dermatologist (deal with skin)

Q. Nocturnal : Bat
(active at night)

✓ a) Amphibian : frog \rightarrow Stay land & water

b) Sly : cat \rightarrow cunning (deceitful)

c) Carnivorous : cow \rightarrow eating flesh

d) Aquatic : liz.
↳ Lizard.

(live in water).

5. Xenophobia : foreigners.
Fear of foreigners & strangers

least
(~~most~~ similar)

a) Bibliophobia : Books

b) Anglophobia : English

c) Hemophobia : Blood

vd) Claustrophobia : Height (fear of height is Acrophobia)
(fear of confined or closed spaces)
or Constricted place.

Phobia

↓
fear

Mania

↓
obsession,
(craze)

Vibrant (full of happiness, Energy)

~~Charming~~
~~depressed~~

Clumsy

↓
◦ dirty, unpleasant
◦ unskilled

Synonyms

Antonyms

◦ Lively

◦ Vivacious

◦ Vigorous

◦ Enthusiastic

◦ Energetic

◦ Passionate

◦ Zealous

◦ Zestful

◦ Exuberant

◦ Active

◦ Lazy

◦ Lethargic

◦ Sluggish

↳ Slow & Inactive

◦ Dormant

◦ Indolent


◦ Dizzy

◦ Drowsy
↳ Sleepy

◦ Lethargical

Fatigue

↳ tiredness

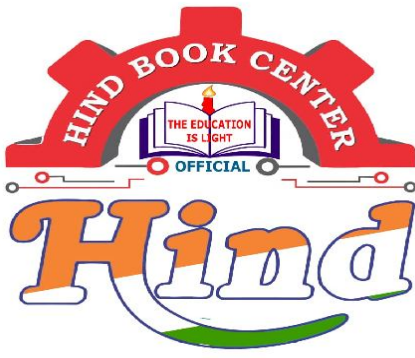

Hindbookcenter



Hind Book Center & Photostat

MADE EASY

IES/GATE/PSUs

Toppers Handwritten Notes


REASONING AND APTITUDE

By-Dheeraj Parasar Sir

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

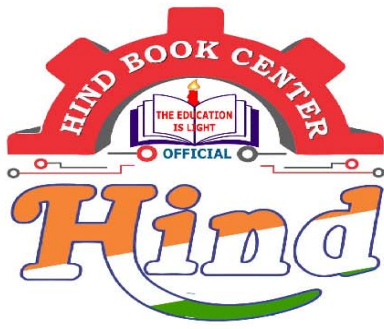Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

* NUMBER SYSTEM:

- V → Vinculum (BAR)
- B → Bracket. {}
- O → of.
- D → Division. (÷)
- M → Multiplication (x)
- A → Addition. (+)
- S → Subtraction (-)

Q1) Convert the following recurring terms into their corresponding P/Q forms?

a) $27.\overline{17}$
 ↓
 Complete Bar

$27.171717\dots$

(Bar immediately after point).

b) $27.2\overline{17}$
 ↓
 Partial Bar

$27.21717\dots$

c) $0.00\overline{17}$
 ↓
 Partial Bar

$0.00171717\dots$

Soln. a) $27.\overline{17}$

$x = 27.171717\dots$
 $100x = 2717.1717\dots$

$100x - x = 2717.1717\dots - 27.1717\dots$
 $99x = 2690$

$x = \frac{2690}{99}$

SHORTCUT

$x = 27.\overline{17}$
 $P/Q = \frac{2717 - 27}{99}$
 $= \frac{2690}{99}$

b) $27.2\overline{17}$

$x = 27.21717\dots$

$\frac{P}{Q} = \frac{27217 - 272}{990}$

$\frac{P}{Q} = \frac{26945}{990}$

c) $0.00\overline{17}$

$\frac{P}{Q} = \frac{00017 - 000}{9900}$

$\frac{P}{Q} = \frac{17}{9900}$

Q2) $27 \cdot 27 \times 33 + 6$

Soln: $\frac{(2727 - 27)}{443} \times 33 + 6$

$= \frac{2700 \times 33}{3} + 6$
 $= 300 \cdot 906$

Q3) What is the unit's digit in the expansion of $(766)^{136}$.

Soln: a) $(766)^{136}$ ← Based on cyclicity or power cycle →

- b) $(277)^{134}$
- c) $(454)^{41}$
- d) $(888)^{103}$
- e) $(1028)^{100}$
- f) $(459)^{40}$

- $0^N = 0$
- $1^N = 1$
- $2^N =$
- $2^1 = 2$
- $2^2 = 4$
- $2^3 = 8$
- $2^4 = 16$
- $2^5 = 32$
- $2^6 = 64$
- $2^7 = 128$
- $2^8 = 256$
- $2^9 = 512$

→ cyclicity of 2^N is 4 ie 2, 4, 8, 6

3^N ← cyclicity is 4 ie (3, 9, 7, 1)

- $3^1 = 3$
- $3^2 = 9$
- $3^3 = 27$
- $3^4 = 81$
- $3^5 = 243$
- $3^6 = 729$
- 3^7

4^N ← cyclicity is (4, 6)

- $4^1 = 4$
- $4^2 = 16$
- $4^3 = 64$
- $4^4 = 256$
- $4^5 = 1024$

NUMBERS	FREQN OF NOS. as POWER CYCLE
0, 1, 5, 6	STAY AS IT IS
2, 3, 7, 8	4
4, 9	2

a) $(766)^{136} \rightarrow$ unit digit = 6.

b) $(277)^{134} \rightarrow 4$

c) $(454)^{134} \rightarrow 2$

d) $(222)^{103} \rightarrow 4$

a) $(766)^{136} = 766 \times 766 \times 766 \times 766 \times \dots \times 766$ 136 times.
 $= \dots 6 \times \dots 6 \times \dots 6 \times \dots 6 \times \dots$
 $= \dots 6$

$(\dots 0/1/5/6)^{\alpha \times \alpha \times \dots \alpha} = \dots 0/1/5/6$

b) $(277)^{134} = 277 \times 277 \times 277 \times 277 \times \dots \times 277$ 134 times.
 $= \dots 7 \times \dots 7 \times \dots 7 \times \dots 7 \times \dots$ 134 times.

$\dots \times \dots \times \dots \times \dots \times (277 \times 277)$

\downarrow
 49
 \downarrow
 units digit is (9)

33 ← Complete sections.

$4 \overline{) 134}$
 $\underline{12}$
 14
 $\underline{12}$
 $x 2$

↗

Short cut:

$(277)^{134} \rightarrow$ Power cycle = 4
 $\frac{134}{4} = 33$
 $4 \overline{) 134}$
 $\underline{12}$
 $x 14$
 $\underline{12}$
 $x 2$
 $x 7 = 49$
 \downarrow
 units place (units digit)

* $(454)^{41} \rightarrow$ Power cycle = 2

$$\begin{array}{r} 20 \\ 2 \overline{) 41} \\ \underline{40} \\ x1 \end{array}$$

$4^1 = 4$

* $(888)^{103} \rightarrow$ Power cycle = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 103} \\ \underline{100} \\ 3 \end{array}$$

$8^3 = 512$

* $(1028)^{100} \rightarrow$ Power cycle = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 100} \\ \underline{100} \\ 000 \leftarrow \text{Remainder} \end{array} \quad \times$$

$8^0 = 1$

* $(459)^{40} \rightarrow$ Power cycle = 2

Remainder = 0

* Special case of Remainder zero:

* All complete sections.

* NO incomplete section.

$(1028)^{100} \rightarrow$ P.C = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 100} \\ \underline{100} \\ xxx \\ 0 \end{array}$$


$8^4 = 8^2 \times 8^2$
 $= 64 \times 64$
 $= \dots \dots (6)$

* $(459)^{40} \rightarrow$ P.C = 2

$$\begin{array}{r} 20 \\ 2 \overline{) 40} \\ \underline{40} \\ 00 \end{array}$$

$9^2 = 9 \times 9 = 81$

* Remainder 0 short cut:

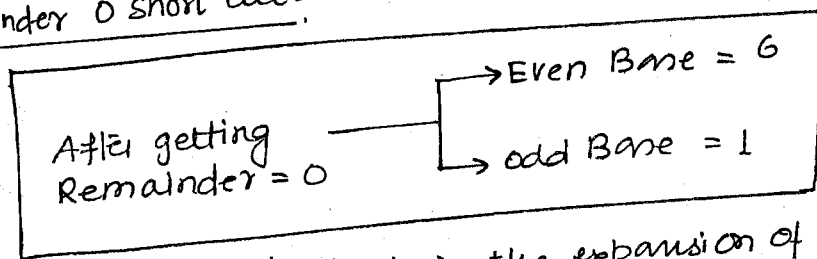

Q4) What is the unit's digit in the expansion of the following expression:

$(666)^{666} \times (877)^{134} + (959)^{20}$

$$\begin{array}{r} 33 \\ 4 \overline{) 134} \\ \underline{132} \\ 2 \end{array}$$


$7^2 = 49$

Soln: $(\dots 6 \times \dots 9) + \dots + 1$
 $= (\dots 4) + (\dots 1) = \dots 5$

$$\begin{array}{r} 5 \\ 9 \overline{) 20} \\ \underline{20} \\ 00 \end{array}$$

$(959) \rightarrow$ odd Base = 1

SUMMARY

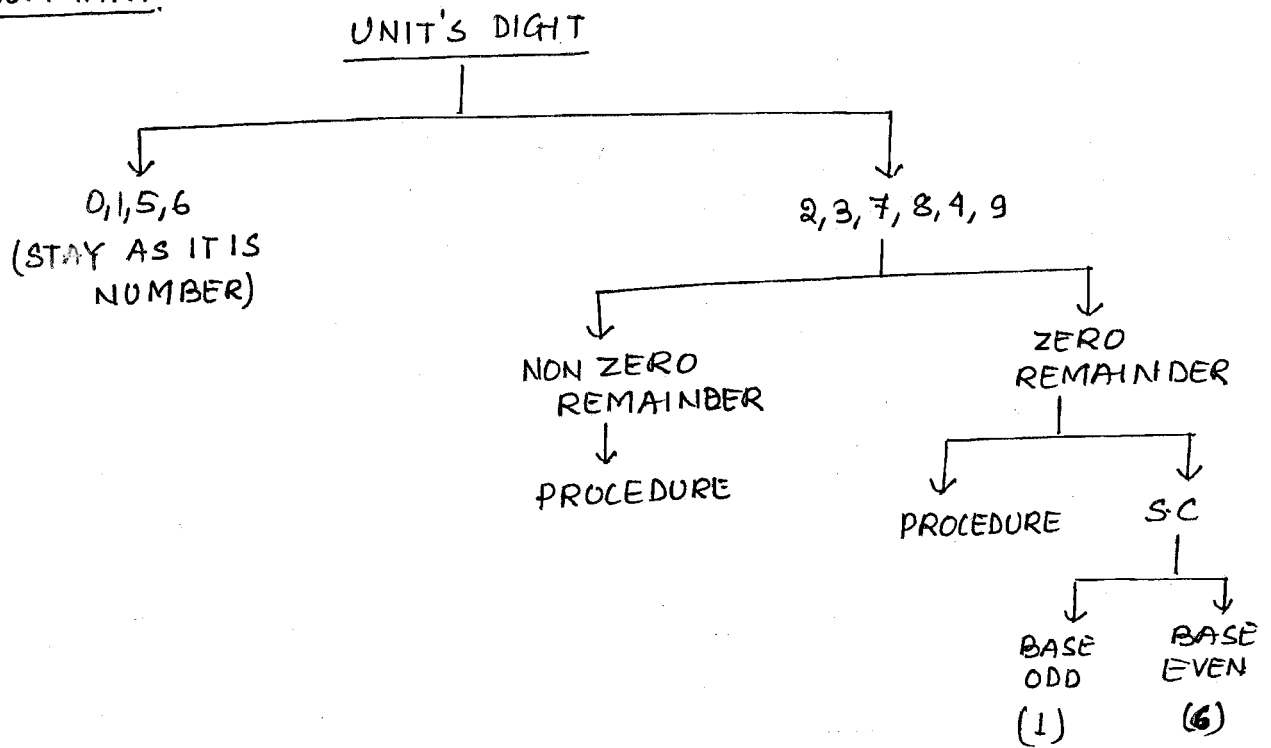

Q) How many zeroes are there at last in the expansion of

a) $25 \times 4 \times 8 \times 7 \times 10 \times 16 \times 100$

b) $(25)^{125} \times 4^{40}$

Soln:

a) $25 \times 4 \times 8 \times 7 \times 10 \times 16 \times 100$
 $100 \times 56 \times 16 \times 1000$
 $= 56 \times 16 \times 100000$

b) $(25)^{125} \times (4)^{40}$

$(5)^{250} \times 2^{80}$
 ← LEAST POWER
 80 ZERO

$5^2 \times 2^2 \times 2^3 \times 7 \times 5 \times 2 \times 2^4 \times 2^2 \times 5^2$
 $= 2^{12} \times 5^5 = 2^7 \times 2^5 \times 5^5$ ← least power
 $= 2^7 \times 10^5$
 $= 5 \text{ ZEROS}$

Note: $7^{125} \times 4^{50}$
 $7^{125} \times 2^{100}$
 NO ZEROS

ZERO'S AT LAST CONDITION ∴

- i) Multiple of 10. → direct multiple ie 10, 100, 1000, ...
- ii) Hidden multiple → (2, 5)

*The total no. of (2x5) combinations = no. of zeroes at last in the expansion

(total no. of (2x5) combⁿ) = (no. of zeroes at last in expansion)

Q6) How many zeros are there at last in the expansion of !.

- a) 6!
- b) 10!
- c) 100!
- d) 145!
- e) 1000!

Note !.

1! ; 2! = 2 ; 3! = 6 ; 4! = 24

5! = 120

↓ onwards only zeros will start coming not before that.

Soln a) 6! = 6x5x4x3x2x1
 = 6x5¹x3x2³
 = 1 ZERO.

720

b) 10! = 10x9x8x7x6x5x4x3x2x1
 = 2x5x9x2³x7x3x2x5x2²x3x2x1
 = 2⁸x5²
 = 2 ZEROS

(3628800)

c) 100!

- ↓
- 100 → 20x5
- 95 → 19x5
- 90 → 18x5
- 85 → 17x5
- 80 → 16x5
- 75 → 15x5 = 3x5x5
- 70 → 14x5

- 65 → 13x5
- 60 → 12x5
- 55 → 11x5
- 50 → 10x5 = 2x5x5
- 45 → 9x5
- 40 → 8x5
- 35 → 7x5
- 30 → 6x5
- 25 → 5x5
- 20 → 5x4
- 15 → 3x5
- 10 → 2x5
- 5 → 1x5

Note ∴ for 100! Zeros are by default. They will come by default and no. of zeros depends on no. of 5's present in it.

100! = 1x2x3x4x5x6x7x8x9x10x11x12x13x14x15x16x17x18x19x20x...x100

$\frac{100}{5} = 20$ sections ← divide the complete 100! in 20 sections.

* In these sections some special nos (which contain 2 5's will also be there). such as:

Already taken into account in dividing sections.


25 → 5x5 (NOT TAKEN INTO ACCOUNT IN 20 SECTIONS)

50 → 5x5x2

75 → 5x5x3

100 → 5x5x4

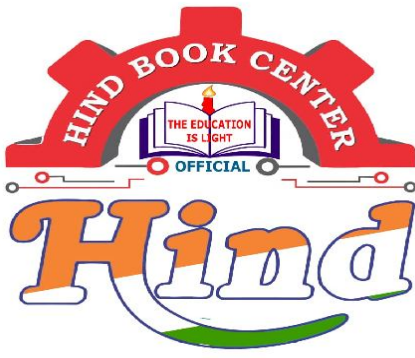→ NOW taking = $\frac{100}{5} + \frac{100}{25} = 24$.



Hindbookcenter



Hind Book Center & Photostat

MADE EASY

IES/GATE/PSUs

Toppers Handwritten Notes


MATHEMATICS

By-RAMU MALADI Sir

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT
- All Notes Available & All Book Availabile
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

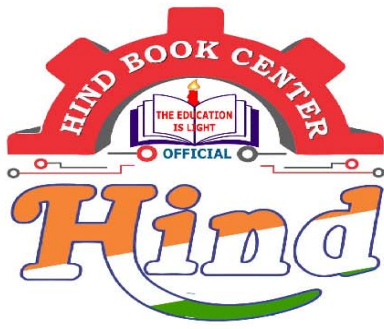Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393


* LINEAR ALGEBRA ∴

Analysis

$$\begin{aligned}x+2y &= 3 \\ 2x+3y &= 5\end{aligned}$$

$$\text{So, } x=1, y=1$$

Intersecting line

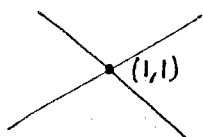

(x' and y')

* Any 1st degree 2 dimensional equation in $x+y$ represents a line in the XY PLANE. (LINEAR SYSTEM OF EQUATION IN 2 VARIABLES)

Note ∴

* The study of LINEAR SYSTEM OF EQUATIONS is called LINEAR ALGEBRA.

$$\begin{aligned}x+2y &= 3 \\ 2x+3y &= 5\end{aligned}$$

On solving the equation

$$x=1; y=1$$

(UNIQUE SOLUTION)

$$\begin{aligned}x+2y &= 3 \\ 2x+4y &= 6\end{aligned}$$

let $y=k$

$$x=3-2k$$

(INFINITE NO. OF SOLUTION)

$$\begin{aligned}x+2y &= 3 \\ x+2y &= 5\end{aligned}$$

(NO SOLUTION)

* To study about the linear system of equations, we require the concept "RANK OF MATRIX". Hence we study about MATRICES in the concept LINEAR ALGEBRA.

* MATRIX ∴

* Arrangement of elements or numbers in Rows and Columns such that each row will have same no. of element and each column will have same no. of element is called a MATRIX.

*Operation on Matrices:

- 1) Addition
- 2) Subtraction
- 3) Multiplication $\{ A_{m \times l} \times B_{l \times n} = C_{m \times n} \}$
- 4) TRACE OF SQUARE MATRIX:

*The sum of the PRINCIPAL DIAGONAL ELEMENTS OF A SQUARE MATRIX is called TRACE.

5) SYMMETRIC MATRIX:

When $A^T = A$

$$\begin{bmatrix} 1 & 5 & -1 \\ 5 & 2 & 9 \\ -1 & 9 & 3 \end{bmatrix}$$

the matrix A is ~~is~~ Symmetric

6) SKEW SYMMETRIC MATRIX:

When $A^T = -A$

$$\begin{bmatrix} 0 & 3 & -5 \\ -3 & 0 & 9 \\ 5 & -9 & 0 \end{bmatrix}$$

then Matrix A is SKEW SYMMETRIC.

COMPULSORY CONDITION
(diagonal elements should be zero)

*DETERMINANT OF SQUARE MATRIX:

*For a 1x1 MATRIX, the no. ~~itself~~ itself is the Determinant

*For a 2x2 MATRIX of the form:

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

the determinant is given by (ad-bc)

*MINOR OF AN ELEMENT:

let

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

then Minor of $a_{11} = \begin{vmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{vmatrix} = (a_{22}a_{33} - a_{32}a_{23})$

Minor of $a_{21} = \begin{vmatrix} a_{12} & a_{13} \\ a_{32} & a_{33} \end{vmatrix} = (a_{12}a_{33} - a_{32}a_{13})$

* COFACTOR of an element :-

* Minor of a_{ij} is M_{ij} ; then cofactor of a_{ij} is

$$\text{Cofactor of } a_{ij} = (-1)^{i+j} \cdot M_{ij}$$

* The Determinant of square matrix is defined as "The sum of product of elements of any row or any column with the corresponding cofactors"

* Analysis :-

let $A = \begin{bmatrix} 1 & 0 & 2 & 1 \\ 1 & 0 & 1 & -1 \\ 1 & 2 & 3 & 1 \\ 1 & 0 & 2 & 0 \end{bmatrix}$

* we have to find the determinant of given 4×4 matrix. For this choose any row or column having the max^m no. of zeroes.

using 2nd column we get:

$$\begin{aligned} & 2(-1)^{3+2} \begin{vmatrix} 1 & 2 & 1 \\ 1 & 1 & -1 \\ 1 & 2 & 0 \end{vmatrix} \\ & \rightarrow \{ 1(0+2) - 2(0+1) + 1(2-1) \} \\ & = -2 \end{aligned}$$

using 4th column we get

$$\begin{aligned} & 1 \cdot (-1)^{4+1} \begin{vmatrix} 0 & 2 & 1 \\ 0 & 1 & -1 \\ 2 & 3 & 1 \end{vmatrix} + 2(-1)^{4+3} \begin{vmatrix} 1 & 0 & 1 \\ 1 & 0 & -1 \\ 1 & 2 & 1 \end{vmatrix} \\ & = -1 \{ 2(2) + 1(-2) \} - 2 \{ 1(1+2) + 1(-2) \} \\ & = -6 - 8 = -14 \end{aligned}$$

Note :-

* A matrix is said to be NON SINGULAR when

$$\text{DET}(A) \neq 0$$

and is said to be SINGULAR when

$$\text{DET}(A) = 0$$

** $\text{Det}(A \cdot B) = (\text{Det } A)(\text{Det } B)$

** $\text{Det}(A+B)$ is not necessarily $(\text{Det } A) + (\text{Det } B)$

** If any two rows are same or constant multiples (columns) then Determinant of that Matrix is zero.

** If ~~one~~ ^{SUM} of the elements in every row or every column is zero then the determinant of such matrix is zero.

for eg.

$$\begin{bmatrix} 1 & 2 & -3 \\ 0 & 2 & -2 \\ 1 & 1 & -2 \end{bmatrix} \left[\begin{array}{l} \leftarrow \\ \leftarrow \\ \leftarrow \end{array} \right. \text{Sum of Rows zero.} \\ \text{(Sum of each row is zero).}$$

* ADJOINT OF SQUARE MATRIX :

* It is the Transpose of Cofactor Matrix ie

$$\text{if } A = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

then the cofactor of $a_{ij} = A_{ij}$

$$\text{then } \text{Adj } A = \begin{bmatrix} A_{11} & A_{21} & A_{31} \\ A_{12} & A_{22} & A_{32} \\ A_{13} & A_{23} & A_{33} \end{bmatrix}$$

NOTE :

** $A(\text{adj } A) = (\det A) I$ $I \rightarrow$ Identity matrix.

** $\det(\text{adj } A) = (\det A)^{n-1}$; $n =$ order of matrix

** $\text{Adj}(\text{adj } A) = (\det A)^{n-2} A$

* INVERSE OF SQUARE MATRIX :

* A matrix B is said to be inverse of a non singular matrix A if

** $AB = BA = I$

* To find A^{-1} we have

** $A^{-1} = \frac{\text{Adj } A}{\det A}$

* For Matrix A;

$$A = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

** $A^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$; $ad-bc \neq 0$

$$\det(A^T) = \frac{1}{(\det A)}$$

ELEMENTARY TRANSFORMATION ON A MATRIX:

*There are only 3 elementary transformations; they are:

✓1) Interchanging of any two rows ($R_1 \leftrightarrow R_2$)

✓2) Multiplication of a row by a constant ($R_2 \rightarrow 3R_2$)

✓3) Addition of 1 row to the corresponding elements of some other row ($R_2 \rightarrow R_2 + R_1$).

Note:.

* $R_2 \rightarrow R_2 + 3$
 * $R_2 \rightarrow R_2 \times R_1$ } Not elementary ximation.

*Inverse of Matrix (using elementary ximation)

GAUSS JORDAN METHOD:

Q1) Find the Inverse of

Use this element to make all the elements below/above this as zero.

$$A = \begin{bmatrix} 1 & 3 & 3 \\ 1 & 4 & 3 \\ 1 & 3 & 4 \end{bmatrix}$$

Soln:

$$\left[\begin{array}{ccc|ccc} 1 & 3 & 3 & 1 & 0 & 0 \\ 1 & 4 & 3 & 0 & 1 & 0 \\ 1 & 3 & 4 & 0 & 0 & 1 \end{array} \right]$$

$$(R_2 \rightarrow R_2 - R_1); (R_3 \rightarrow R_3 - R_1)$$

$$\left[\begin{array}{ccc|ccc} 1 & 3 & 3 & 1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

$$(R_1 \rightarrow R_1 - 3R_2)$$

$$\left[\begin{array}{ccc|ccc} 1 & 0 & 3 & 4 & -3 & 0 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

$$R_1 \rightarrow R_1 - 3R_3$$

$$\left[\begin{array}{ccc|ccc} 1 & 0 & 0 & 7 & -3 & -3 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

Hence,

$$A^{-1} = \begin{bmatrix} 7 & -3 & -3 \\ -1 & 1 & 0 \\ -1 & 0 & 1 \end{bmatrix}$$

(Q2) Find the inverse of $A = \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 1 & 0 & -2 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$

Soln: By Gauss Jordan method:

$$\left[\begin{array}{cccc|cccc} 1 & 0 & 0 & 3 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -2 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{array} \right]$$

$(R_1 \rightarrow R_1 - 3R_4); (R_2 \rightarrow R_2 + 2R_4)$

$$\left[\begin{array}{cccc|cccc} 1 & 0 & 0 & 0 & 1 & 0 & 0 & -3 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 & 2 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{array} \right]$$

So, $A^{-1} = \begin{bmatrix} 1 & 0 & 0 & -3 \\ 0 & 1 & 0 & 2 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$

*MINOR OF A MATRIX:

let

$$A = \begin{bmatrix} a_1 & b_1 & c_1 & d_1 & e_1 \\ a_2 & b_2 & c_2 & d_2 & e_2 \\ a_3 & b_3 & c_3 & d_3 & e_3 \\ a_4 & b_4 & c_4 & d_4 & e_4 \end{bmatrix} 4 \times 5$$

* For finding the No. of minors of given order choose no. of rows or columns from given no. of Rows or Columns.

Note:

- $(4 \times 4) \checkmark$ No. of minors of order 4 is 5. (${}^4C_4 \times {}^5C_4 = 5$)
- $(3 \times 3) \checkmark$ No. of minors of order 3 is ${}^4C_3 \times {}^5C_3 = 4 \times 10 = 40$ (choose any 3 rows or columns)
- $(2 \times 2) \checkmark$ No. of minors of order 2 is ${}^4C_2 \times {}^5C_2 = 6 \times 10 = 60$ (choose any 2 rows or columns).
- $(1 \times 1) \checkmark$ No. of minors of order 1 is $4 \times 5 = 20$.

* In general, for matrix $A_{m \times n}$:

i) ~~The~~ The no. of minors of order 'r' that can be generated is $({}^m C_r \times {}^n C_r)$.

ii) The order of greatest minor that can be obtained for this matrix is $\min(m, n)$. $\begin{cases} A_{5 \times 2} \Rightarrow A_{2 \times 2} \rightarrow \text{greatest minor } \neq \text{NO}(A_{3 \times 3}). \\ A_{3 \times 7} \rightarrow A_{3 \times 3} \rightarrow \text{greatest minor } \neq \text{NO}(A_{4 \times 4}). \end{cases}$

RANK OF A MATRIX :

*Exists for both square as well as Rectangular matrix.

*A no. "r" is said to be the "RANK OF A MATRIX A" if :

- i) there exist a minor of order "r" of A which is not zero.
- ii) all minors of order more than "r" of A must be zero.

for eg.:

*All red dotted minors A =

$$\begin{bmatrix} 1 & 2 & 3 \\ 2 & 4 & 6 \\ 3 & 6 & 10 \end{bmatrix}$$

have det = 0.

*Green dotted minor donot then have det = 0.

$$\det A = 0$$

and

$$\det \begin{bmatrix} 4 & 6 \\ 6 & 10 \end{bmatrix} \neq 0 \Rightarrow 40 - 36 = 4$$

*Note: For given 3x3 matrix, the Minor of 3rd order is the given matrix itself. Also the det. of given minor is zero Hence, also no. other minor of order 4x4 is available Hence the matrix A cannot have P(A)=3. We need to search for 2x2 minor and check for availability of such minor whose det ≠ 0.

Hence, there exist a minor of order 2x2 whose det is not zero. Hence

$$\begin{array}{l} \text{Rank} = 2 \\ P(A) = 2 \end{array}$$

← Rank of Matrix can also be defined as the order of Largest non zero minor of the matrix (Here 2x2 minor).

Note:

*To find the Rank of the matrix we can use ELEMENTARY OPERATIONS.

*By converting, the given matrix into its "ECHELON FORM"; the no. of NON ZERO ROWS in the "ECHELON FORM IN THE MATRIX" represents the rank of the matrix.

Note: Calculation of Rank through Minor calculation is very time taking. Hence we use Rank calculation through "ECHELON FORM".

*ECHELON FORM:

*By applying elementary transformations we can convert a given matrix into a form in which :

i) All zero rows must be present below non zero rows.

ii) In the non zero rows; the no. of zeroes before the 1st non zero no. to the next row must increase.

*Such a form is called "ECHELON FORM OF GIVEN MATRIX".

Q3) Find the Rank of :

$$A = \begin{bmatrix} -2 & -1 & -3 & -1 \\ 1 & 2 & 3 & -1 \\ 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

*Note: Going through MINOR Calculations to obtain RANK OF MATRIX is time taking. Hence ECHELON FORM FORMATION is used to calculate the Rank of A MATRIX

$$P(A) = \text{RANK OF MATRIX A}$$

$$A = \begin{bmatrix} -2 & -1 & 3 & -1 \\ 1 & 2 & 3 & -1 \\ 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

$$R_2 \rightarrow 2R_2 + R_1$$

$$R_3 \rightarrow 2R_3 + R_1$$

* NO Zeros before (-)

* 1 Zero before 3.

Hence no. of zero increased from going from 1st row to 2nd row.

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & -1 & -1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

* 1 Zero before (-)

hence no increase in no. of zero from 2nd to 3rd row.

Hence not in ECHELON FORM.

$$R_3 \rightarrow 3R_3 + R_2$$

$$R_4 \rightarrow 3R_4 - R_2$$

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

All zero Row present below Non zero Row.

$$\boxed{\rho(A) = 2}$$

Note: (Assumption) ↓

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & 0 & 0 & 5 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

matrix in Echelon form only.

$$\boxed{\rho(A) = 3}$$

Q4) Find the Rank of

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 3 & 4 & 5 & 6 & 7 \\ 4 & 5 & 6 & 7 & 8 \\ 5 & 6 & 7 & 8 & 9 \end{bmatrix}$$

Soln:

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 3 & 4 & 5 & 6 & 7 \\ 4 & 5 & 6 & 7 & 8 \\ 5 & 6 & 7 & 8 & 9 \end{bmatrix}$$

$$R_2 \rightarrow 2R_2 - 3R_1$$

$$R_3 \rightarrow R_3 - 2R_1$$

$$R_4 \rightarrow 2R_4 - 5R_1$$

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & -3 & -6 & -9 & -12 \end{bmatrix}$$

$$R_3 \rightarrow R_3 - R_2$$

$$R_4 \rightarrow R_4 - 3R_2$$

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\boxed{\rho(A) = 2}$$